



Lecture 12

- Frequency Response




Outline


- Frequency response
- Transfer function
- Bode plots (or diagram)
- Resonance



Frequency Response

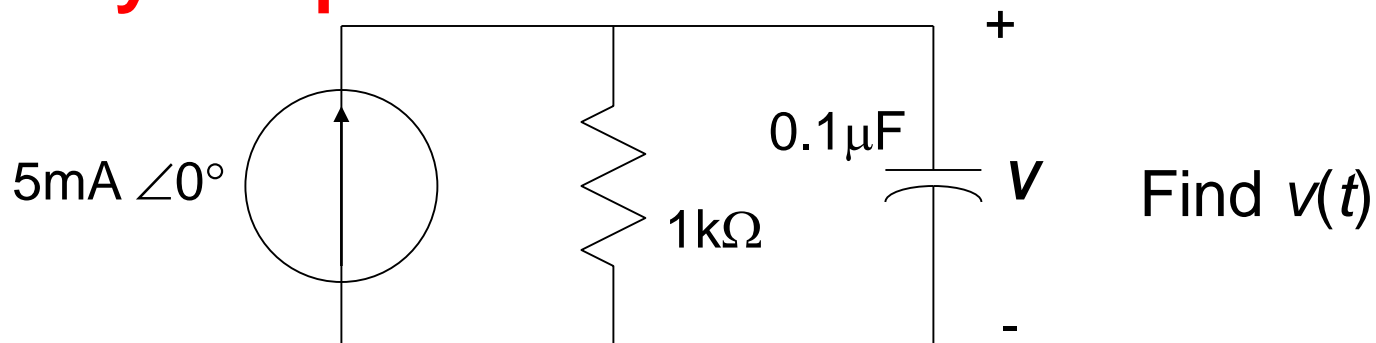


Case 1: $\omega = 2\pi \times 3000$

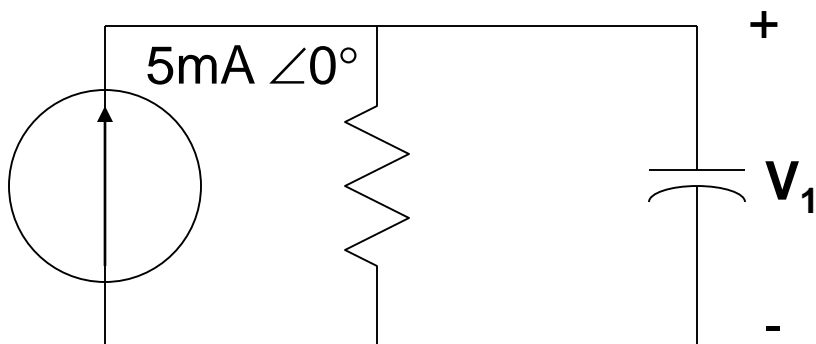

$$\mathbf{Z}_{eq} = 468.2 \angle -62.1^\circ \Omega$$

$$\mathbf{V}_1 = 2.34 \angle -62.1^\circ \text{V}$$


Case 2: $\omega = 2\pi \times 455000$

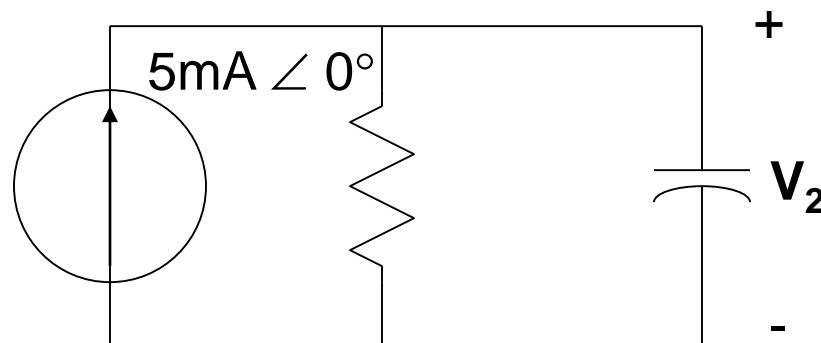

$$\mathbf{Z}_{eq} = 3.5 \angle -89.8^\circ \Omega$$

$$\mathbf{V}_2 = 17.5 \angle -89.8^\circ \text{mV}$$

Frequency Response

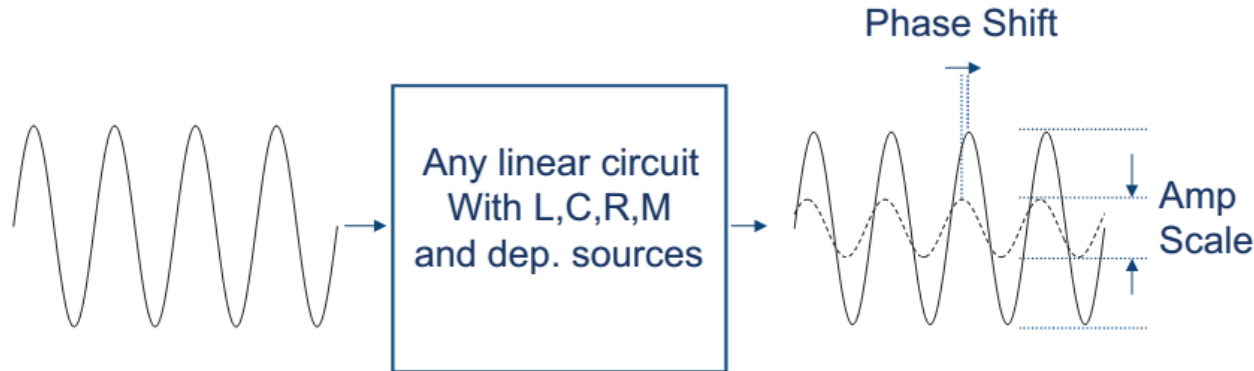

- When a linear, time invariant (LTI) circuit is excited by a sinusoid, its output is a sinusoid at the *same* frequency.
 - Only the magnitude and phase of the output differ from the input.
- The “Frequency Response” is a characterization of the input-output response for sinusoidal inputs at all frequencies.
 - Significant for applications, esp. in communications and control systems.




Outline

- Frequency response
- Transfer function
- Bode plots (or diagram)
- Resonance

Transfer Function

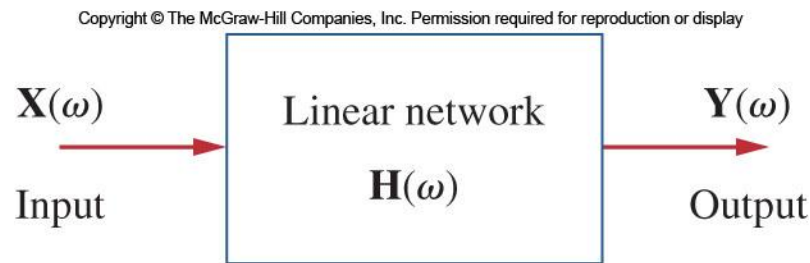- The transfer function $H(\omega)$ is the frequency-dependent ratio of a forced function $Y(\omega)$ to the forcing function $X(\omega)$.



$$H(\omega) = \frac{Y(\omega)}{X(\omega)}$$

$$H(\omega) = \text{Voltage gain} = \frac{V_o(\omega)}{V_i(\omega)}$$


$$H(\omega) = \text{Current gain} = \frac{I_o(\omega)}{I_i(\omega)}$$

$$H(\omega) = \text{Transfer impedance} = \frac{V_o(\omega)}{I_i(\omega)}$$

$$H(\omega) = \text{Transfer admittance} = \frac{I_o(\omega)}{V_i(\omega)}$$

Transfer Function – Voltage Gain

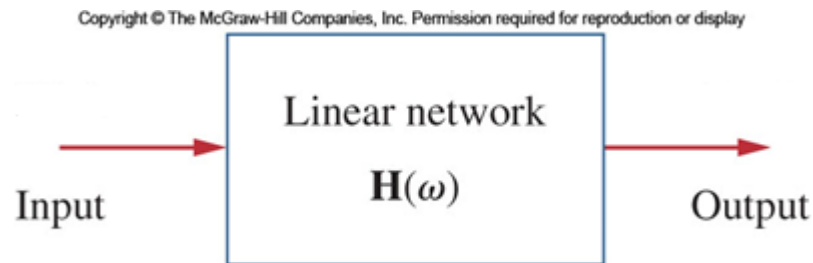- Complex quantity
- Both magnitude and phase are function of frequency





$$\mathbf{H}(f) = \frac{\mathbf{V}_{out}}{\mathbf{V}_{in}} = \frac{V_{out}}{V_{in}} \angle (\theta_{out} - \theta_{in})$$

$$\mathbf{H}(f) = H(f) \angle \theta$$





Example

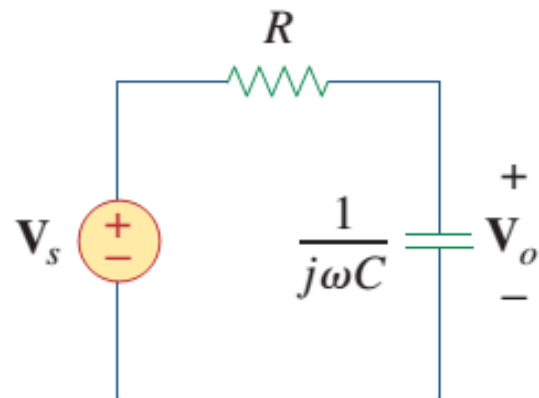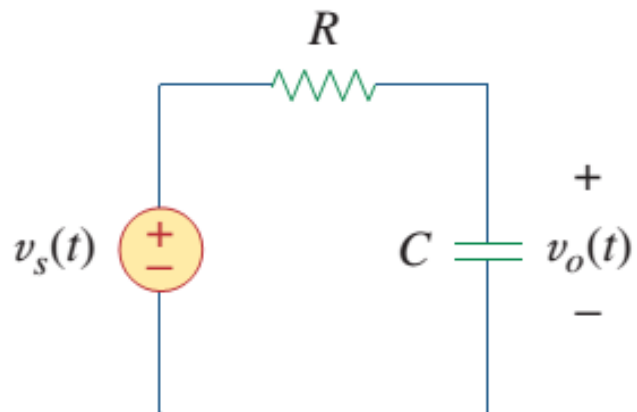






$$H = \frac{1}{\sqrt{1 + (\omega/\omega_0)^2}}, \quad \phi = -\tan^{-1} \frac{\omega}{\omega_0}$$

ω/ω_0	H	ϕ	ω/ω_0	H	ϕ
0	1	0	10	0.1	-84°
1	0.71	-45°	20	0.05	-87°
2	0.45	-63°	100	0.01	-89°
3	0.32	-72°	∞	0	-90°

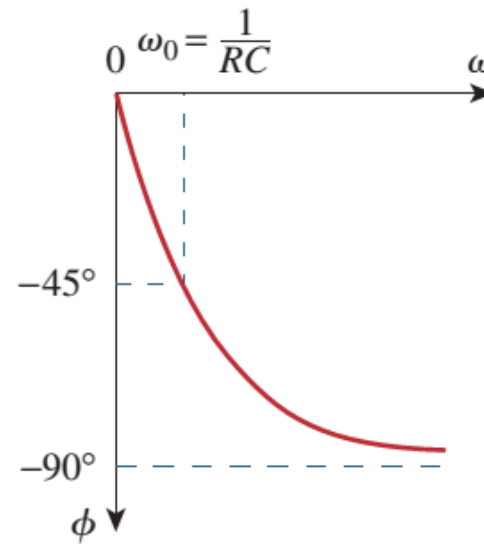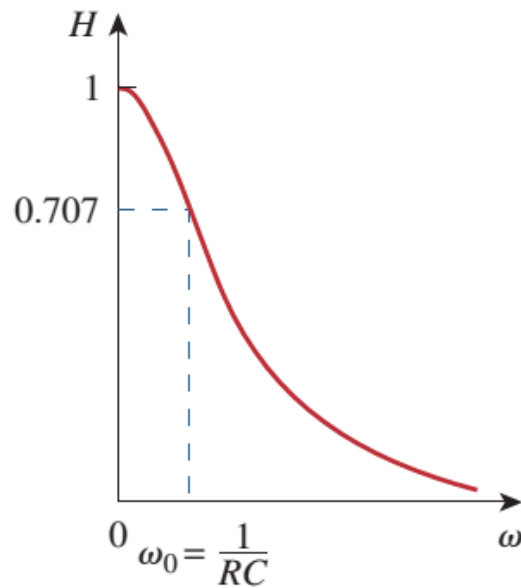

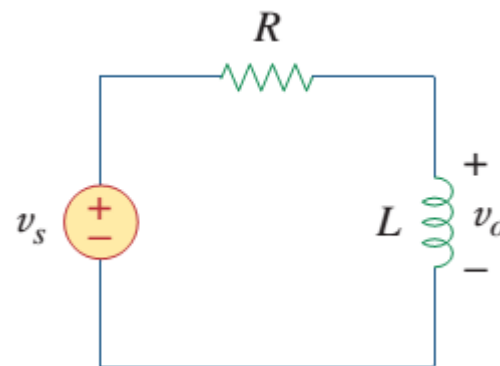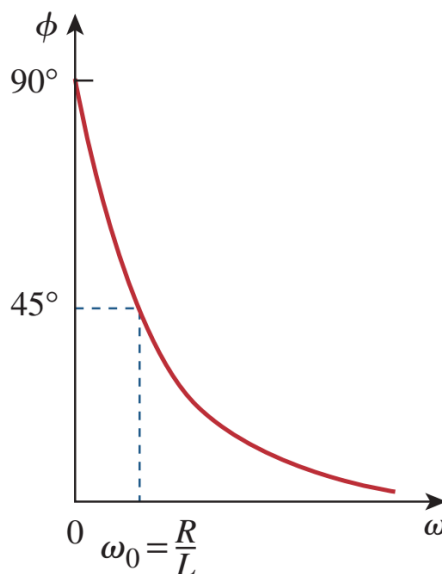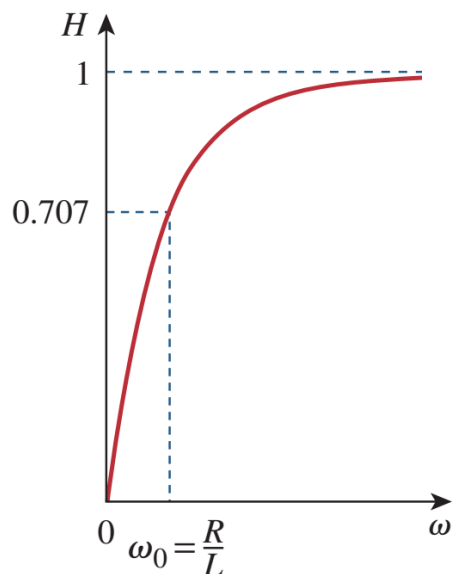Exercise

- Obtain the transfer function V_o/V_s of the RL circuit.
Assuming $v_s = V_m \cos \omega t$.






Outline

- Frequency response
- Transfer function
- Bode plots (or diagram)
- Resonance





Bode Plots

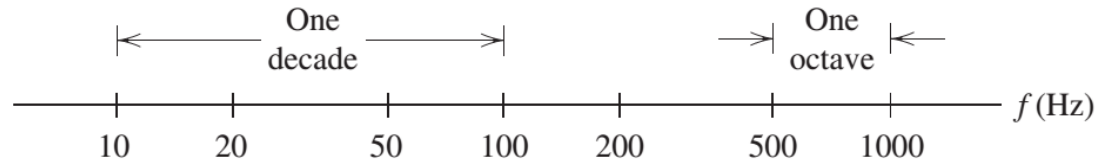

Plotting the frequency response, magnitude or phase, on plots with

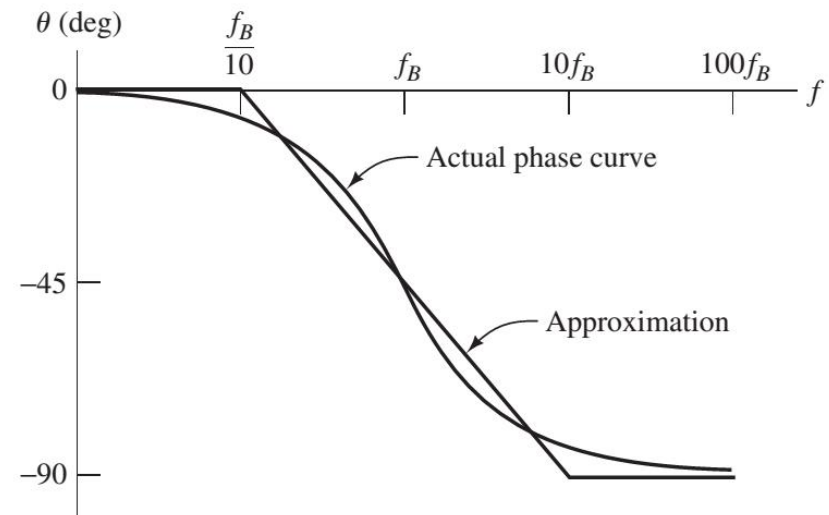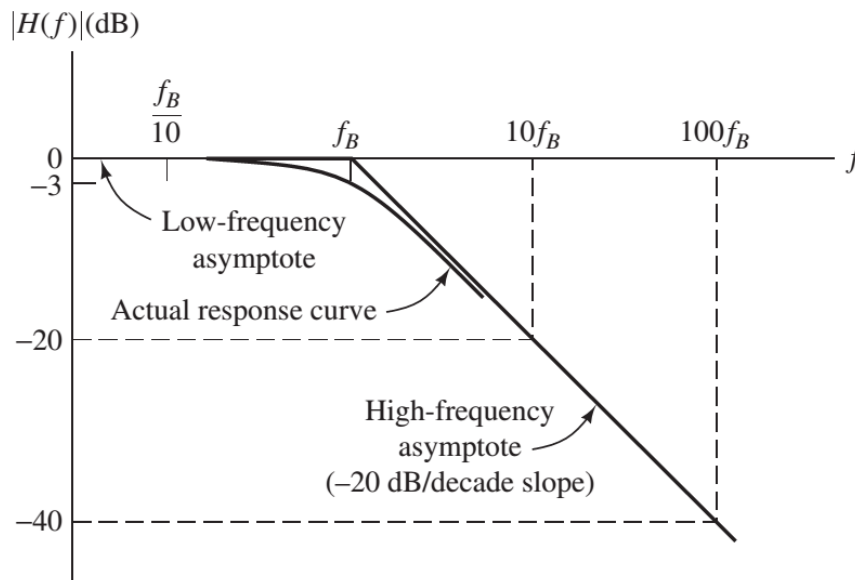- Frequency X in log scale
- Y scale in dB (for magnitude) or degree (for phase)





Bel and Decibel (dB)

- A **bel** (symbol **B**) is a unit of measure of ratios of power levels, i.e. relative power levels.
 - The name was coined in the early 20th century in honor of Alexander Graham Bell, a telecommunication pioneer.
 - Definition of bel:

$$\text{Ratio with a unit of B} = \log_{10}(P_1/P_2)$$

where P_1 and P_2 are power levels.

- One bel is too large for everyday use, so the **decibel (dB)**, equal to 0.1B, is more commonly used.

$$\text{Ratio with a unit of dB} = 10 \log_{10}(P_1/P_2)$$

- used to measure electric power, gain or loss of amplifiers, etc.



dB for Power

- To express a power in terms of decibels, one starts by choosing a reference power, $P_{\text{reference}}$, and write

$$\text{Power } P \text{ in decibels} = 10 \log_{10}(P/P_{\text{reference}})$$


- Exercise: Express a power of 50 mW in decibels relative to 1 watt and 1mW.

$$P \text{ (dB)} =$$

Decibel Scale


- The transfer function includes an expression of gain, which is typically expressed in log form.
 - in bels, or more commonly decibels
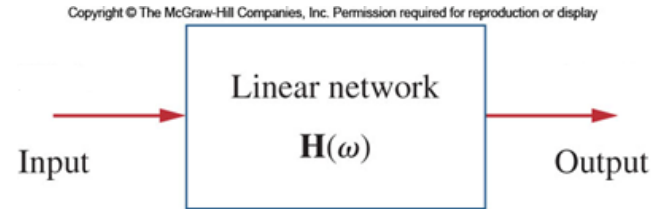
$$G_{dB} = 10 \log_{10} \frac{P_2}{P_1}$$





dB for Voltage or Current

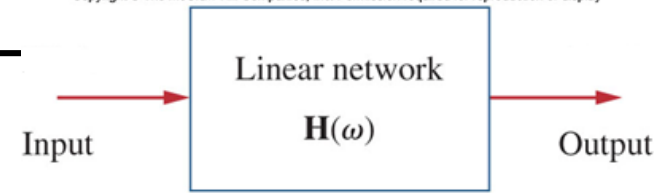

- We can similarly relate the reference voltage or current to the reference power, as

$$P_{\text{reference}} = (V_{\text{reference}})^2/R \text{ or } P_{\text{reference}} = (I_{\text{reference}})^2 R$$

Hence,

$$\begin{aligned} \text{Voltage, } V \text{ in decibels} &= 20\log_{10}(V/V_{\text{reference}}) \\ \text{Current, } I, \text{ in decibels} &= 20\log_{10}(I/I_{\text{reference}}) \end{aligned}$$

Question: How many decibels larger is the voltage of a 9-volt transistor battery than that of a 1.5-volt AA battery?

Question: The voltage gain of an amplifier with input = 0.2 mV and output = 0.5 V is ?



Summary

If G is defined as the power gain,

$$G = \frac{P}{P_0},$$

then the corresponding gain in dB is defined as

$$G \text{ [dB]} = 10 \log G = 10 \log \left(\frac{P}{P_0} \right) \quad (\text{dB}).$$


$$G \text{ [dB]} = 10 \log \left(\frac{\frac{1}{2} |\mathbf{V}|^2 / R}{\frac{1}{2} |\mathbf{V}_0|^2 / R} \right) = 20 \log \left(\frac{|\mathbf{V}|}{|\mathbf{V}_0|} \right)$$

$\frac{P}{P_0}$	dB
10^N	$10N$ dB
10^3	30 dB
100	20 dB
10	10 dB
4	$\simeq 6$ dB
2	$\simeq 3$ dB
1	0 dB
0.5	$\simeq -3$ dB
0.25	$\simeq -6$ dB
0.1	-10 dB
10^{-N}	$-10N$ dB

$\left \frac{\mathbf{V}}{\mathbf{V}_0} \right $ or $\left \frac{\mathbf{I}}{\mathbf{I}_0} \right $	dB
10^N	$20N$ dB
10^3	60 dB
100	40 dB
10	20 dB
4	$\simeq 12$ dB
2	$\simeq 6$ dB
1	0 dB
0.5	$\simeq -6$ dB
0.25	$\simeq -12$ dB
0.1	-20 dB
10^{-N}	$-20N$ dB





Bode Plots

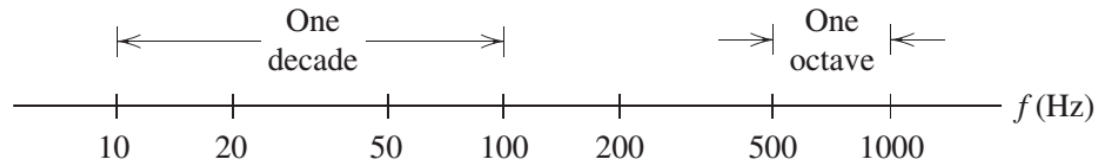

Plotting the frequency response, magnitude or phase, on plots with

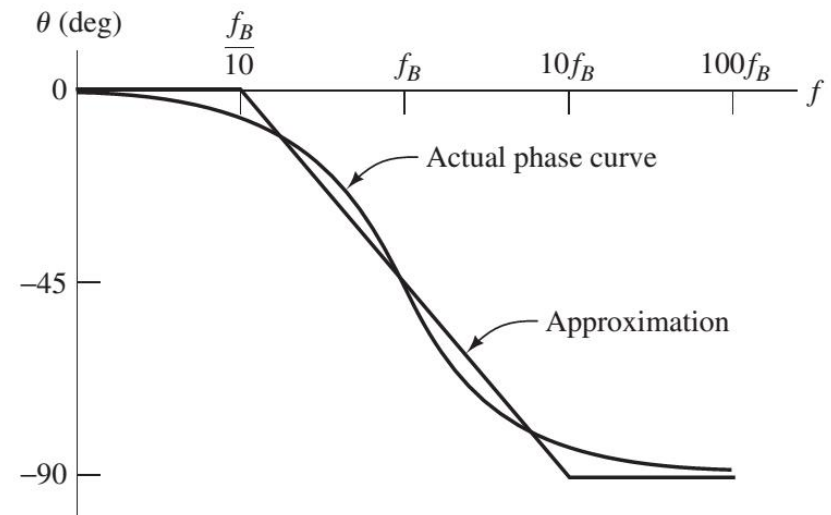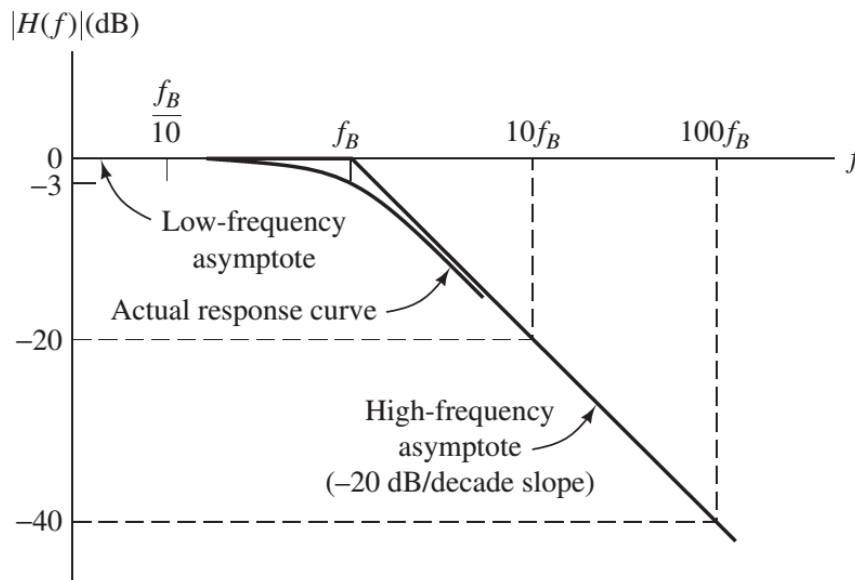- Frequency X in log scale
- Y scale in dB (for magnitude) or degree (for phase)





Bode Plots

- Bode plot is particularly useful for displaying transfer function-- a general form is displayed as:

$$\mathbf{H}(\omega) = \frac{K(j\omega)^{\pm 1} (1 + j\omega/z_1)[1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2]\cdots}{(1 + j\omega/p_1)[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2]\cdots}$$


In constructing a Bode plot, we plot each factor separately and then add them graphically. The factors can be considered one at a time and then combined additively because of the logarithms involved. It is this mathematical convenience of the logarithm that makes Bode plots a powerful engineering tool.




Constant term K

$$\mathbf{H}(\omega) = \frac{K(j\omega)^{\pm 1} (1 + j\omega/z_1)[1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2]\cdots}{(1 + j\omega/p_1)[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2]\cdots}$$

$K > 0$

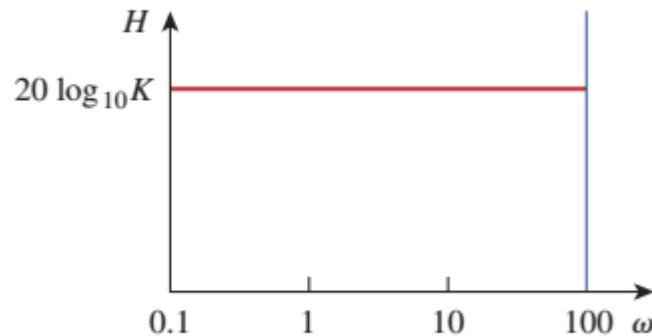

(a)

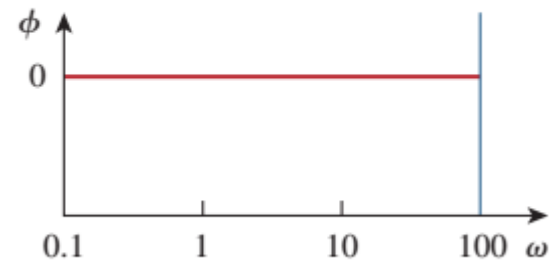


(b)

$K < 0$




$j\omega$
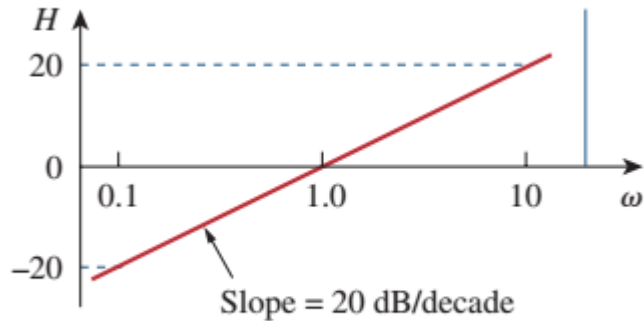
$$\mathbf{H}(\omega) = \frac{K(j\omega)^{\pm 1} (1 + j\omega/z_1)[1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2]\cdots}{(1 + j\omega/p_1)[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2]\cdots}$$



(a)

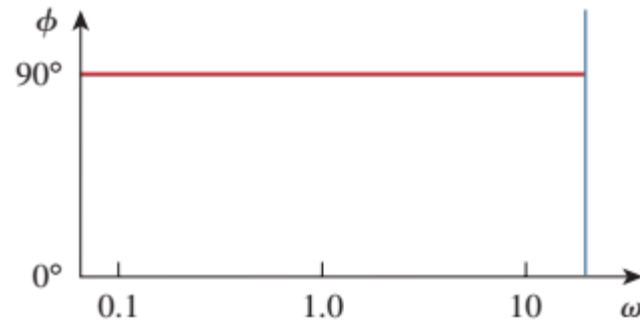


(b)

$(j\omega)^{-1}$




$j\omega$
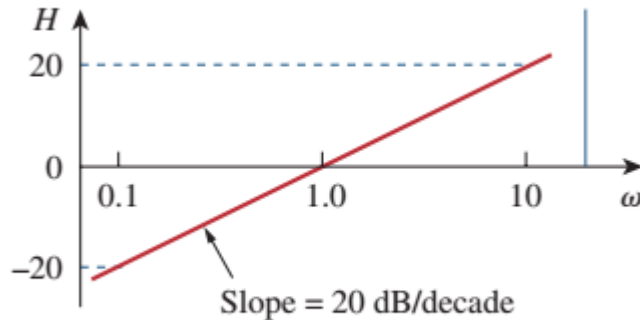
$$\mathbf{H}(\omega) = \frac{K(j\omega)^{\pm 1} (1 + j\omega/z_1)[1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2]\cdots}{(1 + j\omega/p_1)[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2]\cdots}$$




(a)

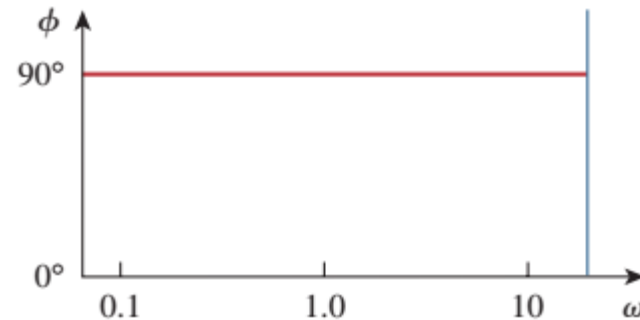

(b)

- In general:

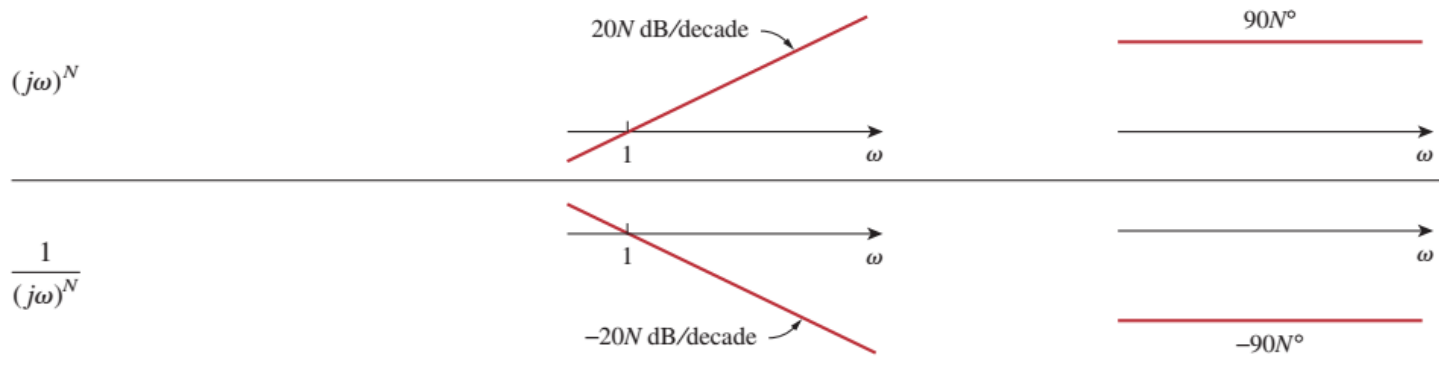



$$1 + j\omega/z_1$$

$$\mathbf{H}(\omega) = \frac{K(j\omega)^{\pm 1} (1 + j\omega/z_1)[1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2] \cdots}{(1 + j\omega/p_1)[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2] \cdots}$$


Simple pole/zero: For the simple zero $(1 + j\omega/z_1)$, the magnitude is $20 \log_{10} |1 + j\omega/z_1|$ and the phase is $\tan^{-1} \omega/z_1$. We notice that

$$H_{\text{dB}} = 20 \log_{10} \left| 1 + \frac{j\omega}{z_1} \right| \Rightarrow 20 \log_{10} 1 = 0$$


as $\omega \rightarrow 0$

$$H_{\text{dB}} = 20 \log_{10} \left| 1 + \frac{j\omega}{z_1} \right| \Rightarrow 20 \log_{10} \frac{\omega}{z_1}$$

as $\omega \rightarrow \infty$

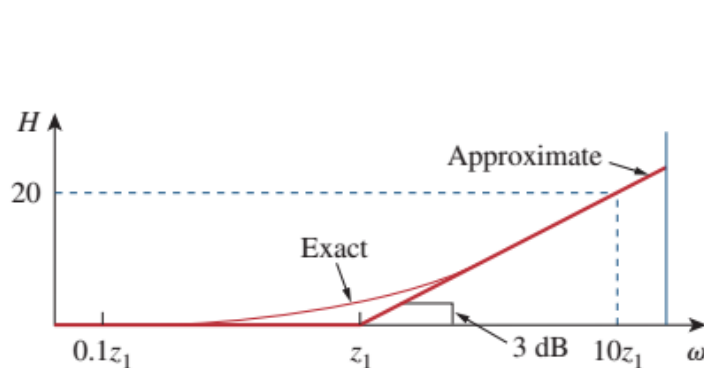

(a)

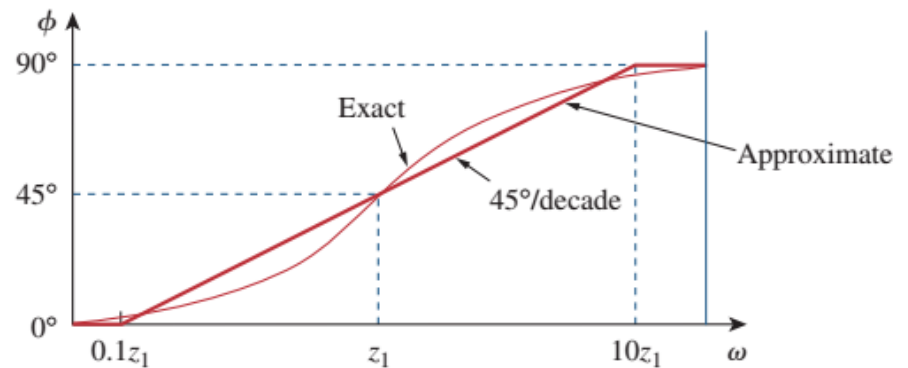

(b)



$$1/(1+j\omega/p_1)$$



$$1/[1+2j\zeta_1\omega/\omega_n + (j\omega/\omega_n)^2]$$

$$\mathbf{H}(\omega) = \frac{K(j\omega)^{\pm 1} (1 + j\omega/z_1)[1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2]\cdots}{(1 + j\omega/p_1)[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2]\cdots}$$


Magnitude:

$$H_{dB} = -20 \log_{10} \left| 1 + \frac{j2\zeta_2\omega}{\omega_n} + \left(\frac{j\omega}{\omega_n}\right)^2 \right| \Rightarrow 0$$

and

$$H_{dB} = -20 \log_{10} \left| 1 + \frac{j2\zeta_2\omega}{\omega_n} + \left(\frac{j\omega}{\omega_n}\right)^2 \right| \Rightarrow -40 \log_{10} \frac{\omega}{\omega_n}$$

as $\omega \rightarrow \infty$

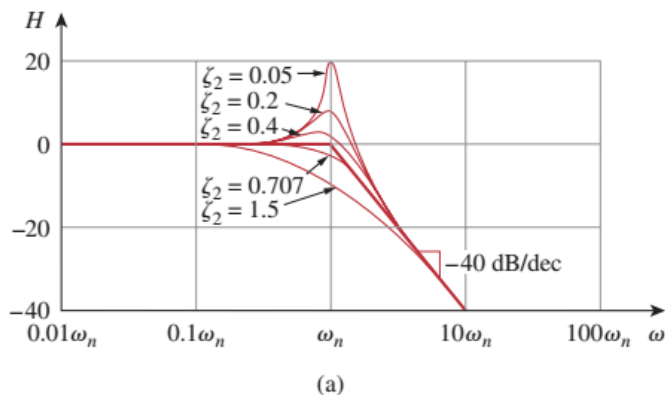

the phase is $-\tan^{-1}(2\zeta_2\omega/\omega_n)/(1 - \omega^2/\omega_n^2)$.




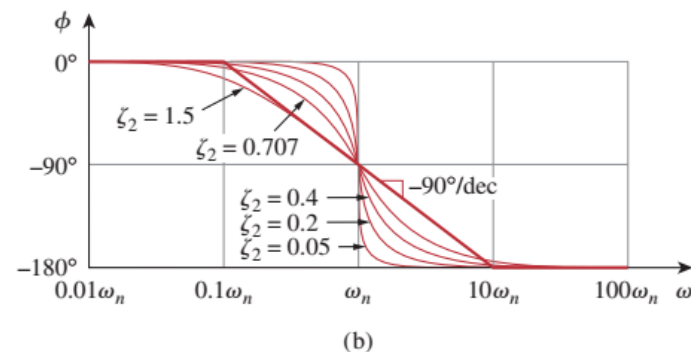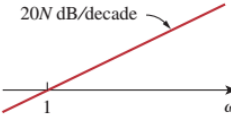

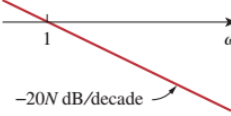
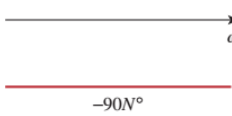
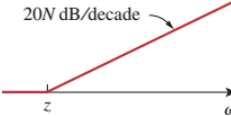
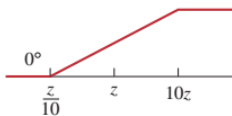
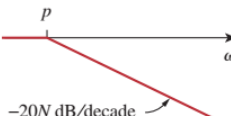
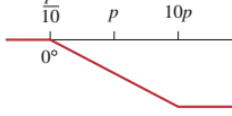



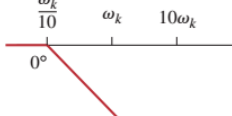




TABLE 14.3

Summary of Bode straight-line magnitude and phase plots.

Factor	Magnitude	Phase
K	 $20 \log_{10} K$	 0°
$(j\omega)^N$	 $20N \text{ dB/decade}$	 $90N^\circ$
$\frac{1}{(j\omega)^N}$	 $-20N \text{ dB/decade}$	 $-90N^\circ$
$\left(1 + \frac{j\omega}{z}\right)^N$	 $20N \text{ dB/decade}$	 0° , $90N^\circ$
$\frac{1}{(1 + j\omega/p)^N}$	 $-20N \text{ dB/decade}$	 0° , $-90N^\circ$
$\left[1 + \frac{2j\omega\zeta}{\omega_n} + \left(\frac{j\omega}{\omega_n}\right)^2\right]^N$	 $40N \text{ dB/decade}$	 0° , $180N^\circ$
$\frac{1}{[1 + 2j\omega\zeta/\omega_k + (j\omega/\omega_k)^2]^N}$	 $-40N \text{ dB/decade}$	 0° , $-180N^\circ$



Example--Standard Form


$$\mathbf{H}(\omega) = \frac{200j\omega}{(j\omega + 2)(j\omega + 10)}$$

$$\mathbf{H}(\omega) = \frac{10j\omega}{(1 + j\omega/2)(1 + j\omega/10)}$$



Example - Magnitude

$$\begin{aligned} \mathbf{H}(\omega) &= \frac{10j\omega}{(1 + j\omega/2)(1 + j\omega/10)} \\ &= \frac{10|j\omega|}{|1 + j\omega/2||1 + j\omega/10|} \angle 90^\circ - \tan^{-1} \omega/2 - \tan^{-1} \omega/10 \end{aligned}$$

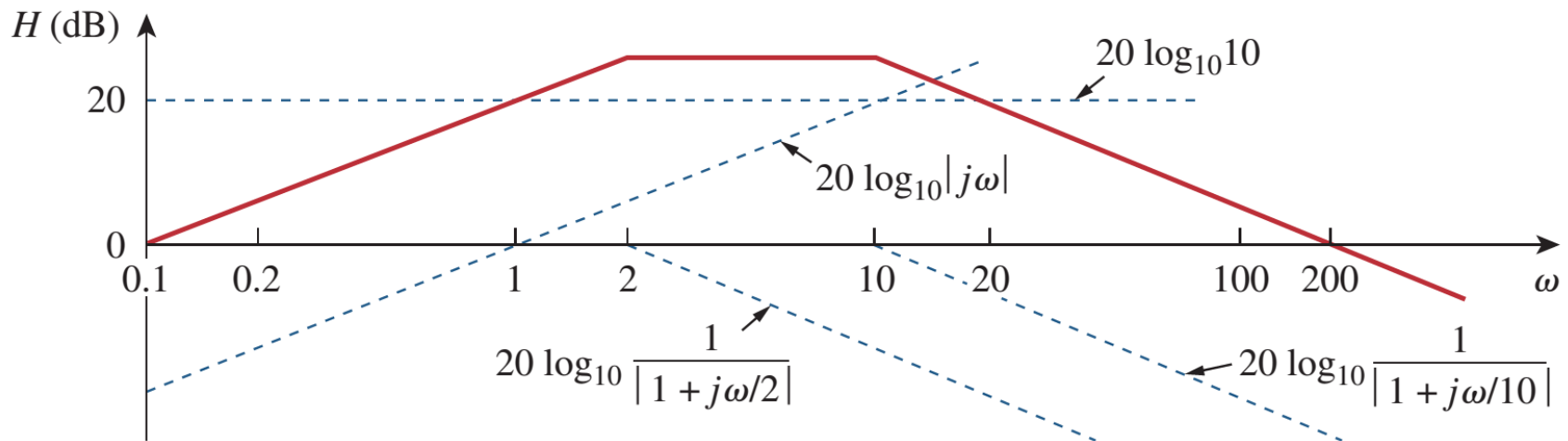


$$H_{\text{dB}} = 20 \log_{10} 10 + 20 \log_{10} |j\omega| - 20 \log_{10} \left| 1 + \frac{j\omega}{2} \right| - 20 \log_{10} \left| 1 + \frac{j\omega}{10} \right|$$



Example - Phase

$$\begin{aligned} \mathbf{H}(\omega) &= \frac{10j\omega}{(1 + j\omega/2)(1 + j\omega/10)} \\ &= \frac{10|j\omega|}{|1 + j\omega/2||1 + j\omega/10|} \angle \frac{90^\circ - \tan^{-1} \omega/2 - \tan^{-1} \omega/10}{} \end{aligned}$$
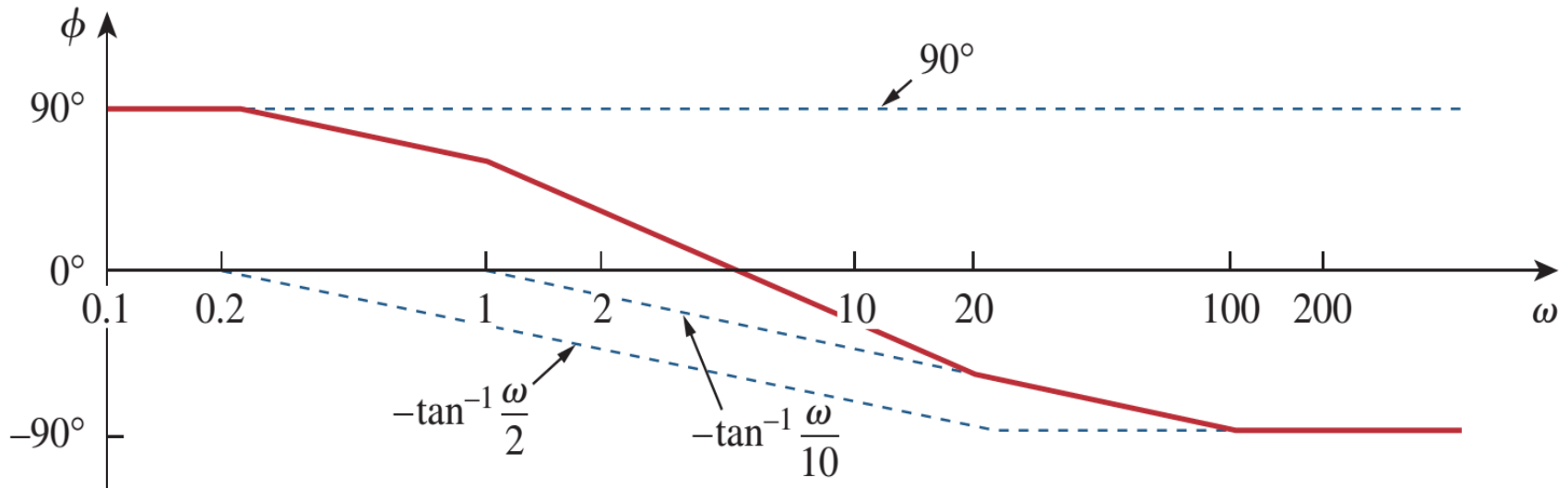
$$\phi = 90^\circ - \tan^{-1} \frac{\omega}{2} - \tan^{-1} \frac{\omega}{10}$$





Exercises

- $H(\omega) = K$
- $H(\omega) = (j\omega)^N$
- $H(\omega) = 1/(j\omega)^N$




Exercises

- $\mathbf{H}(\omega) = \frac{(20 + j4\omega)^2}{j40\omega(100 + j2\omega)}$
- $\mathbf{H}(\omega) = \frac{(j10\omega + 30)^2}{(300 - 3\omega^2 + j90\omega)}$



Obtain the transfer function

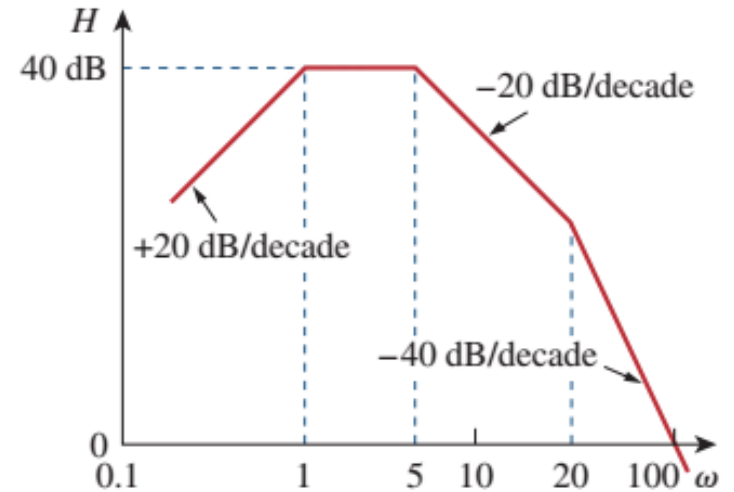




Outline

- Frequency response
- Transfer function
- Bode plots (or diagram)
- Resonance

Series Resonance

- A series resonant circuit consists of an inductor and capacitor in series.

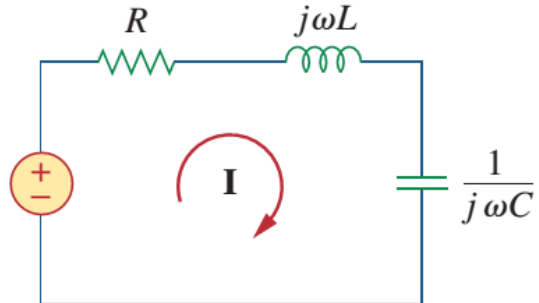
$$H(\omega) = \frac{V}{I} = \mathbf{Z} = R + j\left(\omega L - \frac{1}{\omega C}\right) \quad \mathbf{V}_s = V_m \angle \theta$$


- Resonance occurs when the imaginary part of Z is zero.
- The value of ω that satisfies this is called the resonant frequency.

$$\omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/s}$$

Series Resonance

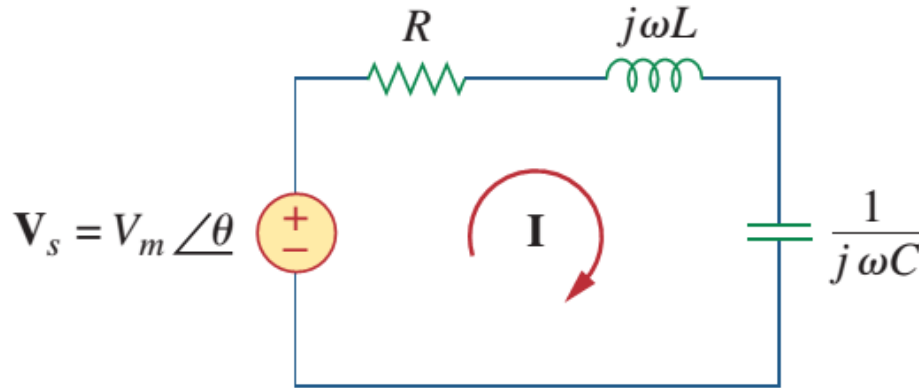- At resonance:
 - The impedance is purely resistive
 - The voltage V_s and the current I are in phase
 - The magnitude of the transfer function is **minimum**
 - The inductor and capacitor voltages can be much more than the source



$$|V_L| = \frac{V_m}{R} \omega_0 L$$



$$|V_C| = \frac{V_m}{R} \frac{1}{\omega_0 C}$$

$$H(\omega) = \frac{V}{I} = \mathbf{Z} = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

Half-Power Frequencies

- the current magnitude:

$$I = |\mathbf{I}| = \frac{V_m}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}}$$

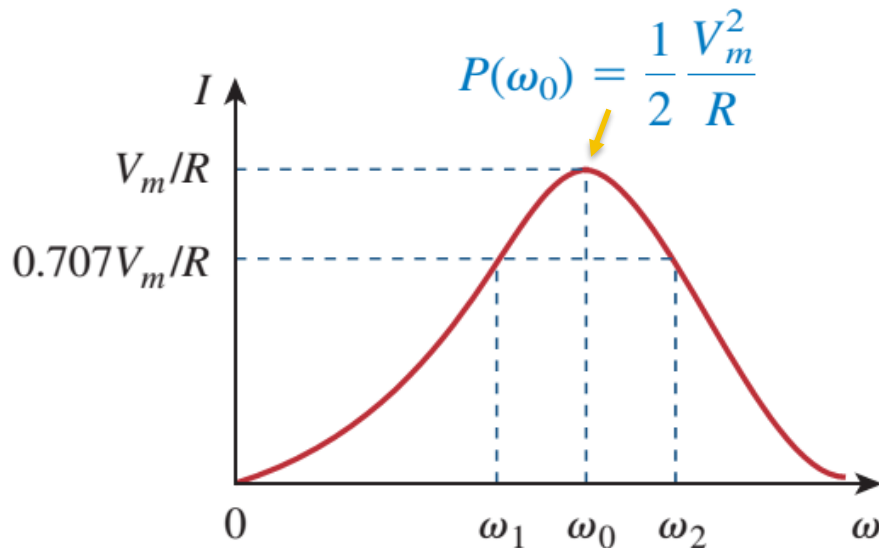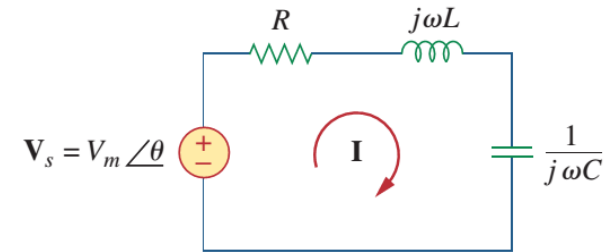

$$\omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/s}$$


$$P(\omega_1) = P(\omega_2) = \frac{1}{2} P(\omega_0)$$

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_0 = \sqrt{\omega_1 \omega_2}$$

Bandwidth

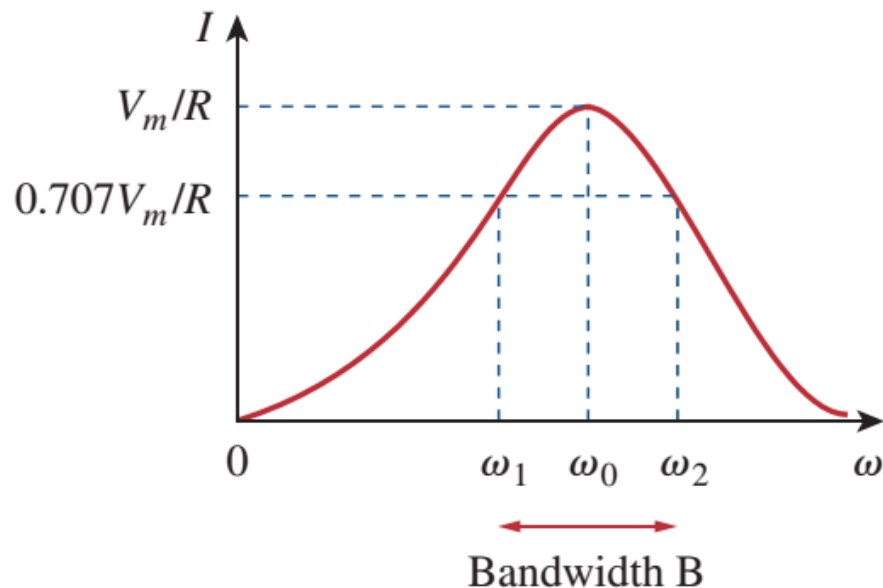

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$
$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$


$$B = \omega_2 - \omega_1 = \frac{R}{L}$$

- Bandwidth: the difference between the two half-power frequencies



Quality Factor Q

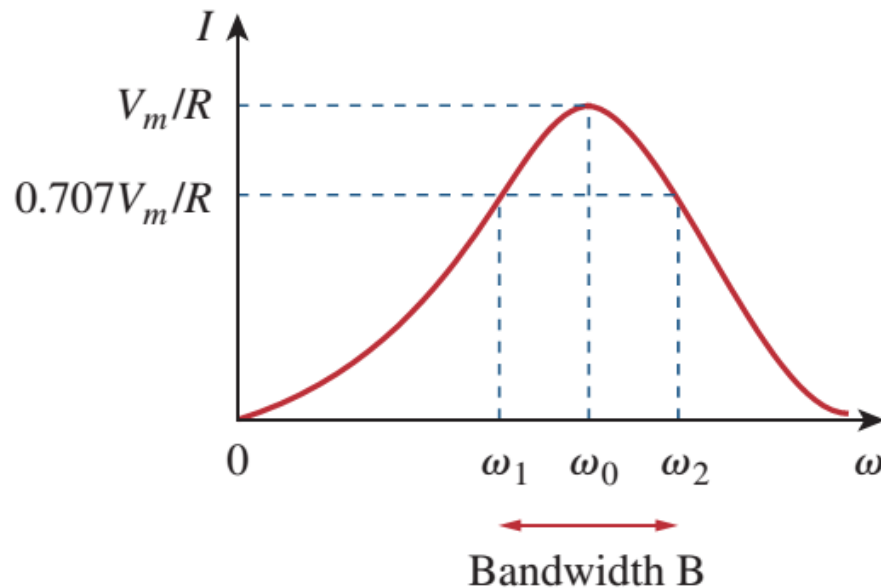- Quality factor Q : measure the “sharpness” of the resonance.




The smaller the B , the higher the Q .

$$Q = \frac{\omega_0}{B}$$


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$B = \omega_2 - \omega_1 = \frac{R}{L}$$
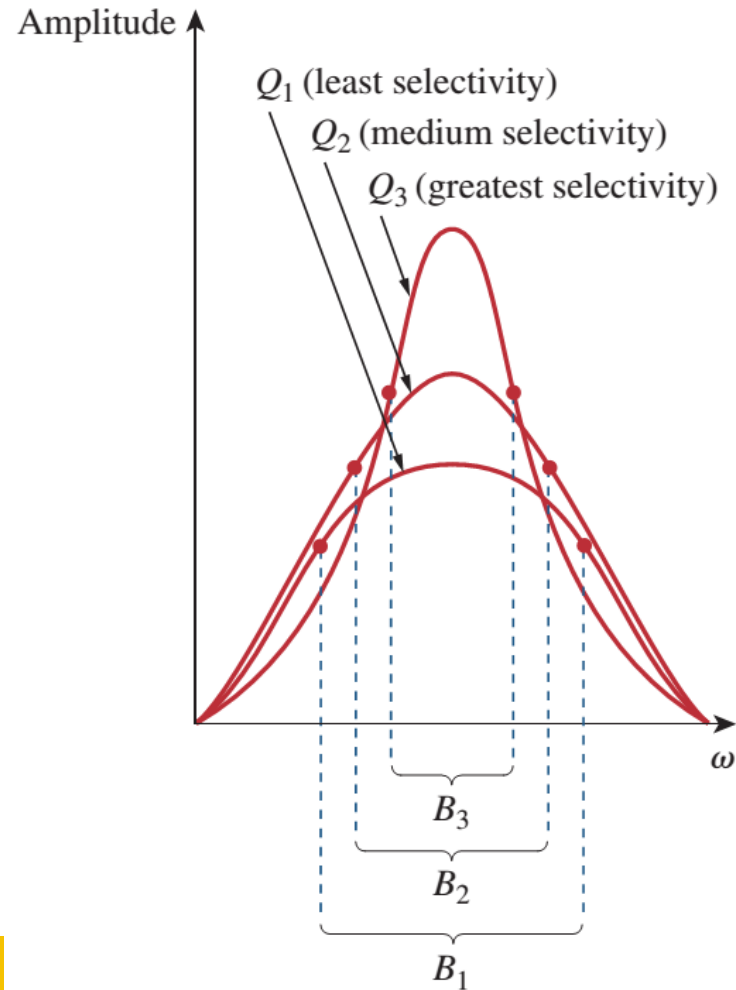
$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R}$$



Quality Factor Q

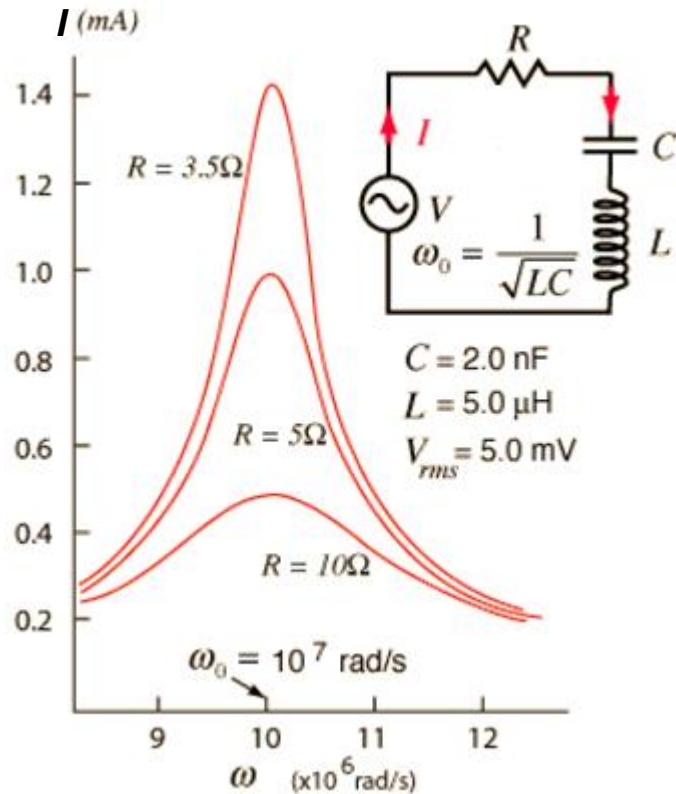


$$Q = \frac{\omega_0}{B}$$

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R}$$

[Source: Georgia State U]

Approximation of Half-Power Frequencies

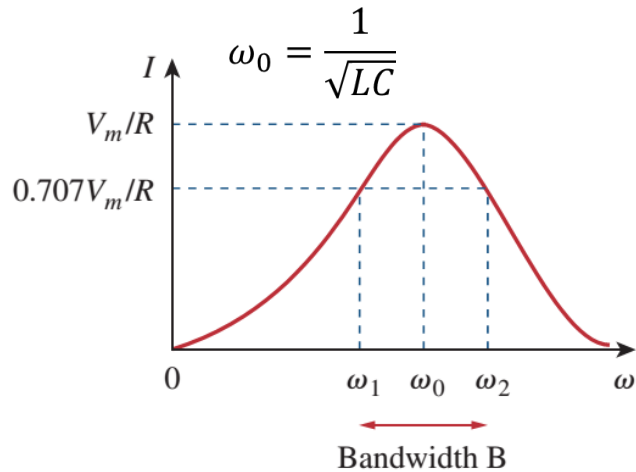

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\frac{R}{L} = B \quad B = \frac{\omega_0}{Q}$$

$$\omega_1 = -\frac{\omega_0}{2Q} + \omega_0 \sqrt{1 + \frac{1}{4Q^2}}$$

$$\omega_2 = \frac{\omega_0}{2Q} + \omega_0 \sqrt{1 + \frac{1}{4Q^2}}$$

- For high-Q ($Q \geq 10$) circuits, half-power frequencies can be approximated as

$$\omega_1 \simeq \omega_0 - \frac{B}{2}, \quad \omega_2 \simeq \omega_0 + \frac{B}{2}$$

Example


In the circuit, $R = 2\Omega$, $L = 1\text{mH}$
and $C = 0.4\mu\text{F}$

- Find resonant frequency ω_0 .
- Calculate Q and bandwidth B .
- Find half-power frequencies.
- Determine the amplitude of the current at ω_0 , ω_1 and ω_2 .

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-3} \times 0.4 \times 10^{-6}}} = 50 \text{ krad/s}$$

$$B = \omega_2 - \omega_1 = 2 \text{ krad/s}$$
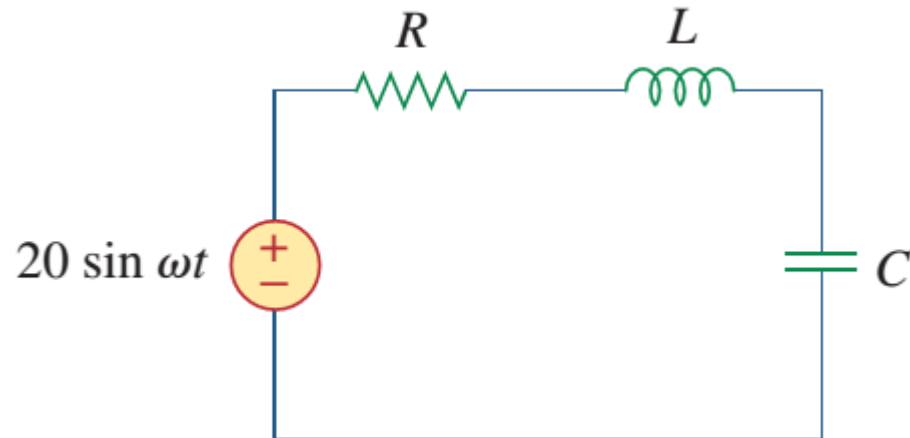
$$Q = \frac{\omega_0}{B} = \frac{50}{2} = 25$$



At $\omega = \omega_0$,


$$I = \frac{V_m}{R} = \frac{20}{2} = 10 \text{ A}$$

At $\omega = \omega_1, \omega_2$,


$$I = \frac{V_m}{\sqrt{2}R} = \frac{10}{\sqrt{2}} = 7.071 \text{ A}$$



Parallel resonance

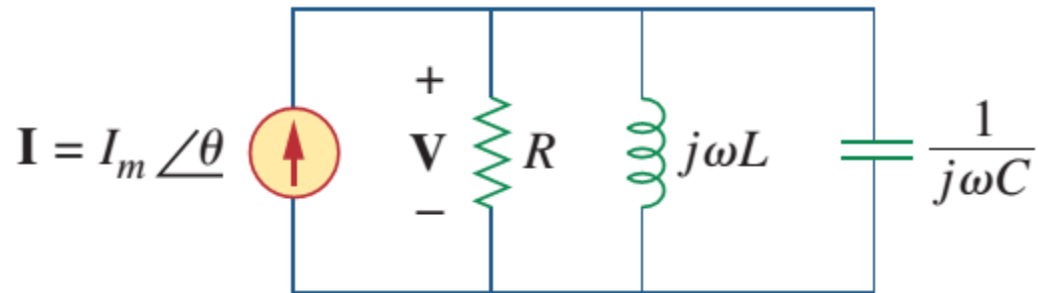


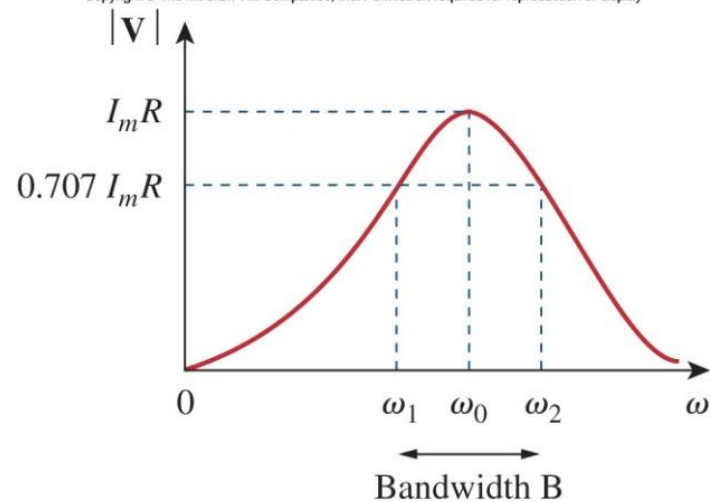Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





RLC Circuit

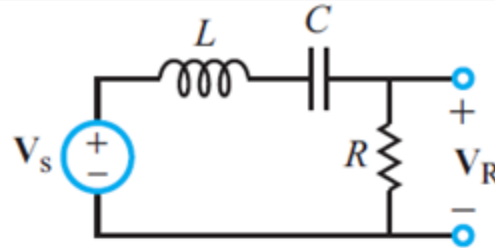

Transfer Function

$$H = \frac{V_R}{V_s}$$

Resonant Frequency, ω_0

$$\frac{1}{\sqrt{LC}}$$

Bandwidth, B

$$\frac{R}{L}$$

Quality Factor, Q


$$\frac{\omega_0}{B} = \frac{\omega_0 L}{R}$$

Lower Half-Power Frequency, ω_1

$$\left[-\frac{1}{2Q} + \sqrt{1 + \frac{1}{4Q^2}} \right] \omega_0$$

Upper Half-Power Frequency, ω_2
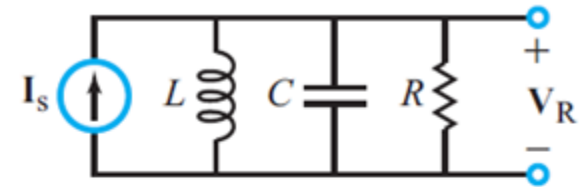
$$\left[\frac{1}{2Q} + \sqrt{1 + \frac{1}{4Q^2}} \right] \omega_0$$



$$H = \frac{V_R}{I_s}$$

$$\frac{1}{\sqrt{LC}}$$

$$\frac{1}{RC}$$

$$\frac{\omega_0}{B} = \frac{R}{\omega_0 L}$$

$$\left[-\frac{1}{2Q} + \sqrt{1 + \frac{1}{4Q^2}} \right] \omega_0$$

$$\left[\frac{1}{2Q} + \sqrt{1 + \frac{1}{4Q^2}} \right] \omega_0$$

Notes: (1) The expression for Q of the series RLC circuit is the inverse of that for Q of the parallel circuit. (2) For $Q \geq 10$, $\omega_1 \simeq \omega_0 - \frac{B}{2}$, and $\omega_2 \simeq \omega_0 + \frac{B}{2}$.

[Source: Berkeley]