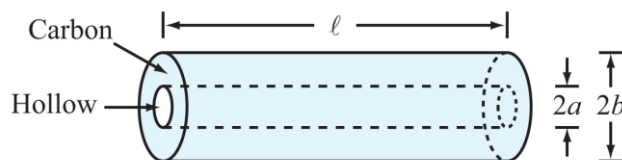


**Problem 1 – Short Answers (20 points)**

- 1) A resistor of length  $\ell$  consists of a hollow cylinder of radius  $a$  surrounded by a layer of carbon that extends from  $r = a$  to  $r = b$ . Develop an expression for the resistance  $R$ .



Carbon resistor of Problem 1.1

**Solution:**

(a)  $R = \frac{\ell}{\sigma A}$ .

The area through which current can flow is the cross section consisting of carbon.


Hence,

$$A = \pi b^2 - \pi a^2.$$


Thus,

$$R = \frac{\ell}{\sigma \pi (b^2 - a^2)}.$$

- 2) Determine the equivalent resistance between terminals (a,b):

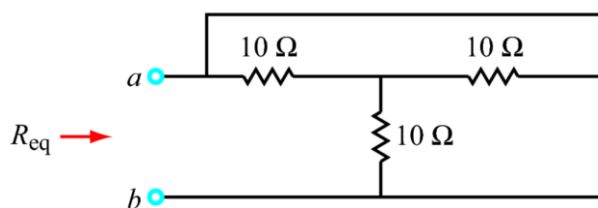
**0.**

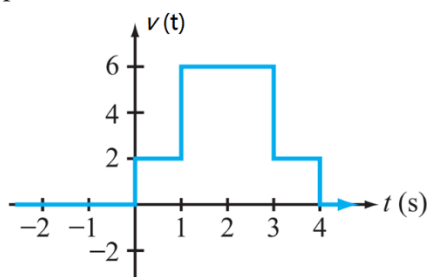- 3) Provide expressions in terms of step functions for the waveform



$$v_5(t) = 2u(t) + 4u(t - 1) - 4u(t - 3) - 2u(t - 4)$$

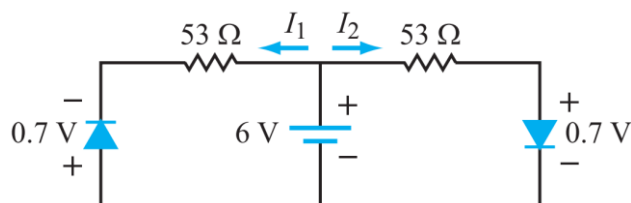- 4) Determine  $I_1$  and  $I_2$  in the circuit of Fig. P2.67. Assume  $V_F = 0.7$  V for both diodes.



**Solution:** The diode in the left-hand loop is reverse biased, so

$$I_1 = 0.$$

In the right-hand loop, the diode is forward biased. Hence,

$$I_2 = \frac{6 - 0.7}{53} = 0.1 \text{ A}.$$

- 5) The excitation function for all four of the circuits shown in Figure 3. is

$$v_s(t) = 0 \quad t < 0$$

$$v_s(t) = 10V \quad t \geq 0$$

For each of the circuits, select the time function on the right that corresponds in magnitude and shape to the output,  $v_o(t)$ . Assume that all capacitors and inductors have zero initial states, (the appropriate state variable is zero for  $t$  less than zero). If no matching response exists, say so and explain briefly. All responses are made up of “**straight lines**” and “**exponentials**.” You may choose a time function more than once.

**Solution:**

$$(A) \rightarrow v_o(t) = 10V(1 - e^{-t/\tau}) ; \tau = R \cdot C$$

$$(B) \rightarrow v_o(t) = 10V \left( \frac{R}{R+R} \right) (1 - e^{-t/\tau}) ; \tau = R \cdot C$$

$$(C) \rightarrow v_o(t): \text{finally} = 10V ; \text{initially} = 0$$

$$v_o(t) = 10(1 - e^{-t/\tau}) ; \tau = L/R$$

$$(D) \rightarrow \frac{V_s}{R} + C \frac{dV_o}{dt} = 0 \Rightarrow V_o = \frac{-10}{RC} \cdot t, \text{ within the linear region of the op. amp.}$$

**3, 7, 3, 4.**


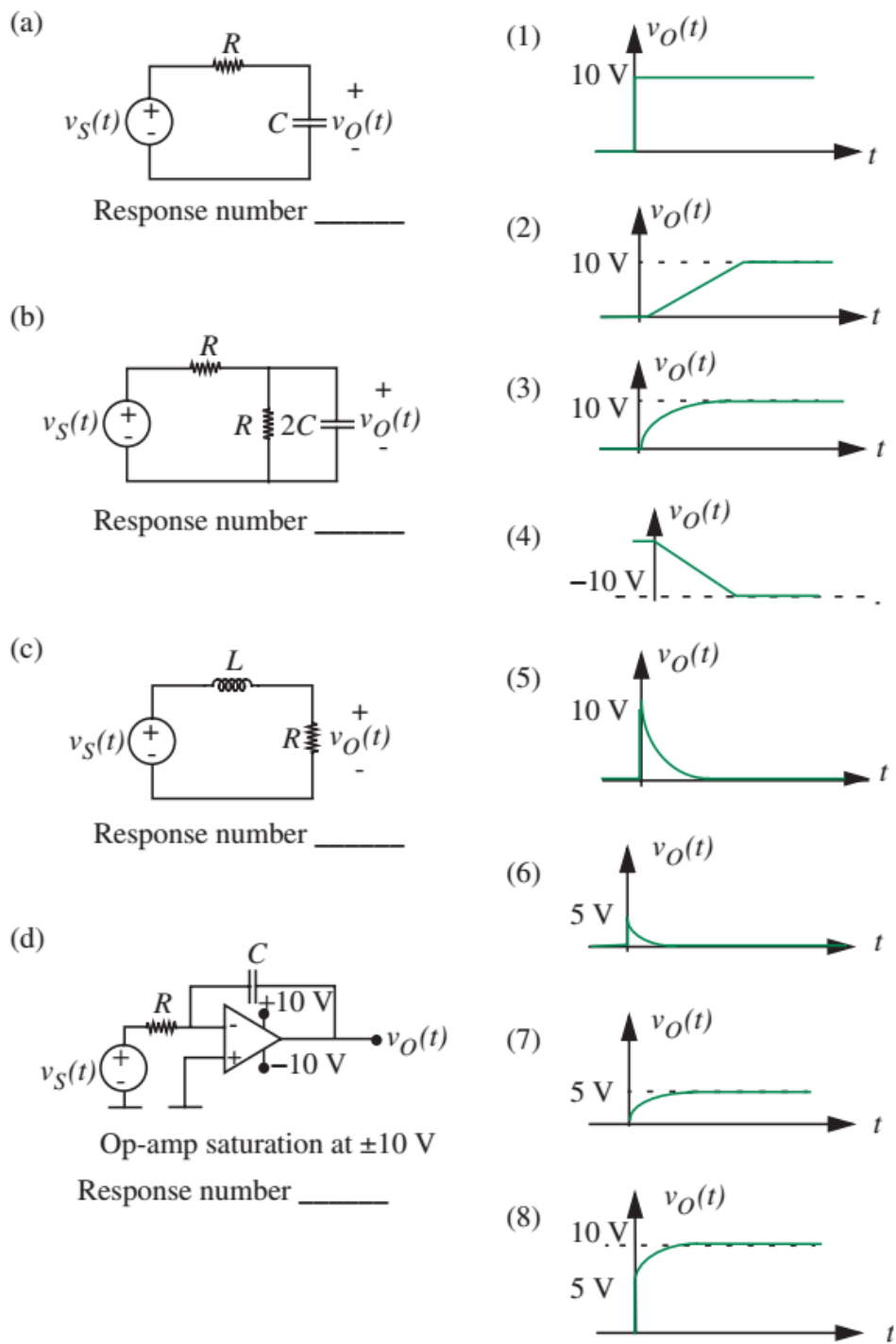


Figure 3.

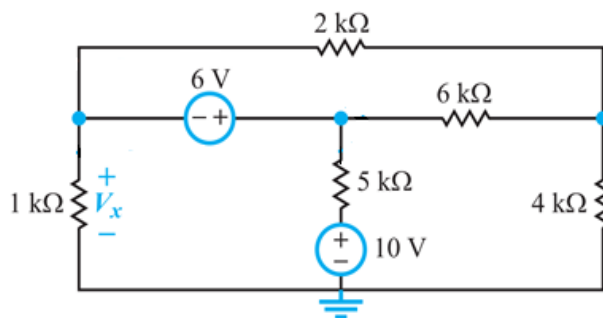**Problem 2 (12 points)** – Determine  $V_x$  in the circuit



**Solution:** The combination of nodes  $V_1$  and  $V_2$  constitutes a supernode. Hence, for the supernode

$$\frac{V_1}{10^3} + \frac{V_1 - V_3}{2 \times 10^3} + \frac{V_2 - 10}{5 \times 10^3} + \frac{V_2 - V_3}{6 \times 10^3} = 0 \quad (1)$$

For node  $V_3$ ,

$$\frac{V_3 - V_1}{2 \times 10^3} + \frac{V_3 - V_2}{6 \times 10^3} + \frac{V_3}{4 \times 10^3} = 0. \quad (2)$$

The auxiliary equation is

$$V_2 - V_1 = 6 \text{ V}. \quad (3)$$


The three equations can be solved to yield

$$V_1 = 0.38 \text{ V}, \quad V_2 = 6.38 \text{ V}, \quad V_3 = 1.37 \text{ V}.$$


Hence,

$$V_x = V_1 = 0.38 \text{ V}.$$

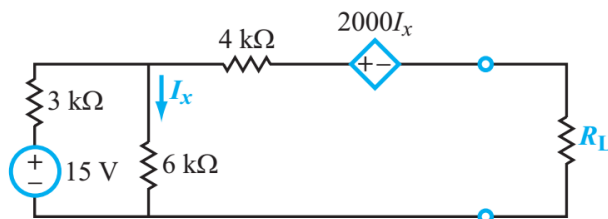**Problem 3 (18 points)** Determine the maximum power that can be extracted by the load resistor from the circuit shown below.



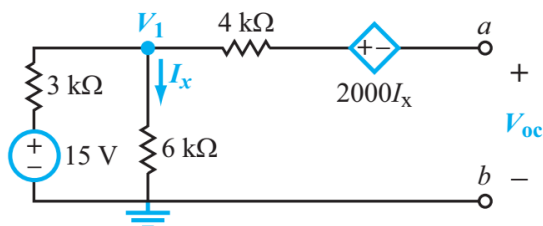**Solution:** To find the Thévenin equivalent circuit, we start by determining  $V_{Th} = V_{oc}$ .



Voltage division:

$$V_1 = \frac{15}{(3+6)k} \times 6k = 10 \text{ V}$$


$$I_x = \frac{V_1}{6k} = \frac{10}{6} \text{ mA}.$$

The dependent voltage source is:

$$2000I_x = 2 \times \frac{10}{6} \times 10^3 \times 10^{-3} = \frac{20}{6} \text{ V}.$$

With  $(a, b)$  an open circuit, no current flows through the 4-kΩ resistor. Hence, there is no voltage drop across it.
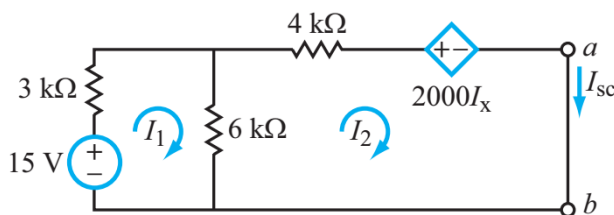
$$V_{Th} = V_{oc} = V_1 - 2000I_x = 10 - \frac{20}{6} = \frac{40}{6} = 6.67 \text{ V}.$$



Next, we find  $I_{sc}$ :

$$-15 + 3kI_1 + 6k(I_1 - I_2) = 0$$

$$6k(I_2 - I_1) + 4kI_2 + 2000I_x = 0$$

Also,

$$I_x = I_1 - I_2$$


Solution yields:

$$I_1 = 2.5 \text{ mA}, \quad I_2 = 1.25 \text{ mA}.$$

$$I_{sc} = I_2 = 1.25 \text{ mA}.$$

$$R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{6.67}{1.25 \times 10^{-3}} = 5.33 \text{ k}\Omega.$$

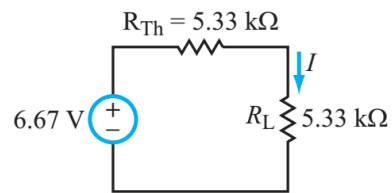Hence,  $R_L = 5.33 \text{ k}\Omega$  extracts maximum power.




$$I = \frac{6.67}{2 \times 5.33} = 0.625 \text{ mA}$$


$$P_{\max} = I^2 R_L = (0.625 \times 10^{-3})^2 \times 5.33 \times 10^3 = 2.09 \quad (\text{mW}).$$

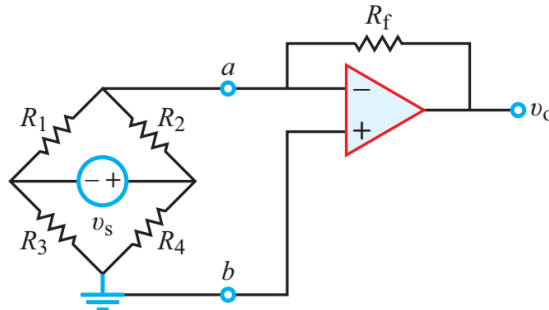**Problem 4 (18 points)** – In the circuit below, a bridge circuit is connected at the input side of an inverting op-amp circuit.

- Obtain the Thevenin equivalent at terminals (a,b) for the bridge circuit.
- Use the result in (a) to obtain an expression for  $G = v_o/v_s$ .



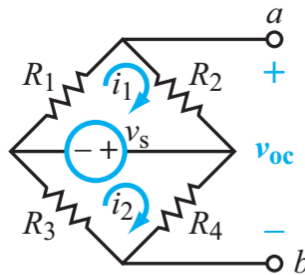**Solution: (a)** The Thévenin equivalent circuit at (a,b):



$$v_s + i_1(R_1 + R_2) = 0$$

or

$$i_1 = \frac{-v_s}{R_1 + R_2}.$$

Also,

$$-v_s + i_2(R_3 + R_4) = 0$$


and

$$i_2 = \frac{v_s}{R_3 + R_4}.$$

$$\begin{aligned} v_{Th} = v_{oc} &= i_1 R_2 + i_2 R_4 \\ &= \frac{-v_s R_2}{R_1 + R_2} + \frac{v_s R_4}{R_3 + R_4} = \frac{[R_4(R_1 + R_2) - R_2(R_3 + R_4)]v_s}{(R_1 + R_2)(R_3 + R_4)}. \end{aligned} \quad (1)$$

Suppressing  $v_s$  (by replacing it with a short circuit) leads to
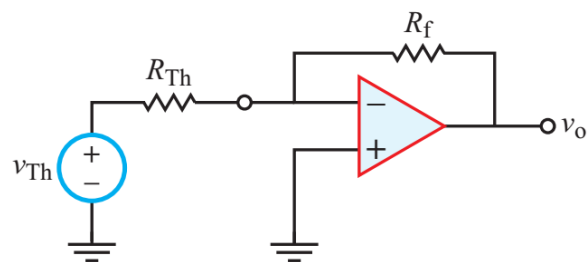
$$\begin{aligned} R_{Th} &= (R_1 \parallel R_2) + (R_3 \parallel R_4) \\ &= \frac{R_1 R_2}{R_1 + R_2} + \frac{R_3 R_4}{R_3 + R_4} = \frac{R_1 R_2 (R_3 + R_4) + R_3 R_4 (R_1 + R_2)}{(R_1 + R_2)(R_3 + R_4)}. \end{aligned}$$




$$v_o = -\frac{R_f}{R_{Th}} v_{Th} \quad (\text{inverting amplifier}) \quad (3)$$

Inserting Eqs. (1) and (2) into (3) leads to

$$G = \frac{v_o}{v_s} = \frac{-R_f[R_4(R_1 + R_2) - R_2(R_3 + R_4)]}{R_1R_2(R_3 + R_4) + R_3R_4(R_1 + R_2)}$$



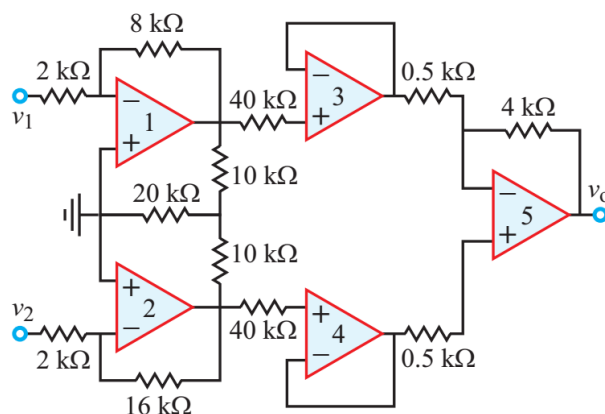**Problem 5 (12 points)** Relate  $v_o$  in the circuit to  $v_1$  and  $v_2$ .



**Solution:**

Op amp 1:  $v_{o1} = \left(-\frac{8}{2}\right) v_1 = -4v_1$

Op amp 2:  $v_{o2} = \left(-\frac{16}{2}\right) v_2 = -8v_2$

Op amp 3:  $v_{o3} = v_{o1}$  (voltage follower)

Op amp 4:  $v_{o4} = v_{o2}$  (voltage follower)


Op amp 5:  $v_o = -\left(\frac{4}{0.5}\right) v_{o3} + \left(\frac{4+0.5}{0.5}\right) v_{o4}$  (difference amplifier)  
 $= 32v_1 - 72v_2.$

**Problem 6 (20 points) – First-order circuit analysis**

You must show your work to get full credit.

The op-amp circuit shown in Fig. 7 is subjected to an input pulse of amplitude  $V_s = 2.4V$  and duration  $T_0 = 0.3s$ . Determine and plot the output voltage  $V_{out}(t)$  for  $t \geq 0$ , assuming that the capacitor was uncharged before  $t = 0$ .

Hint:  $e^{-1.2} = 0.3$ .

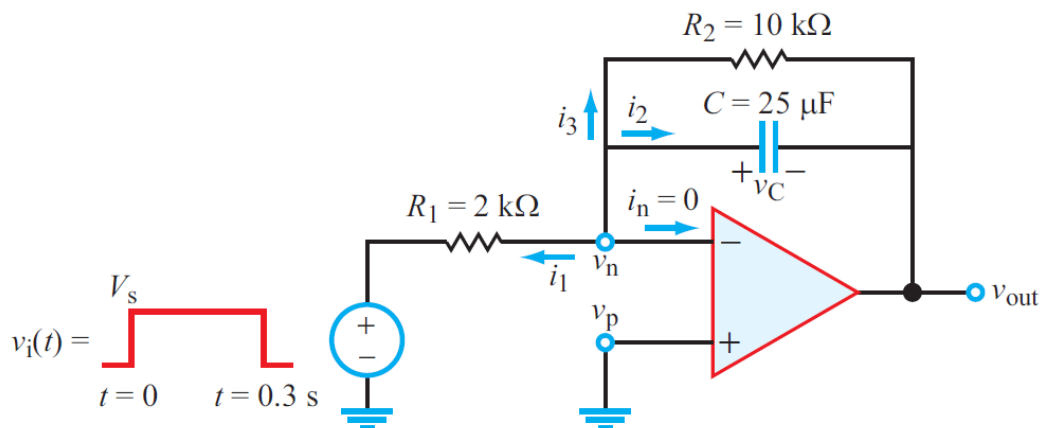

**Your answer:**

$$C \frac{dv_{out}}{dt} + \frac{v_{out}}{R_2} = -\frac{v_i(t)}{R_1}, \quad \tau = R_2 C = 0.25s.$$

For  $0 \leq t \leq 0.3s$ ,  $v_{out} = -12(1 - e^{-4t})V$ ,  $v_{out}(0.3) = -8.4V$ .

For  $t > 0.3s$ ,  $v_{out} = -8.4(1 - e^{-4(t-0.3)})V$ .

