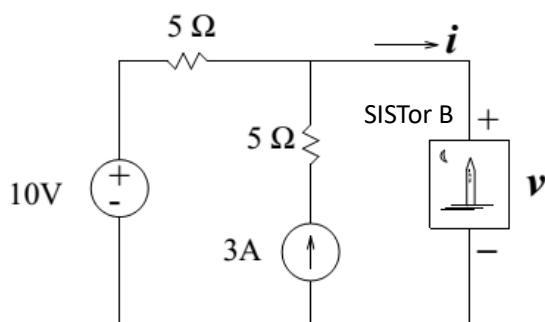


Problem 1 (8 points)

You must show your detailed work to get full credit.

The resistive network shown in Fig.1(a) is connected to an element SISTor B. The SISTor is a nonlinear device with $i - v$ characteristic shown in Fig.1(b). Determine

- 1) the current i drawn by the SISTor and
- 2) the voltage v across the SISTor.



(a)





(b) $i - v$ curve for SISTor B.

Fig. 1 for Problem 1.


Your answer:



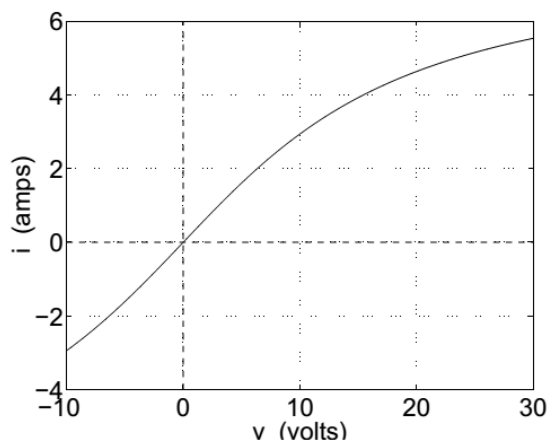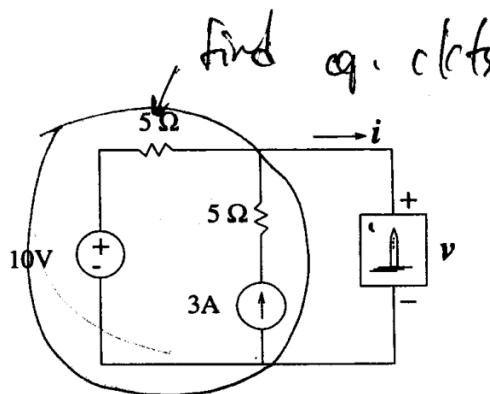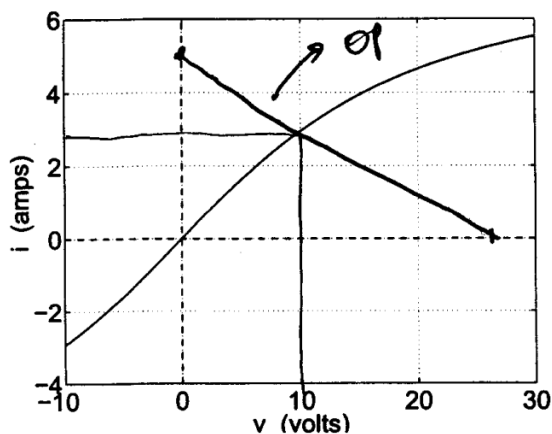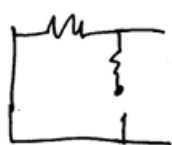find $R_{th} \Rightarrow$ short all indep sources



$$R_{eq} = R_{th} = 5 \Omega$$

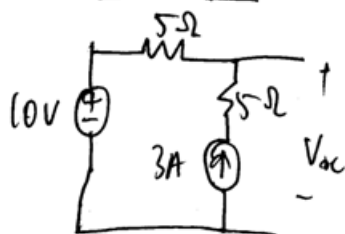

$$3A = \frac{V_{th} - 10}{5} \Rightarrow V_{th} = 25V$$



$$-V_{th} + IR_{th} + V = 0$$

$$V_{th} = IR_{th} + V$$

$$\textcircled{1} I = 0 \Rightarrow V = V_{th} = 25V$$

$$i = 3A$$

$$v = 10V$$

$$\textcircled{2} V = 0 \Rightarrow I = 5A$$

Problem 2 (8 points) — Diodes

You must show your detailed work to get full credit.

In the circuit shown in Fig.2, assume all the diodes are ideal with threshold voltage equals to 700mV. Find V_a and then explain why.

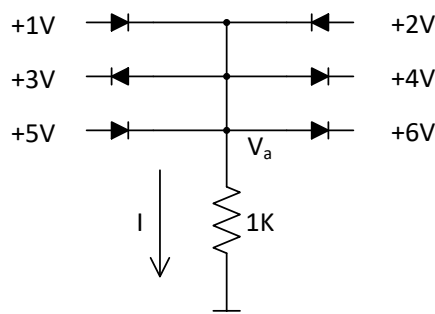


Fig. 2 for Problem 2.

Your answer:

If D_6 is on, $V_a = 6.7V$, so D_6 is off.
 If D_1 is on, $V_a = 0.7V$, ~~so~~ then D_5 is on,
 the $V_a = 4.3V$, so D_1 will be off, so D_1 is off.
 D_3 is the same as D_1 , so D_3 is off.
 If D_4 is on, $V_a = 4.7V$, but V_T is $0.7V$,
 so $V_{a_{max}}$ is $4.3V < 4.7V$, so D_4 is off.
 If D_2 is on, $V_a = 2.7V$, $2.7V < 4.3V$, so D_2 is on.
 In a short, D_2, D_5 is on, others are off.
 so $V_a = 4.3V$ ($2.7V \sim 4.3V$ are all right)


Problem 3 (9 points)

You must show your detailed work to get full credit.


Fig. 3 shows two Switched Capacitor (SC) Converter circuits which convert input DC voltage V_{BAT} to output voltage V_L

- The conversion ratio is defined as $n = \frac{V_{BAT}}{V_L}$.
- All the switches in these circuits are controlled by a periodic square wave with 50% duty cycle: During high voltage phase, the ϕ_1 switches are turned on, meanwhile the ϕ_2 switches are turned off; during low voltage phase, the ϕ_2 switches are turned on, but the ϕ_1 switches are turned off.
- Assuming that the capacitors can be fully charged in a half cycle.

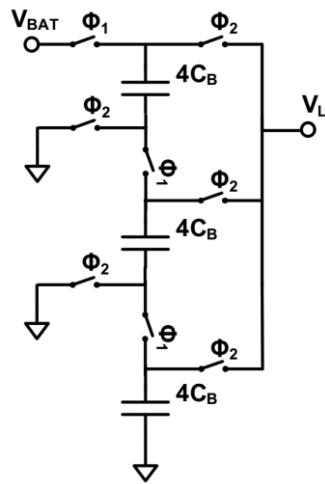Find the conversion ratios n_1 and n_2 for the two SC converters shown in Fig. 3.


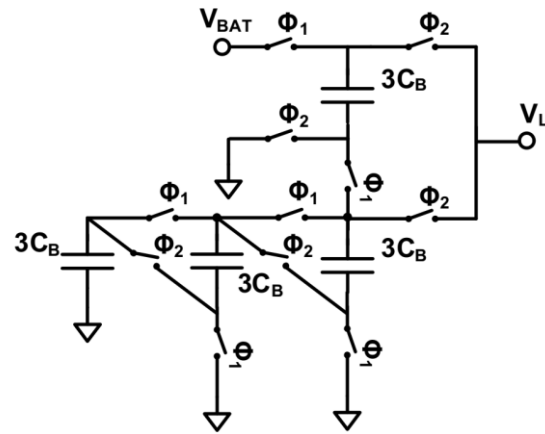
$$(a) \ n_1 = \frac{V_{BAT}}{V_L} = 3/1$$



$$(b) \ n_2 = \frac{V_{BAT}}{V_L} = 4/3$$

Fig. 3 for Problem 3.

Your answer:

$$n_1 = \frac{V_{BAT}}{V_L} = 3/1$$

$$n_2 = \frac{V_{BAT}}{V_L} = 4/3$$

Problem 4 (15 points) — First-Order Circuit Analysis

You must show your detailed work to get full credit.

The circuit shown in Fig. 4 contains two switches, both of which had been open for a long time before $t = 0$. Switch 1 closes at $t = 0$, and Switch 2 closes at $t = 5$ s.

Determine $v_C(t)$ for $t \geq 0$, given that $V_0 = 24$ V, $R_1 = R_2 = 16$ k Ω , and $C = 250$ μ F. Assume that $v_C(0) = 0$.

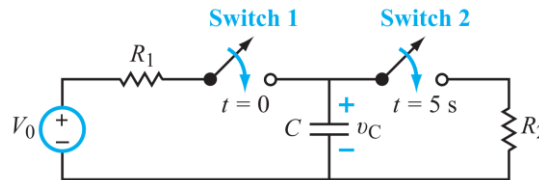
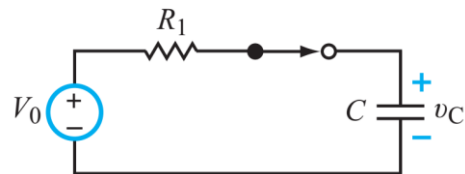


Fig. 4 for Problem 4.

Time Segment 1: $0 \leq t \leq 5$ s

$$\begin{aligned}\tau_1 &= R_1 C = 16 \times 10^3 \times 250 \times 10^{-6} = 4 \text{ s.} \\ v_{C_1}(t) &= v_{C_1}(\infty) + (v_{C_1}(0) - v_{C_1}(\infty))e^{-t/\tau_1} \\ &= V_0 + (0 - V_0)e^{-0.25t} \\ &= 24(1 - e^{-0.25t}), \quad \text{for } 0 \leq t \leq 5 \text{ s.}\end{aligned}$$

**Time Segment 2: $t \geq 5$ s**



Through source transformation, it is easy to see that R_1 and R_2 should be combined in parallel. Hence:

$$\begin{aligned}\tau_2 &= \left(\frac{R_1 R_2}{R_1 + R_2} \right) C = 8 \times 10^3 \times 250 \times 10^{-6} = 2 \text{ s.} \\ v_{C_2}(t) &= v_{C_2}(\infty) + [v_{C_2}(5 \text{ s}) - v_{C_2}(\infty)]e^{-(t-5)/\tau_2}\end{aligned}$$

$$v_{C_2}(\infty) = \frac{V_0 R_2}{R_1 + R_2} = \frac{24 \times 16}{16 + 16} = 12 \text{ V.}$$

$$v_{C_2}(5 \text{ s}) = v_{C_1}(5 \text{ s}) = 24(1 - e^{-0.25 \times 5}) = 17.12 \text{ V}$$
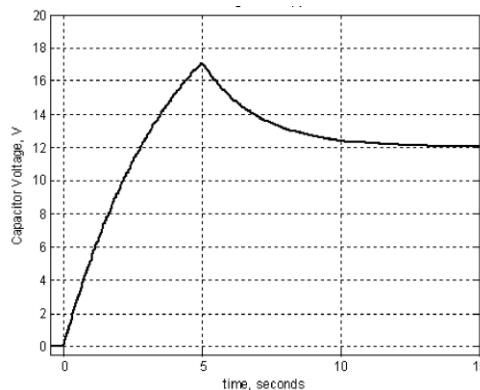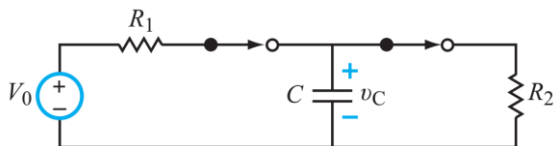
$$\begin{aligned}v_{C_2}(t) &= 12 + [17.12 - 12]e^{-0.5(t-5)} \\ &= 12 + 5.12e^{-0.5(t-5)}, \quad \text{for } t \geq 5 \text{ s.}\end{aligned}$$



Problem 5 (18 points) – General Second-Order Circuit Analysis

You must show your detailed work to get full credit.

Determine $i_L(t)$ in the op-amp circuit of Fig. 4 for $t \geq 0$, where $V_s = 1\text{mV}$, $R_1 = 10\text{k}\Omega$, $R_2 = 1\text{M}\Omega$, $R_3 = 100\Omega$, $L = 5\text{H}$ and $C = 1\mu\text{F}$. Assume the op-amp is ideal.


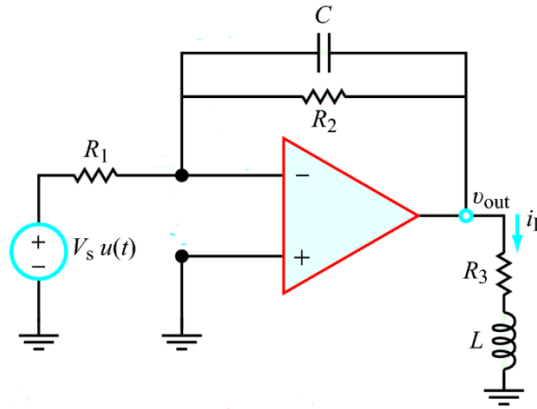


Fig. 5 for Problem 5.

Solution:

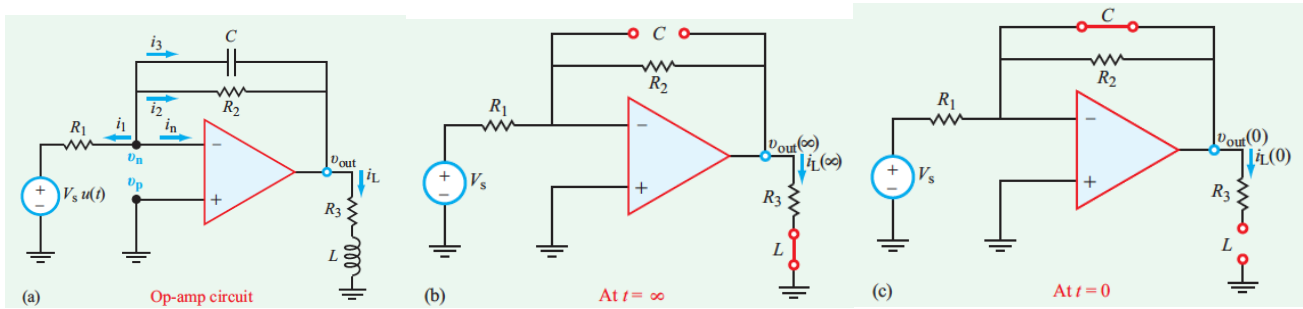

Solution: KCL at node v_n gives

$$i_1 + i_n + i_2 + i_3 = 0,$$

or equivalently,

$$\frac{v_n - V_s}{R_1} + i_n + \frac{v_n - v_{\text{out}}}{R_2} + C \frac{d}{dt}(v_n - v_{\text{out}}) = 0.$$

Since $v_n = v_p = 0$, $i_n = 0$, and

$$v_{\text{out}} = R_3 i_L + L \frac{di_L}{dt},$$

$$\frac{R_3}{R_2} i_L + \left(\frac{L}{R_2} + R_3 C \right) \frac{di_L}{dt} + LC \frac{d^2 i_L}{dt^2} = -\frac{V_s}{R_1}.$$

Rearranging, we have

$$i_L'' + ai_L' + bi_L = c,$$

where

$$a = \frac{L + R_2 R_3 C}{R_2 LC} = 21,$$

$$b = \frac{R_3}{R_2 LC} = 20,$$

and

$$c = \frac{-V_s}{R_1 LC} = -0.02.$$

The damping behavior of i_L is determined by how the magnitude of α compares with that of ω_0 :

$$\alpha = \frac{a}{2} = 10.5 \text{ Np/s},$$

$$\omega_0 = \sqrt{b} = \sqrt{20} = 4.47 \text{ rad/s}.$$

Since $\alpha > \omega_0$, i_L will exhibit an overdamped response given by

$$i_L(t) = [A_1 e^{s_1 t} + A_2 e^{s_2 t} + i_L(\infty)] u(t),$$

with

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -1.0,$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -20.$$

$$i_L(0) = i_L(0^-) = 0,$$

which means that the inductor behaves like an open circuit at $t = 0$, as depicted in Fig. 6-18(c). Also, since the voltage v_C across the capacitor was zero before $t = 0$, it has to remain at zero at $t = 0$, which is why it has been replaced with a short circuit in Fig. 6-18(c). Consequently, $v_{\text{out}}(0) = 0$, $v_L(0) = 0$, and

$$i_L'(0) = \frac{1}{L} v_L(0) = 0.$$

From Table 6-2, with $x = i_L$,

$$A_1 = \frac{i_L'(0) - s_2[i_L(0) - i_L(\infty)]}{s_1 - s_2}$$

$$= \frac{0 + 20(0 + 1)}{-1 + 20} \times 10^{-3} = 1.05 \text{ mA} \quad (6.106)$$

and

$$A_2 = -\left[\frac{i_L'(0) - s_1[i_L(0) - i_L(\infty)]}{s_1 - s_2} \right]$$

$$= -\left[\frac{0 + 1(0 + 1)}{-1 + 20} \right] \times 10^{-3} = -0.053 \text{ mA}. \quad (6.107)$$

The final expression for $i_L(t)$ is then given by

$$i_L(t) = [1.05e^{-t} - 0.053e^{-20t} - 1] \text{ mA}, \quad \text{for } t \geq 0.$$

At $t = \infty$, the circuit assumes the equivalent configuration shown in Fig. 6-18(b), which is an inverting amplifier with an output voltage

$$v_{\text{out}}(\infty) = -\frac{R_2}{R_1} V_s.$$

Hence,

$$i_L(\infty) = \frac{v_{\text{out}}(\infty)}{R_3} = -\frac{R_2 V_s}{R_1 R_3} = -1 \text{ mA}.$$

The expression for $i_L(t)$ becomes

$$i_L(t) = [A_1 e^{-t} + A_2 e^{-20t} - 10^{-3}]. \quad (6.105)$$

Problem 6 (12 points) – AC Circuit Analysis

You must show your detailed work to get full credit.

The impedance Z_L in the circuit shown in Fig. 7 is adjusted for maximum average power transfer to Z_L . The internal impedance of the sinusoidal voltage source is $4 + j7 \Omega$.

- Determine Z_L .
- What is the maximum average power delivered to Z_L ?


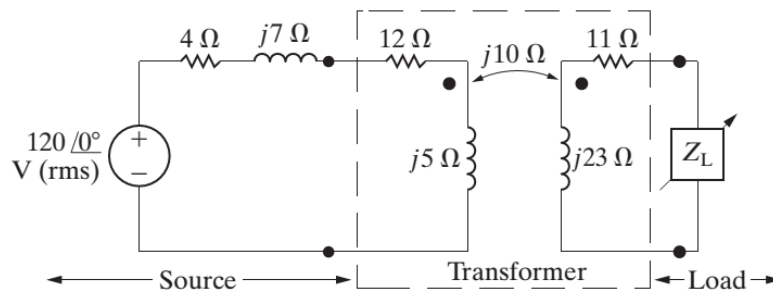


Fig. 6 for Problem 6.

Solution:

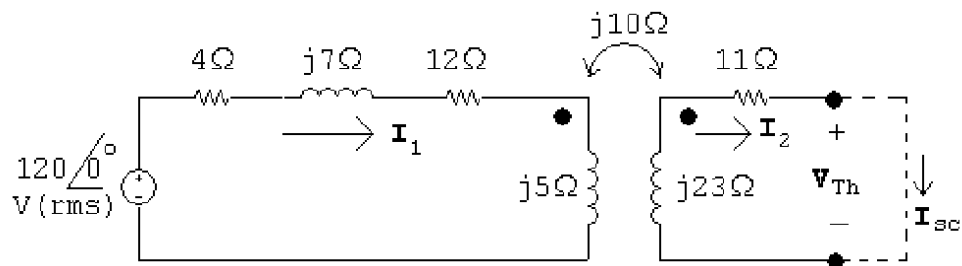First, find the Thevenin Equivalent circuit.



Short circuit:

Open circuit:

$$\mathbf{V}_{Th} = \frac{120}{16 + j12}(j10) = 36 + j48 \text{ V}$$

$$(16 + j12)\mathbf{I}_1 - j10\mathbf{I}_{sc} = 120$$

$$-j10\mathbf{I}_1 + (11 + j23)\mathbf{I}_{sc} = 0$$

Solving,

$$\mathbf{I}_{sc} = 2.4 \text{ A}$$

$$\mathbf{Z}_{Th} = \frac{36 + j48}{2.4} = 15 + j20 \Omega$$

$$\therefore \mathbf{Z}_L = \mathbf{Z}_{Th}^* = 15 - j20 \Omega$$

$$\mathbf{I}_L = \frac{\mathbf{V}_{Th}}{\mathbf{Z}_{Th} + \mathbf{Z}_L} = \frac{36 + j48}{30} = 1.2 + j1.6 \text{ A (rms)}$$

$$P_L = |\mathbf{I}_L|^2(15) = 60 \text{ W}$$

Problem 7 (12 points) – Transfer Response

You must show your detailed work to get full credit.

For the op-amp circuit shown in Fig. 7,

- (a) Obtain an expression for transfer response $H(\omega) = V_o/V_s$ in standard form. Given that $R_1 = R_2 = 100\ \Omega$, $C_1 = 10\ \mu\text{F}$ and $C_2 = 0.4\ \mu\text{F}$.
- (b) What type of filter is it? What is its maximum gain?


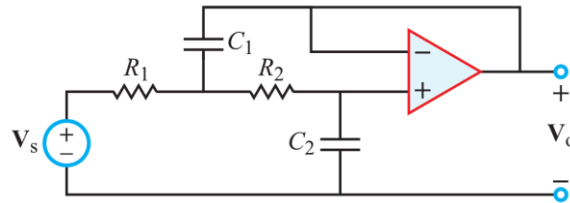


Fig. 7 for Problem 7.

Your answer:

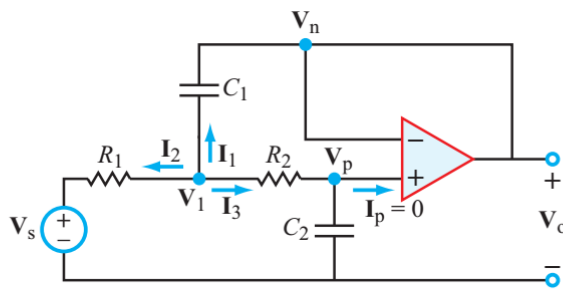

(a) At node V_1 :

$$I_1 + I_2 + I_3 = 0,$$

or equivalently

$$\frac{V_1 - V_o}{1/j\omega C_1} + \frac{V_1 - V_s}{R_1} + \frac{V_1}{R_2 + 1/j\omega C_2} = 0.$$

Also,

$$V_p = V_n = V_o,$$

and by voltage division

$$V_p = \frac{V_1/j\omega C_2}{R_2 + 1/j\omega C_2}.$$

Simultaneous solution leads to:

$$\begin{aligned} H(\omega) = \frac{V_o}{V_s} &= \frac{1}{1 + j\omega(R_1 + R_2)C_2 + (j\omega\sqrt{R_1 R_2 C_1 C_2})^2} \\ &= \frac{1}{1 + j2\xi\omega/\omega_c + (j\omega/\omega_c)^2}, \end{aligned}$$

with

$$\begin{aligned} \omega_c &= \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} = \frac{1}{\sqrt{100 \times 100 \times 10^{-5} \times 0.4 \times 10^{-6}}} = 5000 \text{ rad/s}, \\ \xi &= \frac{(R_1 + R_2)C_2\omega_c}{2} = 100 \times 0.4 \times 10^{-6} \times 5000 = 0.2. \end{aligned}$$

- (b) Low pass filter, with max gain equals one.

Problem 8 (18 points) – Filters

You must show your detailed work to get full credit.

Given that $R = 2\Omega$, $L = 10\text{mH}$, and $C = 1\mu\text{F}$,

- (a) Determine the center frequency ω_a , bandwidth B_a and quality factor Q_a of the single-stage series RLC filter shown in Fig. 8(a).
- (b) Determine the center frequency ω_b , bandwidth B_b and quality factor Q_b of the two-stage series RLC filter shown in Fig. 8(b).

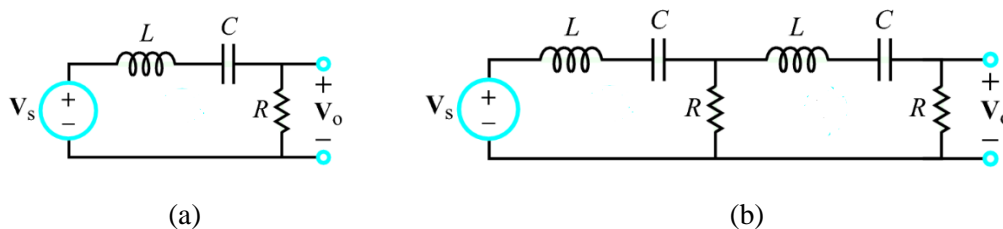


Fig. 8 for Problem 8.


Your answer:

(a) $\omega_a = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-2} \times 10^{-6}}} = 10^4 \text{ rad/s}$

$$Q_a = \frac{\omega_a L}{R} = \frac{10^4 \times 10^{-2}}{2} = 50$$

$$B_a = \frac{\omega_a}{Q_a} = 200$$

(b)

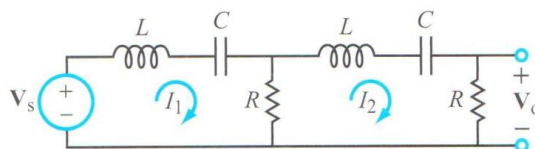

The loop equations for mesh currents I_1 and I_2 are

$$-V_s + I_1 \left(j\omega L + \frac{1}{j\omega C} + R \right) - RI_2 = 0$$

and

$$-RI_1 + I_2 \left(2R + j\omega L + \frac{1}{j\omega C} \right) = 0.$$

Simultaneous solution of the two equations leads to

$$H(\omega) = \frac{V_o}{V_s}$$

$$= \frac{\omega^2 R^2 C^2}{\omega^2 R^2 C^2 - (1 - \omega^2 LC)^2 - j3\omega RC(1 - \omega^2 LC)}$$

$$= \frac{\omega^2 R^2 C^2 [\omega^2 R^2 C^2 - (1 - \omega^2 LC)^2 + j3\omega RC(1 - \omega^2 LC)]}{[\omega^2 R^2 C^2 - (1 - \omega^2 LC)^2]^2 + 9\omega^2 R^2 C^2 (1 - \omega^2 LC)^2}.$$

Resonance occurs when the imaginary part of $\mathbf{H}(\omega)$ is zero, which is satisfied either when $\omega = 0$ (which is a trivial resonance) or when $\omega = 1/\sqrt{LC}$. Hence, the two-stage circuit has the same resonance frequency as a single-stage circuit.

Using the specified values of R , L , and C , we can calculate the magnitude $M(\omega) = |\mathbf{H}(\omega)|$ and plot it as a function of ω . The result is displayed in Fig. 9-18(b). From the spectral plot, we have

$$\omega_{c1} = 9963 \text{ rad/s},$$

$$\omega_{c2} = 10037 \text{ rad/s},$$

$$B_2 = \omega_{c2} - \omega_{c1} = 10037 - 9963 = 74 \text{ rad/s},$$

and

$$Q_2 = \frac{\omega_0}{B_2} = \frac{10^4}{74} = 135,$$

where B_2 is the bandwidth of the two-stage BP-filter response. The two-stage combination increases the quality factor from 50 to 135.

