

EE 111 Homework 6

Due date: May. 13th, 2019


Turn in your homework in class

Rules:

- Work on your own. Discussion is permissible, but similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

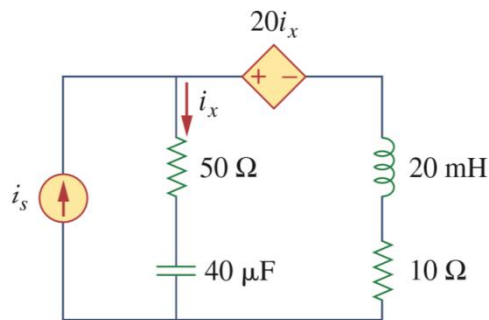1. Instantaneous and Average Power (10')

For the circuit, $i_s = 3\cos 2 \times 10^3 t$ A. Find the average power absorbed by the 50Ω resistor



Solution:

$$20\text{mH} \rightarrow j\omega L = j \times 2 \times 10^3 \times 20 \times 10^{-3} = j40$$

$$40\mu\text{F} \rightarrow \frac{1}{j\omega C} = \frac{1}{j \times 2 \times 10^3 \times 40 \times 10^{-6}} = -j12.5$$

Nodal analysis:

$$-3 + \frac{V_0 - 20I_x}{10 + j40} + \frac{V_0 - 0}{50 - j12.5} = 0$$

$$I_x = \frac{V_0 - 0}{50 - j12.5}$$

$$(0.0203 - j0.0105)V_0 = 3$$

$$V_0 = 3 / (0.0228 \angle -27.4190^\circ) = 131.33 \angle 27.4190^\circ \text{ V}$$

As for the power, all we need is the magnitude of the rms value of I_x .

$$|I_x| = \frac{131.33}{51.54} = 2.548 \text{ A}$$


$$|I_x|_{\text{rms}} = \frac{2.548}{\sqrt{2}} = 1.8017 \text{ A}$$

Then the average power absorbed by the 50Ω resistor can be calculated.

$$P_{\text{avg}} = 1.8017^2 \times 50 = 162.31 \text{ W}$$

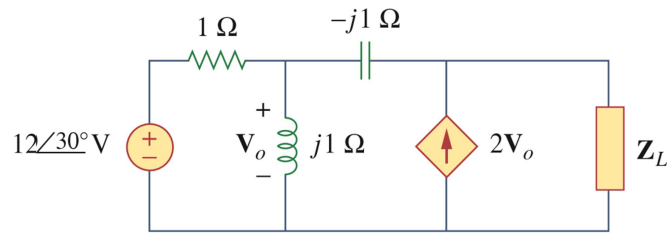
2. Maximum Average Power Transfer (12')

In the circuit, find the value of Z_L that will absorb the maximum power and the value of the maximum power. (note: the voltage is Vm)



Solution:

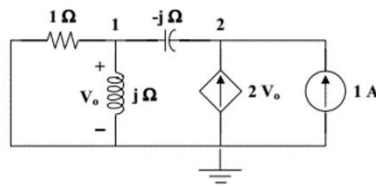Calculate the Z_{th} , insert a 1A current source at the load terminals, and use nodal analysis



$$\frac{V_o}{1} + \frac{V_o}{j} = \frac{V_2 - V_o}{-j} \rightarrow V_o = jV_2 \quad (1)$$


$$1 + 2V_o = \frac{V_2 - V_o}{-j} \rightarrow 1 = jV_2 - (2+j)V_o \quad (2)$$

Substituting (1) into (2), $V_2 = \frac{1}{1-j}$

$$Z_{th} = \frac{V_2}{1} = \frac{1+j}{2} = 0.5 + j0.5$$

$$Z_L = Z_{th}^* = 0.5 - j0.5 \Omega$$

Calculate the V_{th} ,

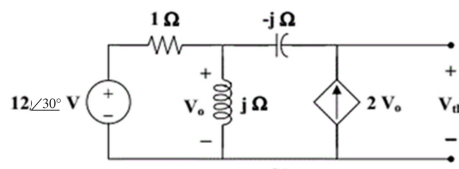

$$12\angle 30^\circ = 6\sqrt{3} + j6 \quad 2V_o + \frac{6\sqrt{3} + j6 - V_o}{1} = \frac{V_o}{j} \rightarrow V_o = \frac{6\sqrt{3} + j6}{1+j}$$


$$-V_o - (-j \times 2V_o) + V_{th} = 0 \rightarrow V_{th} = (1-j2)V_o = -6 \frac{2 + \sqrt{3} + (1-2\sqrt{3})j}{1+j}$$

$$P_{max} = \frac{|V_{th}|^2}{8R_L} = \frac{(6 \times \frac{\sqrt{(2+\sqrt{3})^2 + (1-2\sqrt{3})^2}}{\sqrt{2}})^2}{8 \times 0.5} = 90 W$$


3. Effective or RMS Value (10')

Compute the RMS value of the waveform depicted in the figures.

(1)

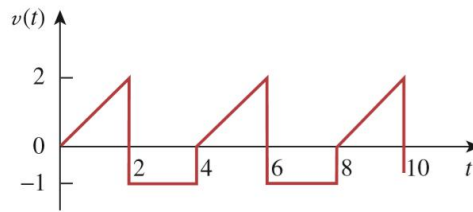

(2)

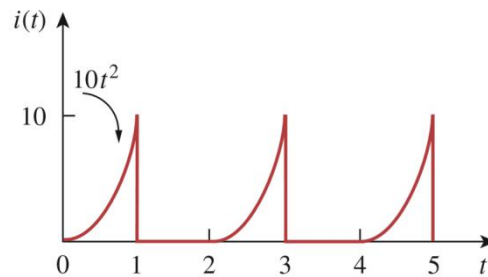

Solution:

(1)

$$v(t) = \begin{cases} t, & 0 < t < 2 \\ -1, & 2 < t < 4 \end{cases}$$

$$V_{\text{rms}}^2 = \frac{1}{4} \left[\int_0^2 t^2 dt + \int_2^4 (-1)^2 dt \right] = \frac{1}{4} \left[\frac{8}{3} + 2 \right] = 1.1667$$

$$V_{\text{rms}} = 1.08V$$


(2)

$$I_{\text{rms}}^2 = \frac{1}{2} \left[\int_0^1 (10t^2)^2 dt + \int_1^2 0^2 dt \right] = 50 \int_0^1 t^4 dt = 10$$


$$I_{\text{rms}} = 3.162A$$

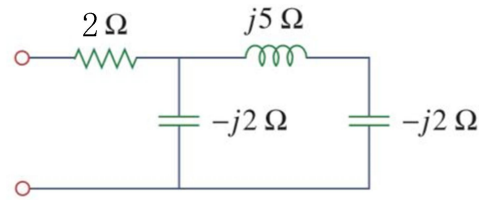4.Apparent Power and Power Factor (12')

Obtain the power factor for each of the circuits. Specify each power factor as leading or lagging.



(a)

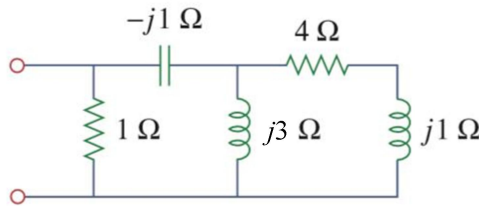

(b)

Solution:

(a)

$$\begin{aligned}
 -j2 \parallel (j5 - j2) &= -j2 \parallel -j3 = -j6 \\
 Z_T &= 2 - j6 = 6.32 \angle -71.57^\circ \Omega \\
 \text{pf} &= \cos(-71.57^\circ) = 0.32 \\
 &\text{(leading)}
 \end{aligned}$$

(b)


$$\begin{aligned}
 j3 \parallel (4 + j) &= \frac{j12 - 3}{4 + j4} = 1.13 + j1.88 \\
 Z &= 1 \parallel (1.13 + j1.88 - j1) = \frac{1.13 + j0.88}{2.13 + j0.88} = 0.6215 \angle 15.46^\circ \Omega \\
 \text{pf} &= \cos(15.46^\circ) = 0.96 \\
 &\text{(lagging)}
 \end{aligned}$$

5. Complex Power (14')

In the circuit, device A receives 2 kW at 0.8 pf lagging, device B receives 3 kVA at 0.8 pf leading, while device C is inductive and consumes 1 kW and receives 7500 VAR.

(a) Determine the power factor of the entire system.

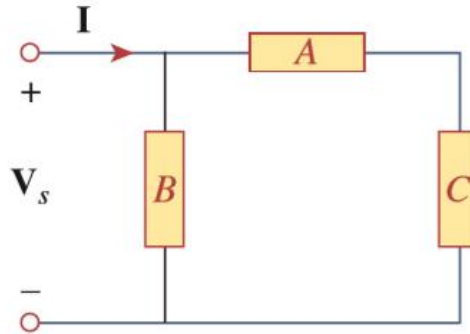(b) Find \mathbf{I} given that $V_s = 120\angle 45^\circ$ V rms.



Solution:

$$S_A = 2000 + j \frac{2000}{0.8} \times 0.6 = 2000 + j1500, \quad (2')$$

$$S_B = 3000 \times 0.8 - j3000 \times \sqrt{1 - 0.8^2} = 2400 - j1800, \quad (2')$$

$$S_C = 1000 + j7500, \quad (2')$$

$$S = S_A + S_B + S_C = 5400 + j7200 \quad (1')$$

(a)

$$\text{pf} = \frac{5400}{\sqrt{5400^2 + 7200^2}} = 0.6, \quad (2'), \text{lagging} \quad (1')$$

(b)


$$S = V_{rms} I_{rms}^* \rightarrow I_{rms}^* = \frac{5400 + j7200}{120\angle 45^\circ} = 75\angle 8.1^\circ A \quad (2')$$

$$I_{rms} = 75\angle -8.1^\circ A \quad (2')$$

6.Power Factor (14')

For the op amp circuit, calculate:

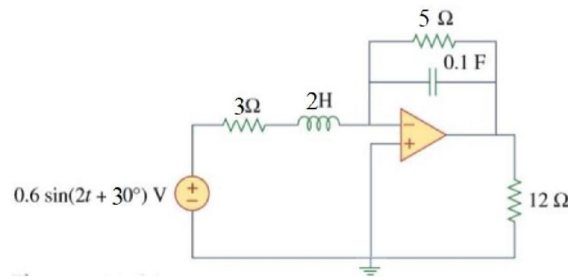- (a) the complex power delivered by the voltage source
 (b) the average power dissipated in the 12Ω resistor




Solution:

$$j\omega L = j2 \times 4 = j4\Omega, \quad \frac{1}{j\omega C} = \frac{1}{j2 \times 0.1} = -j5\Omega$$

$$5 // (-j5) = \frac{-j5 \times 5}{5 - j5} = \frac{5}{2} - j\frac{5}{2}\Omega$$

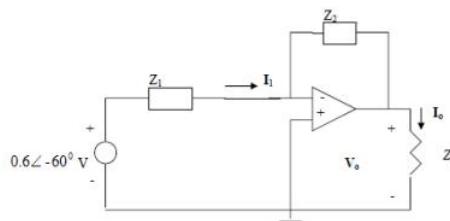The frequency-domain version of the circuit is shown below.



$$Z_1 = 3 + j4\Omega, \quad (2')$$

$$Z_2 = \frac{5}{2} - j\frac{5}{2}\Omega, \quad Z_3 = 12\Omega \quad (2')$$

(a)

$$I_1 = \frac{0.6\angle -60^\circ - 0}{3 + j4} = 0.12\angle -113.1^\circ A, \quad (2')$$

$$S = \frac{1}{2} V_s I_1^* = \frac{1}{2} \times 0.6\angle -60^\circ \times 0.12\angle +113.1^\circ = 0.036\angle 53.1^\circ mVA \quad (2')$$

(b)

$$V_o = -\frac{Z_2}{Z_1} V_s, \quad (2')$$

$$I_o = \frac{V_o}{Z_3} = -\frac{\frac{5}{2} - j\frac{5}{2}}{12(3 + j4)} (0.6\angle -60^\circ) = 0.035\angle -158.1^\circ A \quad (2')$$

$$P = \frac{1}{2} |I_o|^2 R = 0.5 \times 0.035^2 \times 12 = 7.35 mW \quad (2')$$

7. Balanced Three-Phase Voltages (8')

A balanced Y-Y four-wire system has phase voltages

$$V_{an} = 120\angle 0^\circ \text{ V}, V_{bn} = 120\angle -120^\circ \text{ V}, V_{cn} = 120\angle 120^\circ \text{ V}$$

The load impedance per phase is $19 + j13 \Omega$, and the line impedance per phase is $1 + j2 \Omega$. Solve for the line currents and neutral current.

Solution:

$$I_a = \frac{V_{an}}{Z_L + Z_Y} = \frac{120\angle 0^\circ}{20 + j15} = 4.8\angle -36.87^\circ \text{ A} \quad (3')$$


$$I_b = I_a\angle -120^\circ = 4.8\angle -156.87^\circ \text{ A} \quad (2')$$

$$I_c = I_a\angle 120^\circ = 4.8\angle 83.87^\circ \text{ A} \quad (2')$$

$$\text{As a balanced system, } I_n = 0 \text{ A} \quad (1')$$

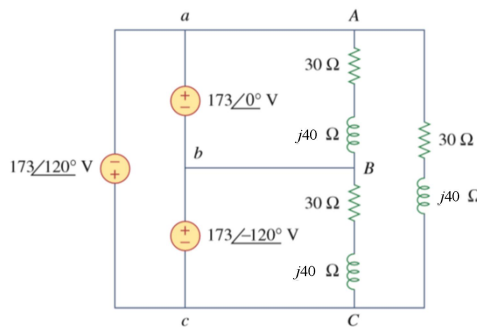8. Balanced Delta-Delta Connection (10')

For the $\Delta - \Delta$ circuit, calculate the phase and line currents.



Solution:

$$Z_{\Delta} = 30 + j40 = 50\angle 53.1^\circ \Omega \quad (2')$$

The phase currents are

$$I_{AB} = \frac{V_{ab}}{Z_{\Delta}} = \frac{173\angle 0^\circ}{50\angle 53.1^\circ} = 3.46\angle -53.1^\circ \text{ A} \quad (2')$$

$$I_{BC} = I_{AB}\angle -120^\circ = 3.46\angle -173.1^\circ \text{ A} \quad (1')$$

$$I_{CA} = I_{AB}\angle 120^\circ = 3.46\angle 66.9^\circ \text{ A} \quad (1')$$

The line currents are


$$I_a = I_{AB} - I_{CA} = I_{AB}\sqrt{3}\angle -30^\circ = 5.99\angle -83.1^\circ \text{ A} \quad (2')$$

$$I_b = I_a\angle -120^\circ = 5.99\angle -203.1^\circ \text{ A} \quad (1')$$

$$I_c = I_a\angle 120^\circ = 5.99\angle 36.9^\circ \text{ A} \quad (1')$$

9. Balanced Delta-Wye Connection (10')

In the circuit, if $V_{ab} = 440\angle 0^\circ V$, $V_{bc} = 440\angle -120^\circ V$, $V_{ca} = 440\angle 120^\circ V$ find the line currents

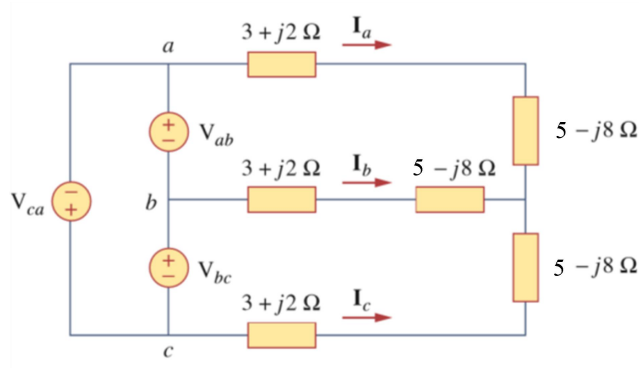**Solution:**

Convert the delta-connected source to an equivalent wye-connected source and consider the single-phase equivalent.

$$I_a = \frac{440\angle(0^\circ - 30^\circ)}{\sqrt{3}Z_Y}, \quad (2')$$

$$\text{where } Z_Y = 3 + j2 + 5 - j8 = 8 - j6 = 10\angle -36.9^\circ \Omega, \quad (2')$$

$$I_a = \frac{440\angle(0^\circ - 30^\circ)}{\sqrt{3} \times 10\angle -36.9^\circ} = 25.404\angle 6.9^\circ A, \quad (2')$$

$$I_b = I_a\angle -120^\circ = 25.404\angle -113.1^\circ A, \quad (2')$$

$$I_c = I_a\angle 120^\circ = 25.404\angle 126.9^\circ A \quad (2')$$