

Homework 4

Due date: Nov. 9th, 2021


Turn in your homework in class

Rules:


- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.
- If needed, round the number to the nearest hundredths, i.e., rounding it to 2 decimal places.

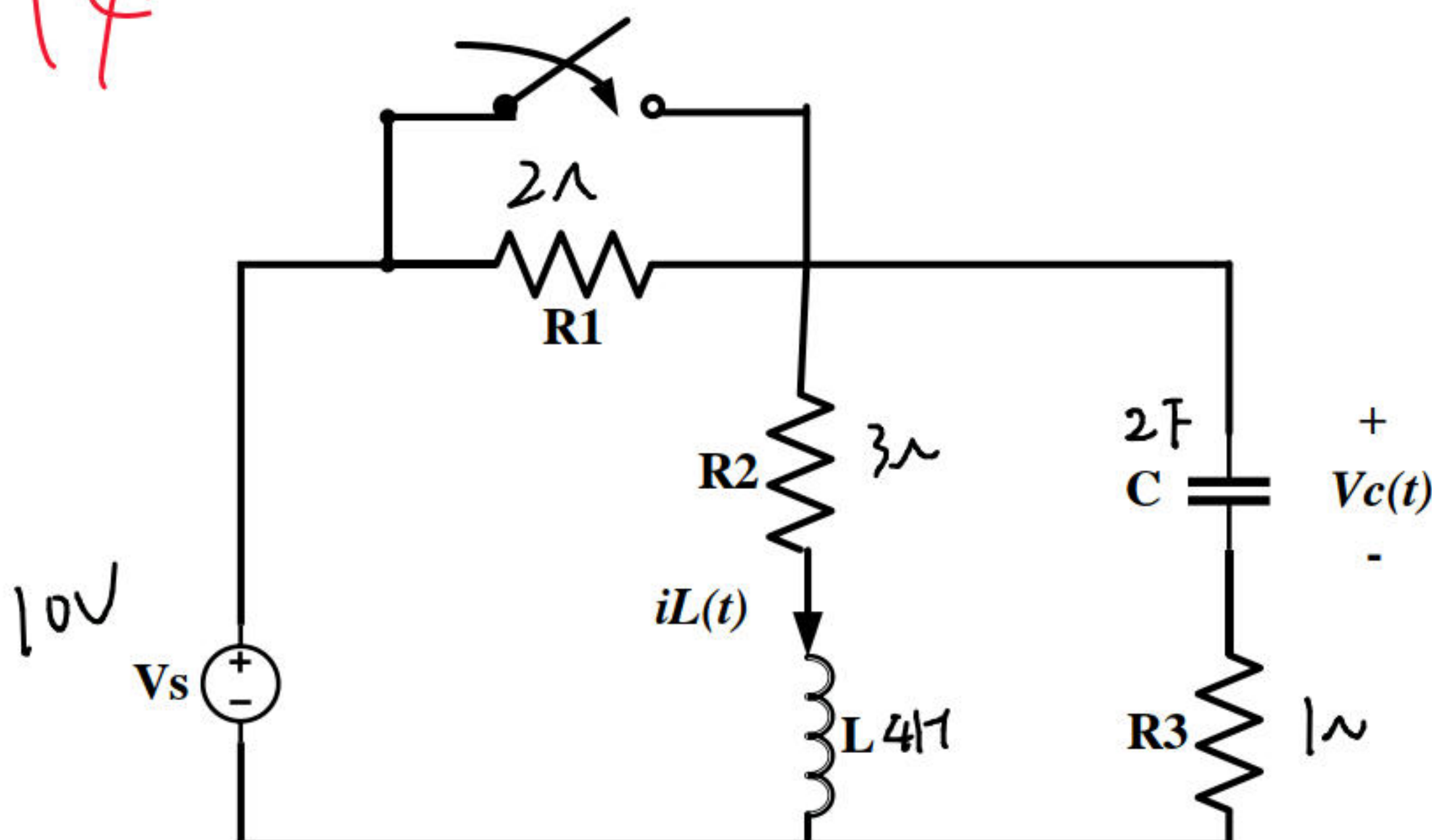1. For the circuit below, the switch has been open for a long time. At $t=0$, the switch was closed. Given $V_s=10V$, $R_1=2\Omega$, $R_2=3\Omega$, $R_3=1\Omega$, $L=4H$, $C=2F$

find $V_c(0+)$, $\frac{dV_c(0+)}{dt}$, $i_L(0+)$, $\frac{di_L(0+)}{dt}$.



$t < 0$ Steady State

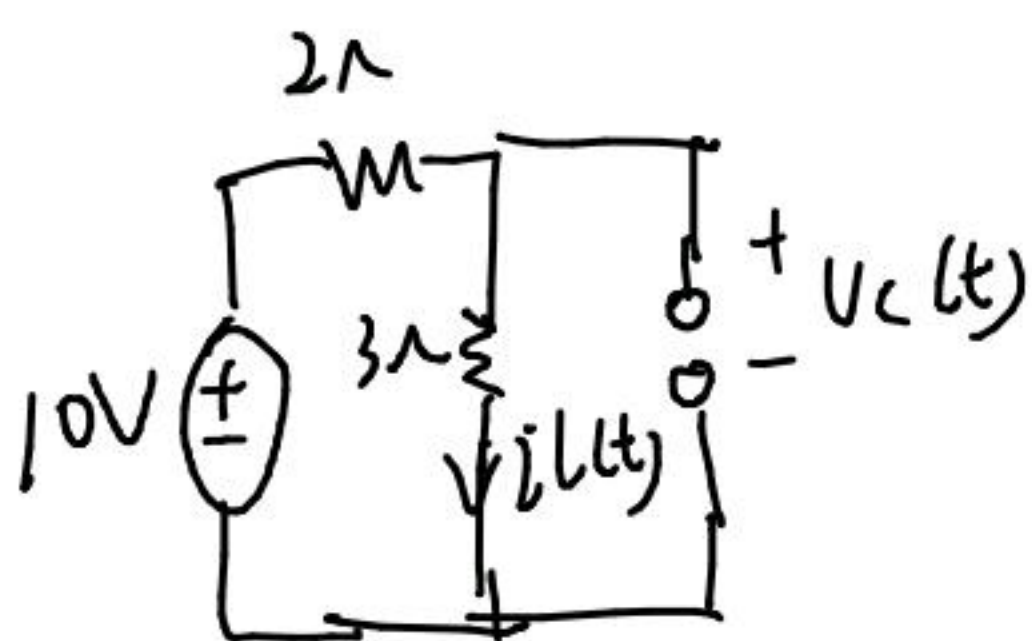

$$i_L(0-) = 2A \quad 2'$$


$$V_c(0-) = 6V \quad 2'$$

$t > 0$

The feature of capacitors and inductors determine:

$$i_L(0+) = i_L(0-) \quad 1'$$

$$V_c(0+) = V_c(0-) \quad 1'$$

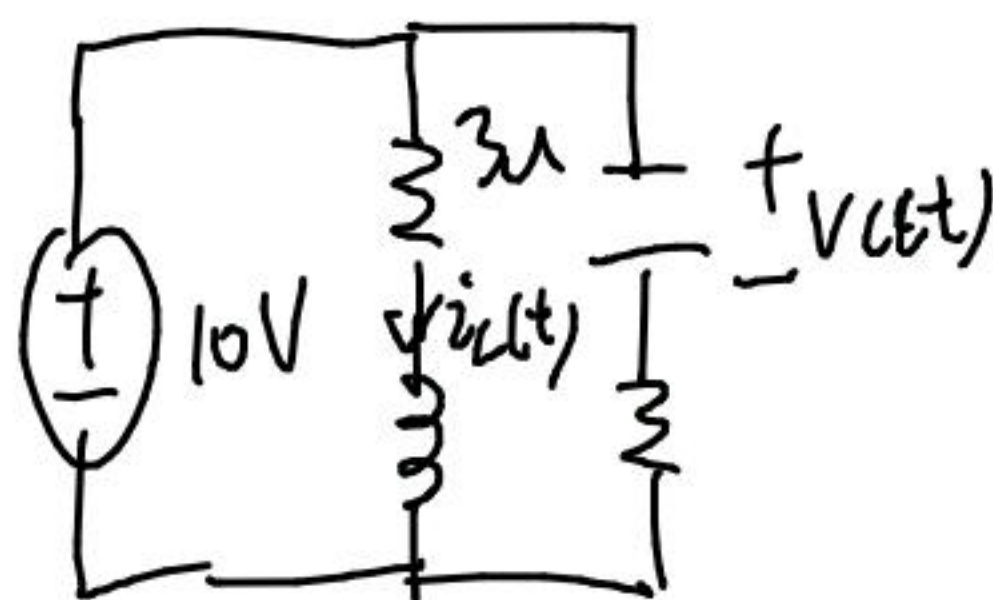

$$V_{R2} = i_L(0+) \cdot R_2 = 6V$$

$$V_L = V_s - V_{R2} = 4V = L \frac{di_L(0+)}{dt} \quad 2'$$

$$\frac{di_L(0+)}{dt} = 1 \quad 2'$$


$$V_{R3} = V_s - V_c(0+) = 4V$$

$$i_c = \frac{V_{R3}}{R_3} = 4A \quad 2'$$

$$= C \frac{dV_c(0+)}{dt}$$


$$\frac{dV_c(0+)}{dt} = 2 \quad 2'$$

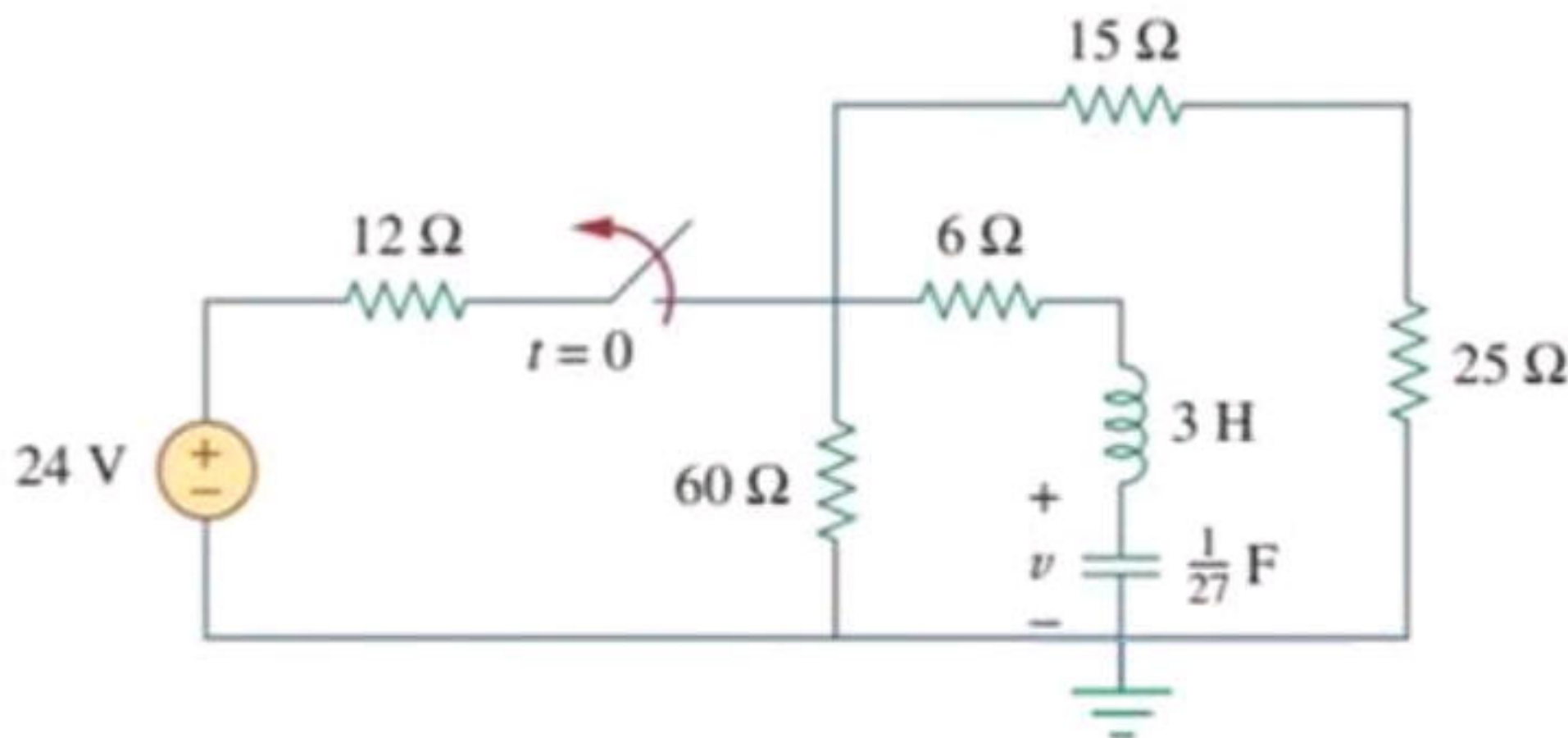- 17/ 2. For the circuit below. The switch has been closed for a long time. At $t=0$, the switch was opened. Calculate $v(t)$ for $t>0$.



$t < 0$

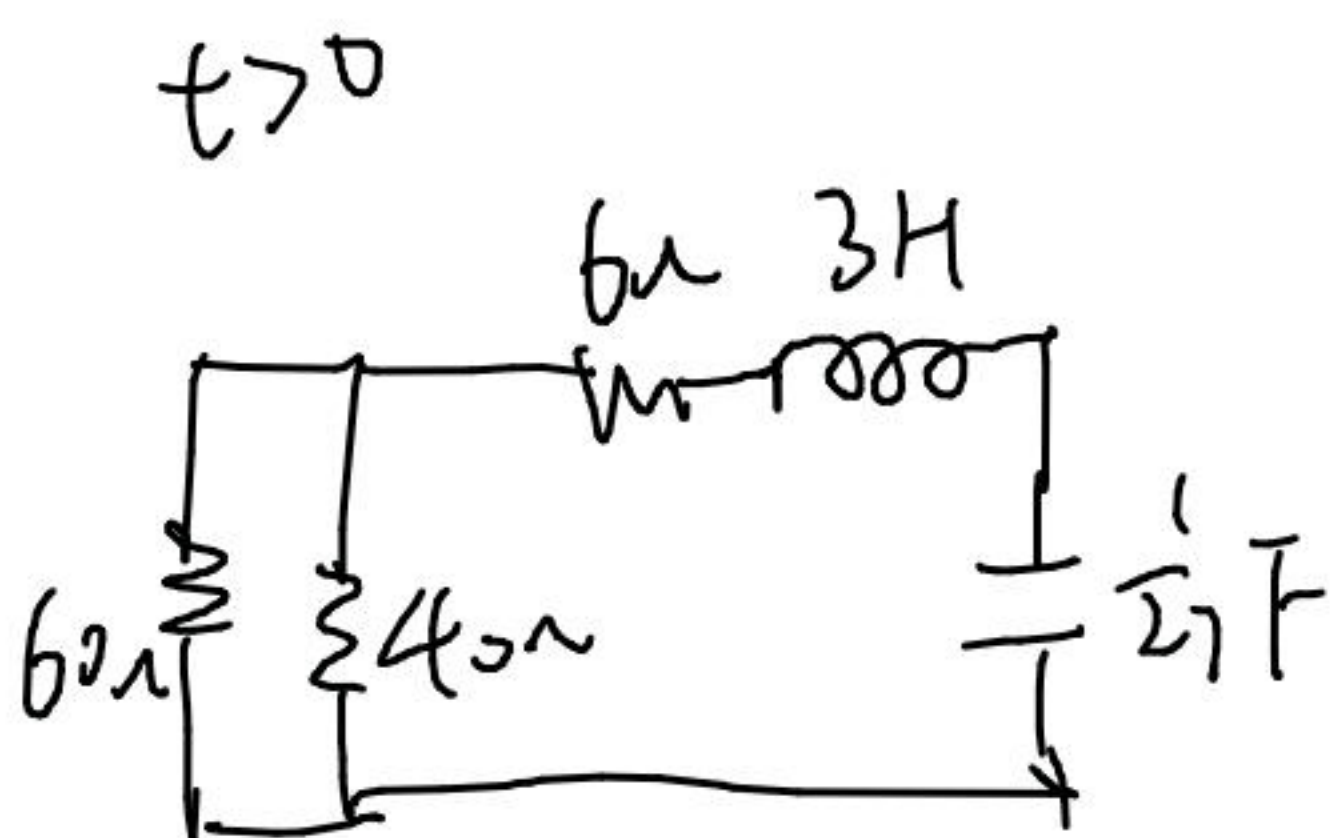$i_L(0^-) = 0 \text{ A}$
 $v_C(0^-) = V_S \cdot \frac{40 \parallel 60}{12 + 40 \parallel 60}$
 $= 16 \text{ V}$



$R_{all} = 40 \parallel 60 + 6 \Omega$
 $= 30 \Omega$

$\frac{d^2 v_C(t)}{dt^2} + \frac{R_{all}}{L} \frac{dv_C(t)}{dt} + \frac{1}{LC} v_C(t) = 0$

$\frac{d^2 v_C(t)}{dt^2} + 10 \frac{dv_C(t)}{dt} + 9 = 0$
 $v_C(t) = A_1 e^{-9t} + A_2 e^{-t}$

$v_C(0^+) = v_C(0^-) = 16 \text{ V}$
 $= A_1 + A_2$

$i_C(0^+) = C \frac{dv_C(0^+)}{dt} = i_L(0^+)$

$= \frac{1}{27} (-9A_1 - A_2) = 0 \text{ A}$


$A_1 = -2 \quad A_2 = 18$

$v_C(t) = -2e^{-9t} + 18e^{-t} \text{ V}$

$t > 0$

- 17 3. For the circuit below: $R=100\Omega$, $L=0.25\text{H}$, $C=\frac{1}{7500}\text{F}$. $V(t)=\begin{cases} 0, & t < 0 \\ 10e^{-10t}, & t > 0 \end{cases}$

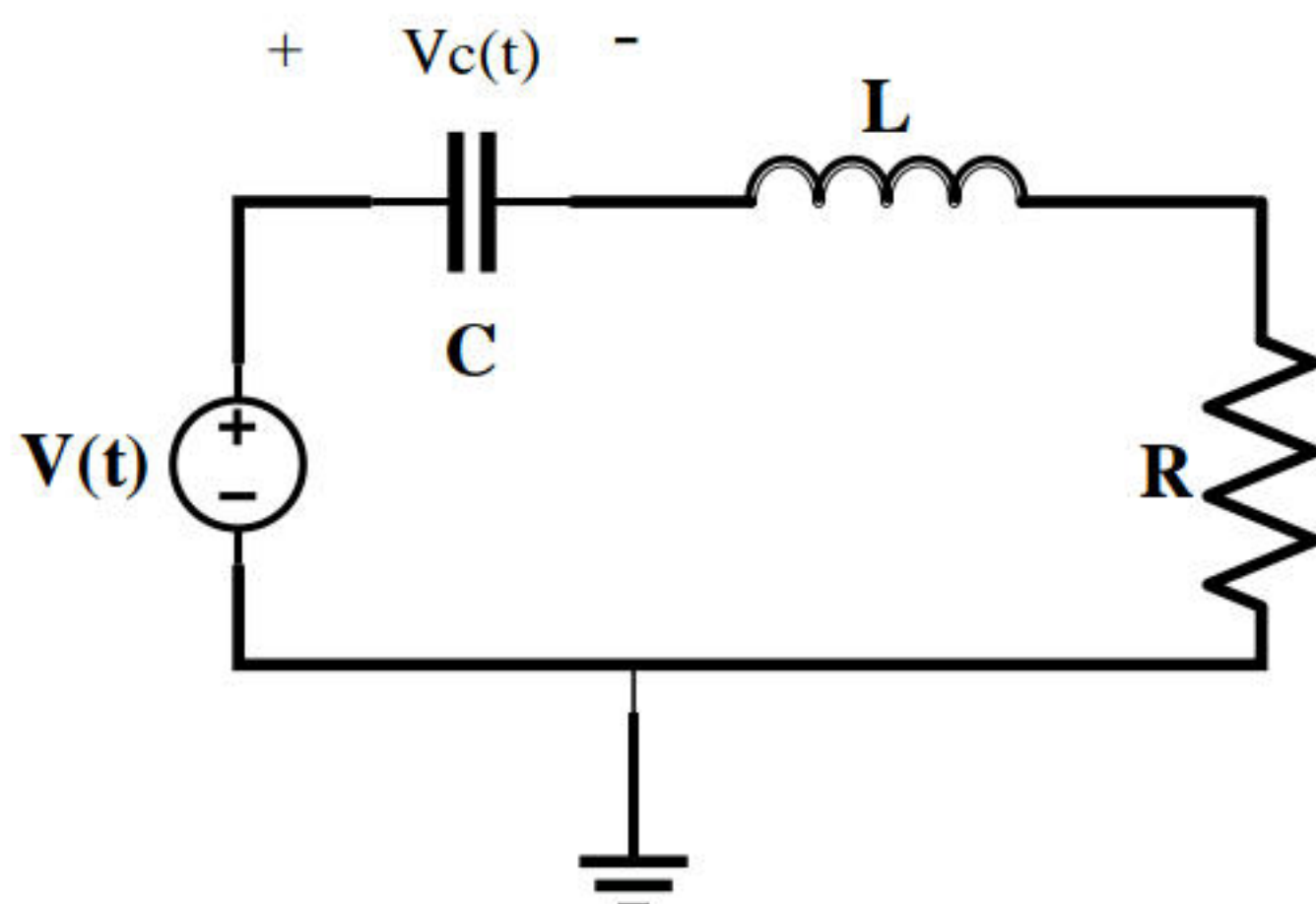Find the expression of $V_C(t)$ for $t > 0$



$$\frac{d^2 V_C(t)}{dt^2} + \frac{R}{L} \frac{dV_C(t)}{dt} + \frac{1}{LC} V_C(t) = \frac{V(t)}{LC}$$

$$\frac{d^2 V_C(t)}{dt^2} + 400 \frac{dV_C(t)}{dt} + 30000 V_C(t) = 3 \times 10^5 e^{-10t} \quad 1'$$

$$y_h: V_C(t) = A_1 e^{-300t} + A_2 e^{-100t} \quad 2'$$

$$y_p: \text{find } s_1, s_2 \quad y_p(t) = A_3 e^{-10t} \quad 2'$$

$$100 A_3 e^{-10t} - 4000 A_3 e^{-10t} + 30000 A_3 e^{-10t} = 3 \times 10^5 e^{-10t}$$

$$A_3 = \frac{1000}{87} \quad 2'$$


$$V_C(t) = A_1 e^{-300t} + A_2 e^{-100t} + A_3 e^{-10t}$$

$$\begin{cases} V_C(0^+) = 0 \text{ V} \\ i_C(0^+) = 0 \text{ A} \end{cases} \Rightarrow \begin{cases} A_1 + A_2 + A_3 = 0 \\ -300 A_1 - 100 A_2 - 10 A_3 = 0 \end{cases}$$

$$A_1 = \frac{150}{29} \quad A_2 = -\frac{30}{3}$$

$$V_C(t) = 5.172 e^{-300t} - 16.667 e^{-100t} + 11.444 e^{-10t} \quad \checkmark \quad 2'$$

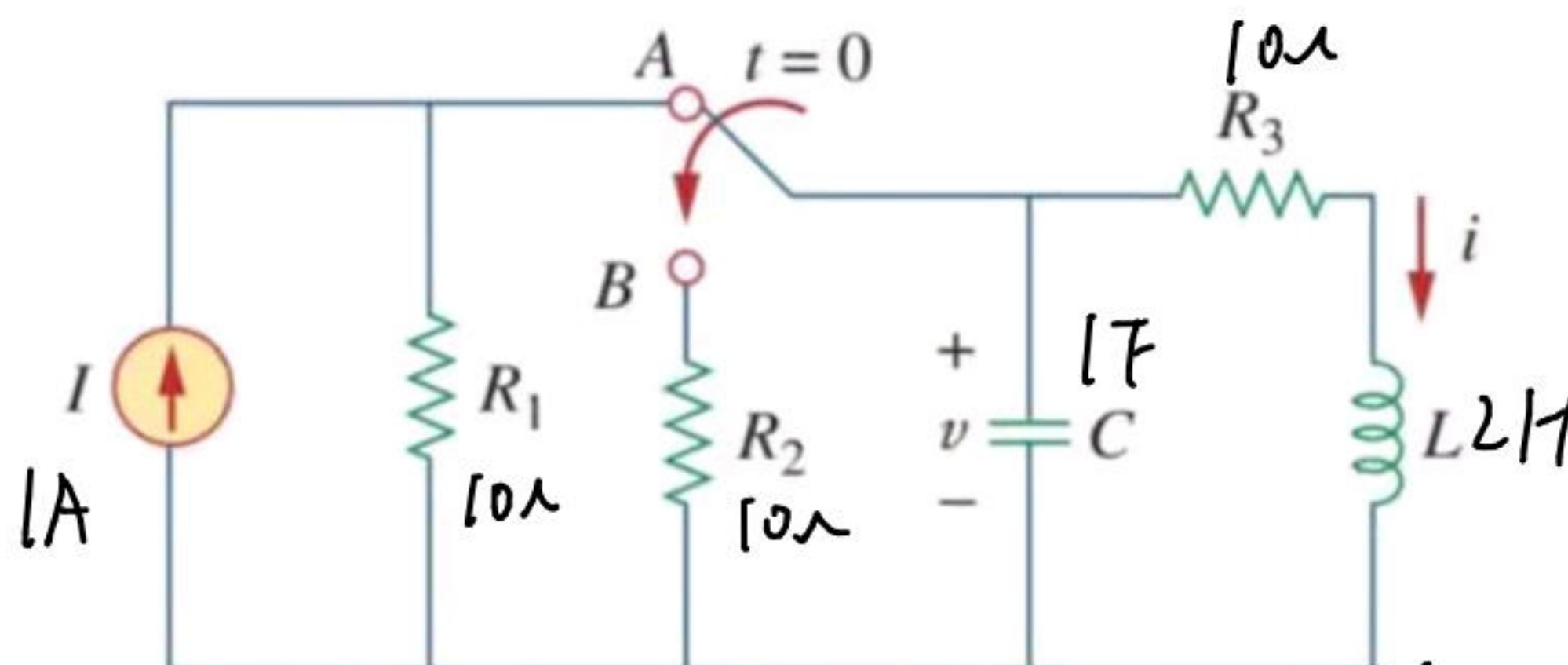4. In the circuit below, we assume that the switch is at Position A for a long time, but moved to Position B at $t = 0$. Given that $I = 1\text{A}$, $R_1 = 10\Omega$, $R_2 = 10\Omega$, $R_3 = 10\Omega$, $C = 1\text{F}$, $L = 2\text{H}$; calculate $i(t)$ for $t > 0$.



$t < 0$

$$V_C(0^-) = 1\text{A} \cdot \frac{10}{10+10} \cdot 10\Omega = 5\text{V}$$

$$\dot{i}_L(0^-) = 1\text{A} \cdot \frac{10}{10+10} = 0.5\text{A}$$

$t > 0$


$$\hat{i}_L(t) = A_1 e^{-0.204t} + A_2 e^{-4.896t} \text{ A}$$

$$\hat{i}_L(0^+) = 0.5\text{A} = A_1 + A_2$$

$$V_L(0^+) = V_C(0^+) - \dot{i}_L(0^+) \cdot R_3 = 0\text{V} = (-0.204A_1 - 4.896A_2) \cdot 2$$

$$A_1 = 0.522 \quad A_2 = -0.022$$
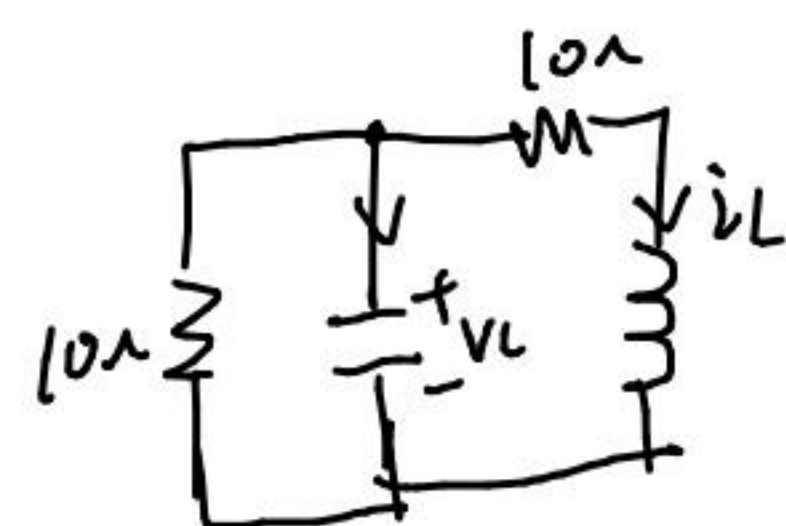
$$\hat{i}_L(t) = 0.522 e^{-0.204t} - 0.022 e^{-4.896t} \text{ A } (t > 0)$$




$$C \frac{dV_C(t)}{dt} + \frac{V_C(t)}{10\Omega} + \frac{V_C(t) - L \frac{d\hat{i}_L(t)}{dt}}{10\Omega} = 0$$

$$V_C(t) = L \frac{d\hat{i}_L(t)}{dt} + 10\Omega \cdot \hat{i}_L(t)$$

$$\frac{d^2 \hat{i}_L(t)}{dt^2} + 5.1 \frac{d\hat{i}_L(t)}{dt} + \hat{i}_L(t) = 0$$

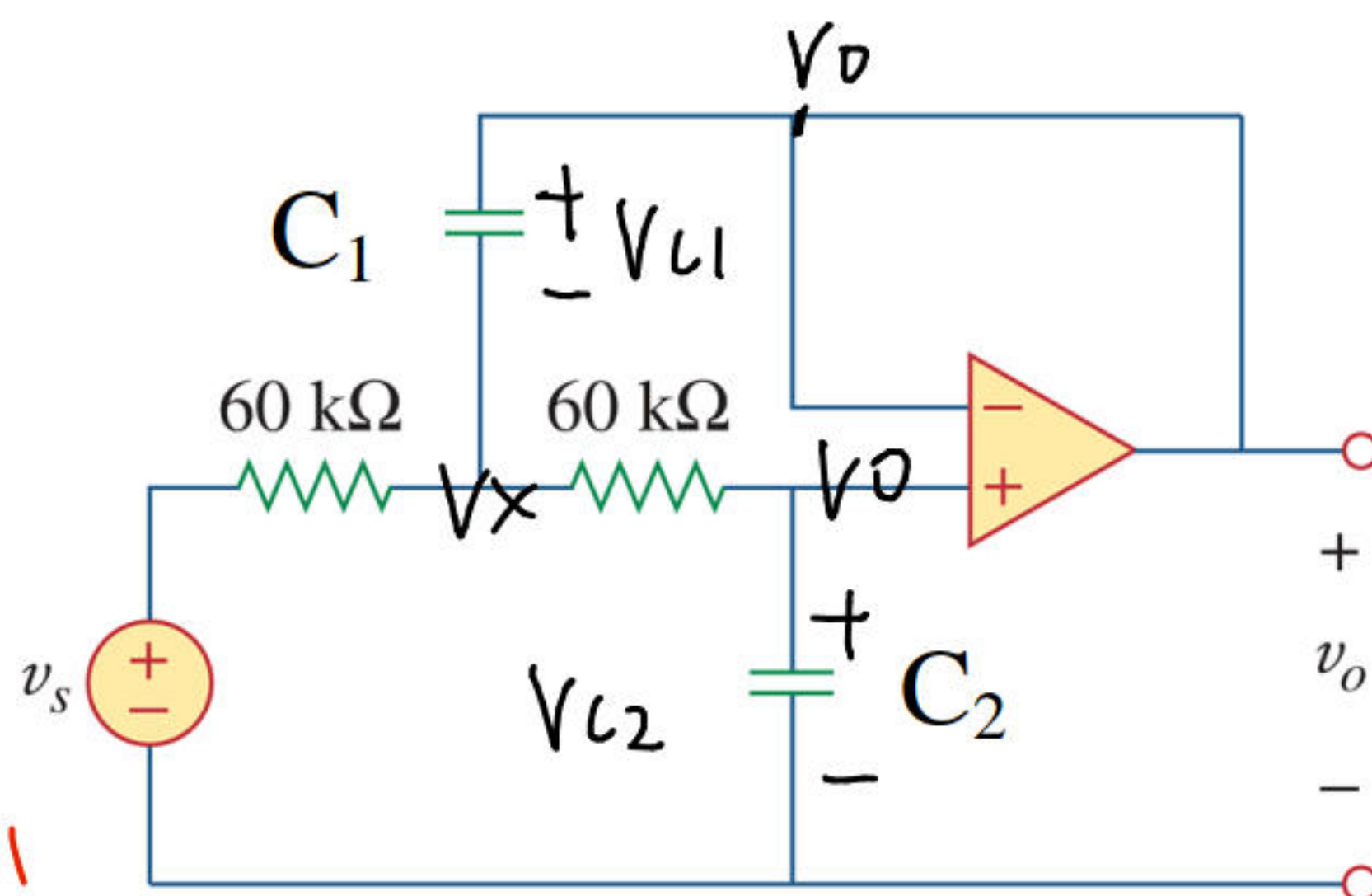5. For the circuit below. The operational amplifier is working in the linear mode.
 Given $V_s = u(t)$ V; $C_1 = C_2 = 60 \mu\text{F}$ and no initial energy stored in both capacitors.
 find expression of $v_o(t)$ for $0 < t < 0.5$ sec.



$$v_o(t) = v_{C2}(t) \quad v_s(t) = 1 \text{ V} \quad t \geq 0$$

$$\frac{V_s - V_X}{60 \text{ k}\Omega} + \frac{V_o - V_X}{60 \text{ k}\Omega} + C \frac{d(V_o - V_X)}{dt} = 0 \quad 2'$$

$$V_o - V_X = V_{C1} \quad 2'$$

$$\frac{V_X - V_o}{60 \text{ k}\Omega} = C \frac{dV_{C2}}{dt} \quad 2'$$

$$V_{C1} = -3.6 \frac{dV_{C2}}{dt}$$

$$\frac{d^2 V_{C2}(t)}{dt^2} + \frac{5}{9} \frac{dV_{C2}(t)}{dt} + \frac{25}{324} V_{C2}(t) = \frac{25}{324} \quad 3'$$

$$V_{C2}(t) = (A_1 t + A_2) e^{-\frac{5}{18} t} + 1 \text{ V}$$

$$V_{C2}(0+) = A_2 + 1 = 0 \text{ V} \quad 2'$$


$$i_{C2}(0+) = C_2 (A_1 - \frac{5}{18} A_2) = 0 \text{ A} \quad 2'$$

$$A_2 = -1 \quad A_1 = -\frac{5}{18}$$

$$V_{C2}(t) = V_o(t) \quad (0 < t < 0.5 \text{ s})$$

$$= (-1 - 0.278t) e^{-0.278t} + 1 \text{ V} \quad 2'$$

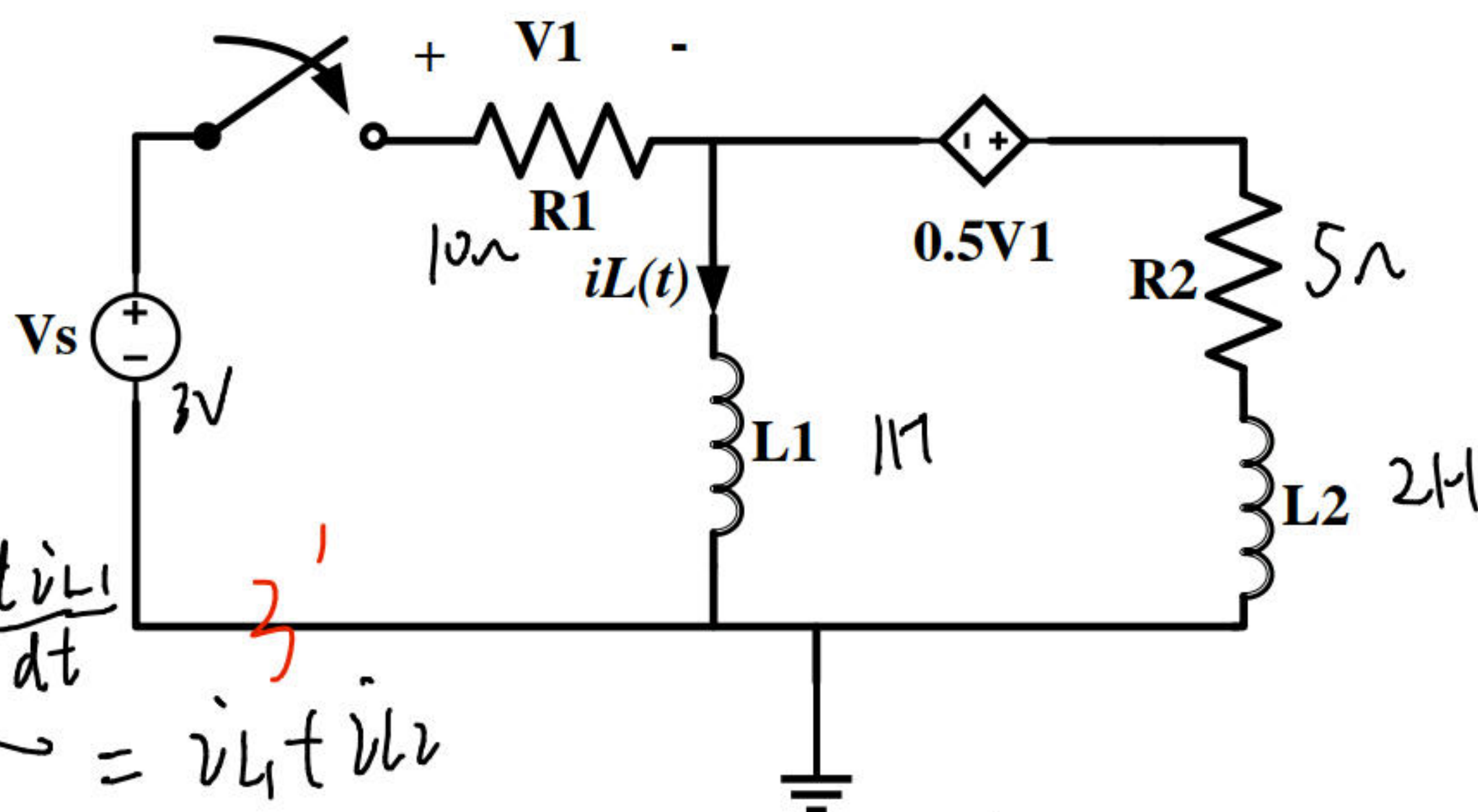5. For the circuit below. The switch has been open for a long time. At $t = 0$ the switch is closed. There is no energy stored in inductors $L1$ and $L2$. Given $R1 = 10\Omega$, $R2 = 5\Omega$, $L1 = 1H$, $L2 = 2H$, $V_s = 3V$, find $i_L(t)$ for $t > 0$.



$$\frac{V_s - L_1 \frac{di_{L1}}{dt}}{R_1} = i_{L1} + i_{L2}$$

$$V_s + 0.5 \left(V_s - L_1 \frac{di_{L1}}{dt} \right) = V_s - L_1 \frac{di_{L1}}{dt} + i_{L2} \cdot R_2 + L_2 \frac{di_{L2}}{dt}$$

$$i_{L2}(t) = \frac{3}{10} - \frac{1}{10} \frac{di_{L1}}{dt} - i_{L1} \quad 2'$$

$$-0.5 V_s - 0.5 \cdot \frac{di_{L1}}{dt} + 5 i_{L1} + 2 \frac{di_{L2}}{dt} = 0$$

$$-1.5 - 0.5 \frac{di_{L1}}{dt} + 1.5 - 0.5 \frac{di_{L1}}{dt} - 5 i_{L1} - 0.2 \frac{d^2 i_{L1}}{dt^2} - 2 \frac{di_{L1}}{dt} = 0$$

$$\frac{d^2 i_{L1}}{dt^2} + 15 \frac{di_{L1}}{dt} + 25 i_{L1} = 0$$

$$i_{L1}(t) = A_1 e^{\frac{-15+5\sqrt{5}}{2} t} + A_2 e^{\frac{-15-5\sqrt{5}}{2} t} \quad A \quad 2'$$

$$i_{L1}(0+) = i_{L1}(0-) = 0A = A_1 + A_2 \quad 1'$$

$$V_{L1}(0+) = -1.91 A_1 - 13.09 A_2 = 3V \quad 1'$$

$$\Rightarrow A_1 = 0.268$$

$$A_2 = -0.268 \quad 2'$$

$$i_{L1}(t) = 0.268 e^{-1.91t} - 0.268 e^{-13.09t} \quad A \quad (t \geq 0) \quad 2'$$