

Homework 8


Due date: 18:30 of Dec.30th, 2021

Turn in your homework to Tutorial Course Classroom 1B- 110

Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.
- If needed, round the number to the nearest hundredths, i.e., rounding it to 2 decimal places.

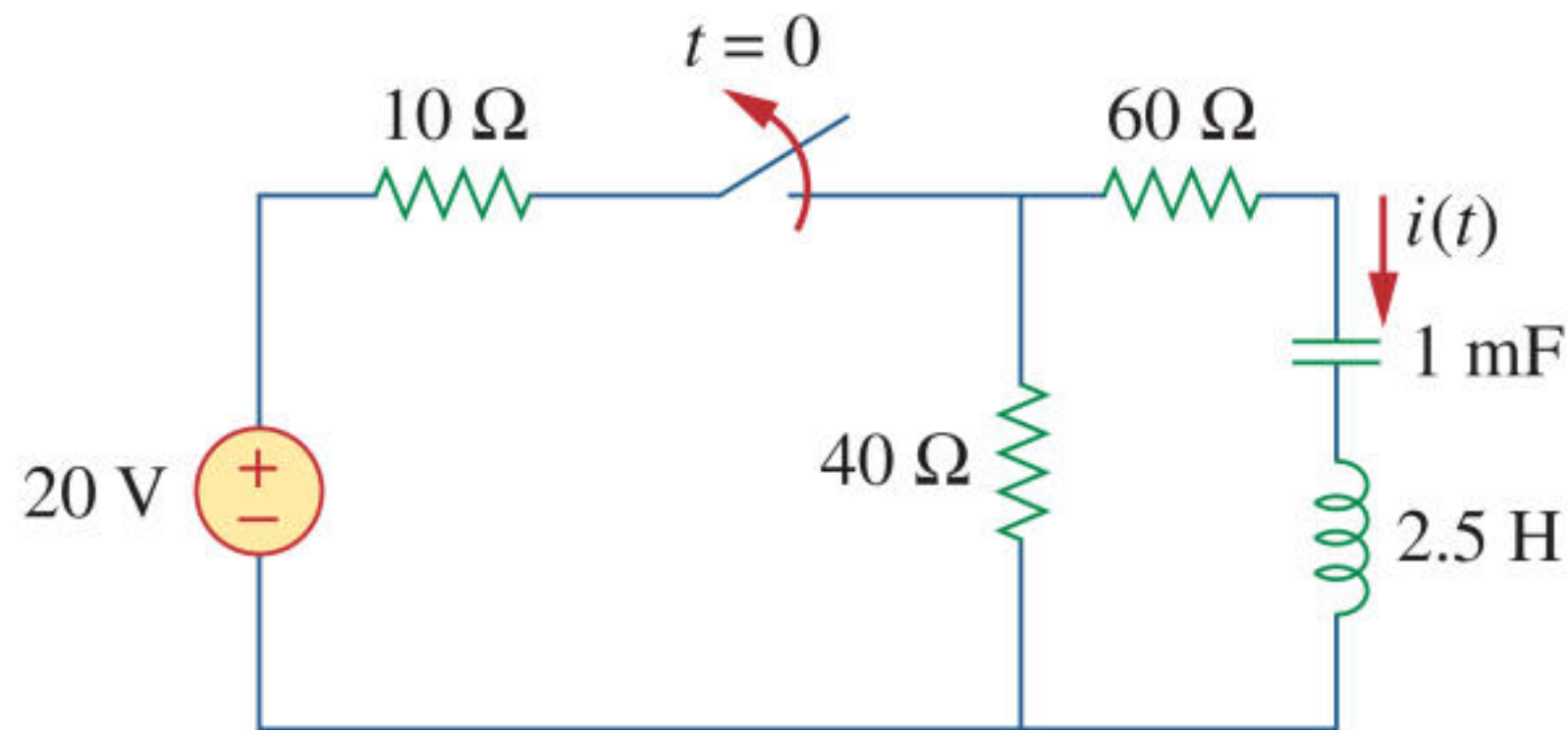
- 16' 1. Use Laplace domain method to find $i(t)$ for $t > 0$ in the circuit below.



$$i_L(0^-) = 0 \text{ A} \quad 2'$$

$$V_C(0^-) = 20 \times \frac{40}{40+10} = 16 \text{ V} \quad 2'$$

s-domain:

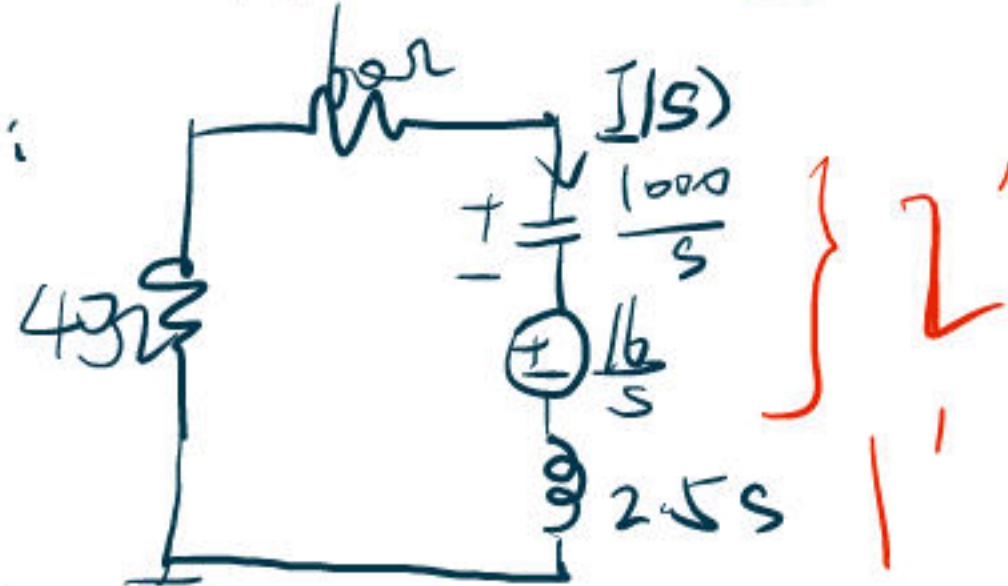

$$\text{Apply KVL: } 100 I(s) + \frac{1000}{s} I(s) + \frac{16}{s} + 2.5 s I(s) = 0 \quad 3'$$


$$I(s) = \frac{-\frac{16}{s}}{100 + \frac{1000}{s} + 2.5s} \quad 2'$$

$$= \frac{-6.4s}{(s+20)^2} \quad 2'$$

$$i(t) = [-6.4t e^{-20t} \text{ (A)}] u(t) \quad t > 0 \quad 2'$$


22

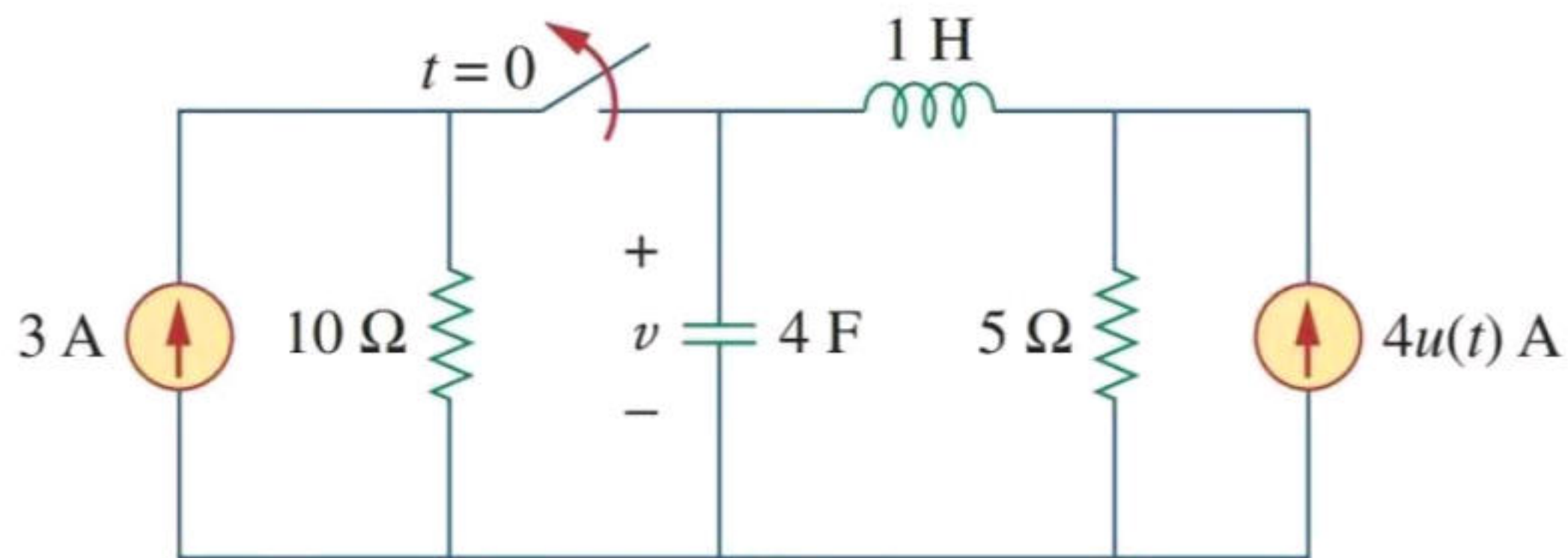2. The switch has been closed for a long time and use Laplace domain method to find $v(t)$ for $t > 0$ in the circuit in the figure below.



$$i_L(0^-) = 3 \times \frac{10}{10+5} = 2A$$

$$V_C(0^-) = (2A) \times 5 = 10V$$

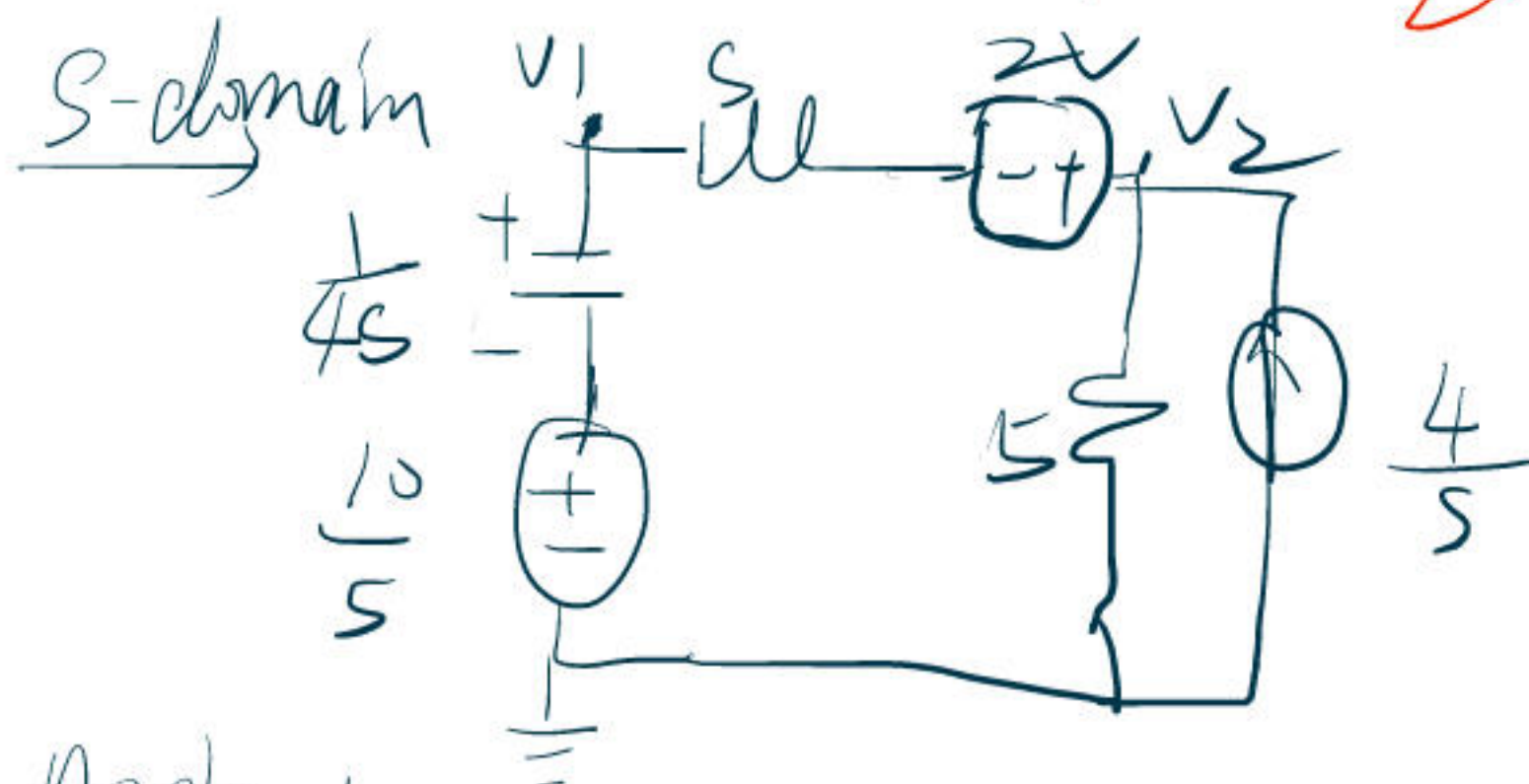

Apply KCL:

$$\frac{v_1 + 2 - v_2}{s} + \frac{4}{s} = \frac{v_2}{5}$$

$$\frac{\frac{10}{s} - v_1}{\frac{1}{4s}} = \frac{v_1 + 2 - v_2}{s}$$

$$\Rightarrow v_1 = V_C(s) = \frac{40s^2 + 18s + 5}{4s^2 + 20s + 1}$$

$$\Rightarrow V_1 = \frac{10s^2 + 48.5s + 5}{s(s^2 + 5s + \frac{1}{4})} = \frac{10s^2 + 48.5s + 5}{s(s - \frac{-5 + 2\sqrt{6}}{2})(s - \frac{-5 - 2\sqrt{6}}{2})}$$

$$= \frac{A}{s} + \frac{B}{s - \frac{-5 + 2\sqrt{6}}{2}} + \frac{C}{s - \frac{-5 - 2\sqrt{6}}{2}}$$

$$A = sV_c(s) \Big|_{s=0} = 20 \quad 2'$$

$$B = \left(s - \frac{-5+2j6}{2} \right) V_c(s) \Big|_{s = \frac{-5+2j6}{2}} = -10.205 \quad 2'$$

$$C = \left(s - \frac{-5-2j6}{2} \right) V_c(s) \Big|_{s = \frac{-5-2j6}{2}} = 0.205 \quad 2'$$

$$\Rightarrow V_c(s) = \frac{20}{s} + \frac{-10.205}{s + 0.0505} + \frac{0.205}{s + 4.949} \quad 2'$$

$$\Rightarrow V_c(t) = [20 - 10.205 e^{-0.0505t} + 0.205 e^{-4.949t} u(t)] \text{ (V)} \quad 2'$$


$t \geq 0$

36

3. For the circuit below, $u(t)$ means unit step function. Use Laplace domain method to calculate


(a) $i_L(t)$ for $t > 0$

(b) $v_c(t)$ for $t > 0$

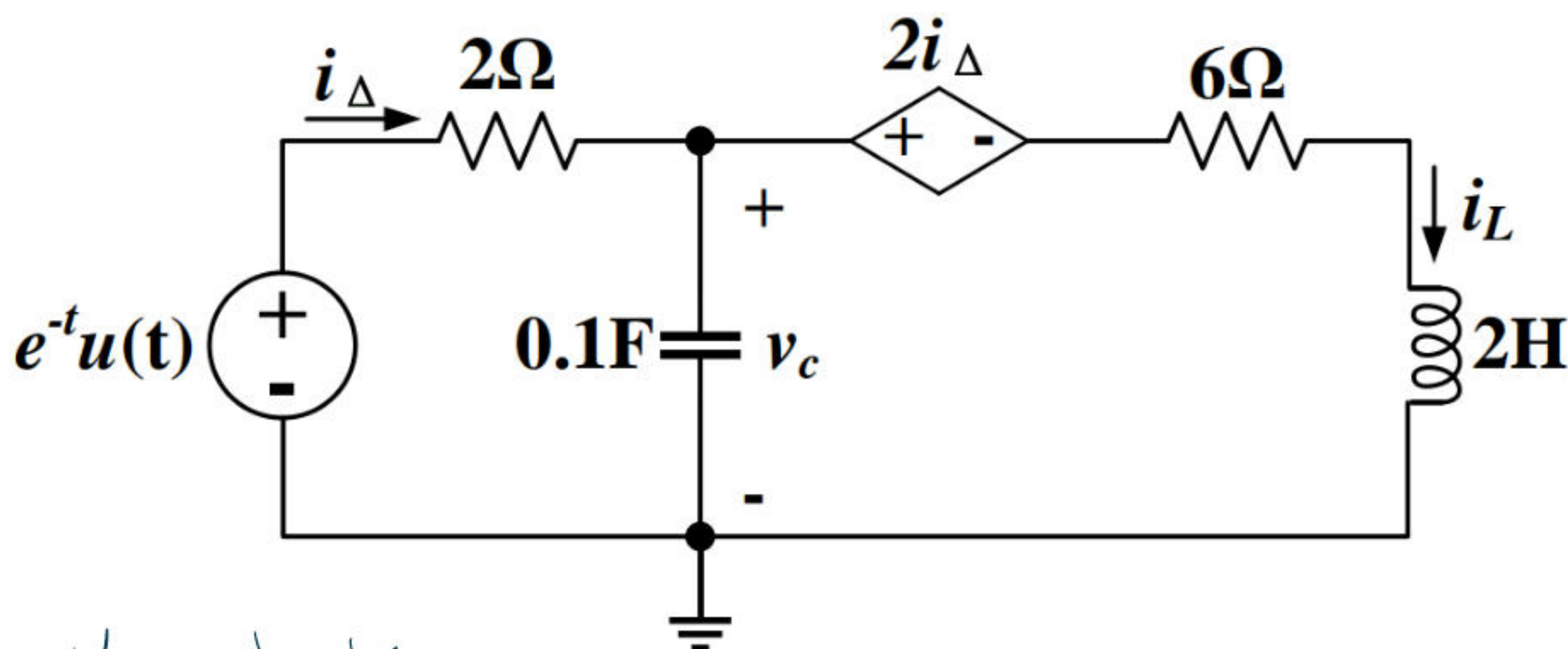

$$v_c(0^-) = V_0 = 0 \quad 2'$$

$$i_L(0^-) = I_0 = 0 \quad 2'$$

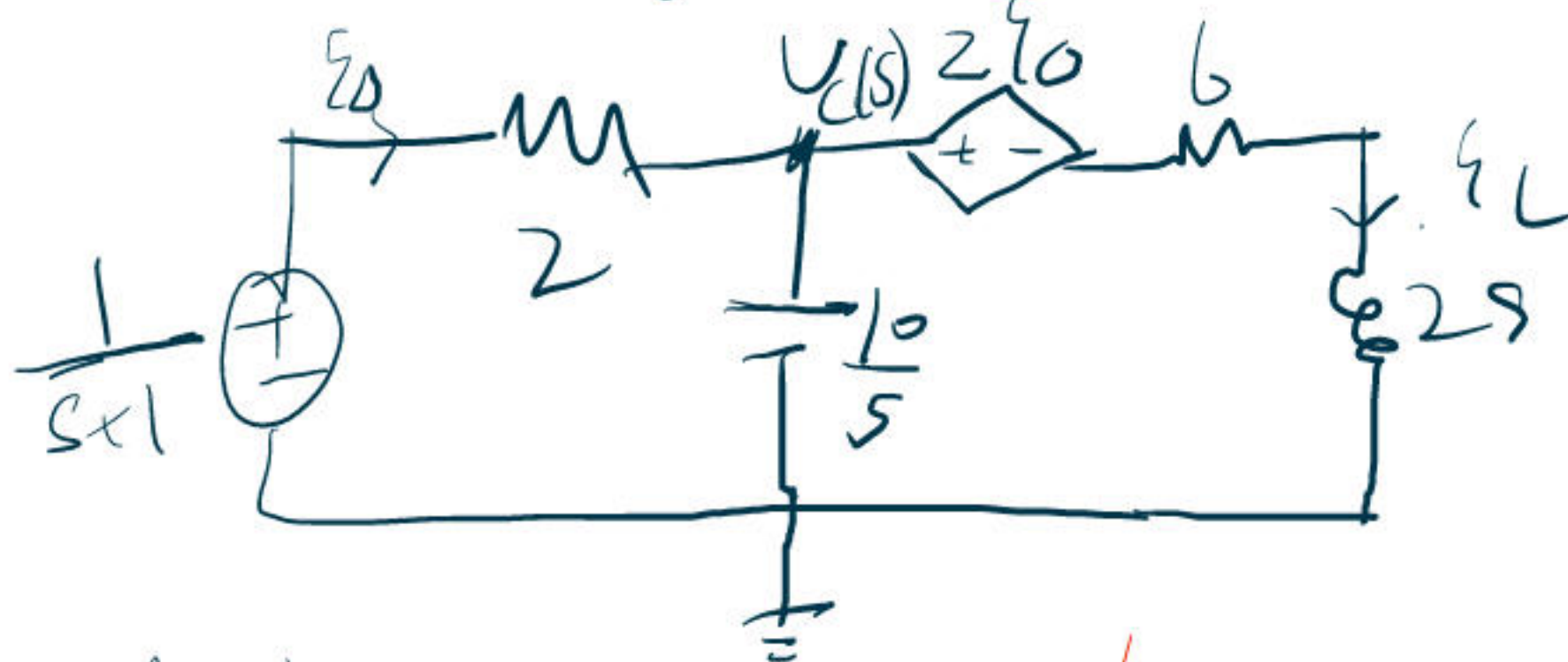

(a) Apply KCL: $3'$

$$\frac{V_c(s) - \frac{1}{s+1}}{2} = -I_\Delta(s) \quad (1)$$

$$-I_\Delta(s) + \frac{V_c(s)}{\frac{10}{s}} + \frac{V_c(s) - 2I_\Delta(s)}{6 + 2s} = 0 \quad (2)$$

$$\frac{V_c(s) - 2I_\Delta(s)}{6 + 2s} = I_L(s) \quad (3)$$

$$\Rightarrow I_L(s) = \frac{5-s}{2(s+1)(s^2+8s+25)} \quad 2'$$

$$= \frac{1}{2} \left[\frac{K_1}{s+1} + \frac{K_2}{s-(-4+3j)} + \frac{K_2^*}{s-(-4-3j)} \right] \quad 2'$$

$$\text{Then } \alpha = -4 \quad w = 3 \quad 2'$$

$$k_1 = \left. \frac{s-s}{2(s^2+8s+25)} \right|_{s=-1} = -\frac{1}{6} \quad 2'$$

$$k_2 = \left. \frac{s-s}{2(s+1)(s-(-4+3j))} \right|_{s=-4+3j} = 0.186 \angle 116.565^\circ \quad 2'$$

$$\Rightarrow I_L(t) = \left[0.167 e^{-t} + 0.373 e^{-4t} \cos(3t + 116.565^\circ) \right] u(t) \text{ (A)} \quad t \geq 0$$

(b) Also from (1)(3)

$$\Rightarrow V_C(s) = \left[\frac{(3+s)(5-s)}{(s+1)(s^2+8s+25)} + \frac{1}{s+1} \right] \cdot \frac{1}{2} \quad 2'$$

$$= \frac{5s+20}{(s+1)(s^2+8s+25)}$$

$$= \frac{k_1}{s+1} + \frac{k_2}{s-(-4+3j)} + \frac{k_2^*}{s-(-4-3j)} \quad 2'$$


$$k_1 = \left. (s+1) V_C(s) \right|_{s=-1} = \frac{5}{6} \quad \alpha = -4, \omega = 3$$

$$k_2 = \left[s - (-4+3j) \right] V_C(s) \Big|_{s=-4+3j} = \frac{5j}{-6-6j} = 0.589 \angle -135^\circ$$

$$\Rightarrow V_C(t) = \left[0.833 e^{-t} + 1.178 e^{-4t} \cos(3t - 135^\circ) \right] u(t) \text{ (V)} \quad t \geq 0$$

26'

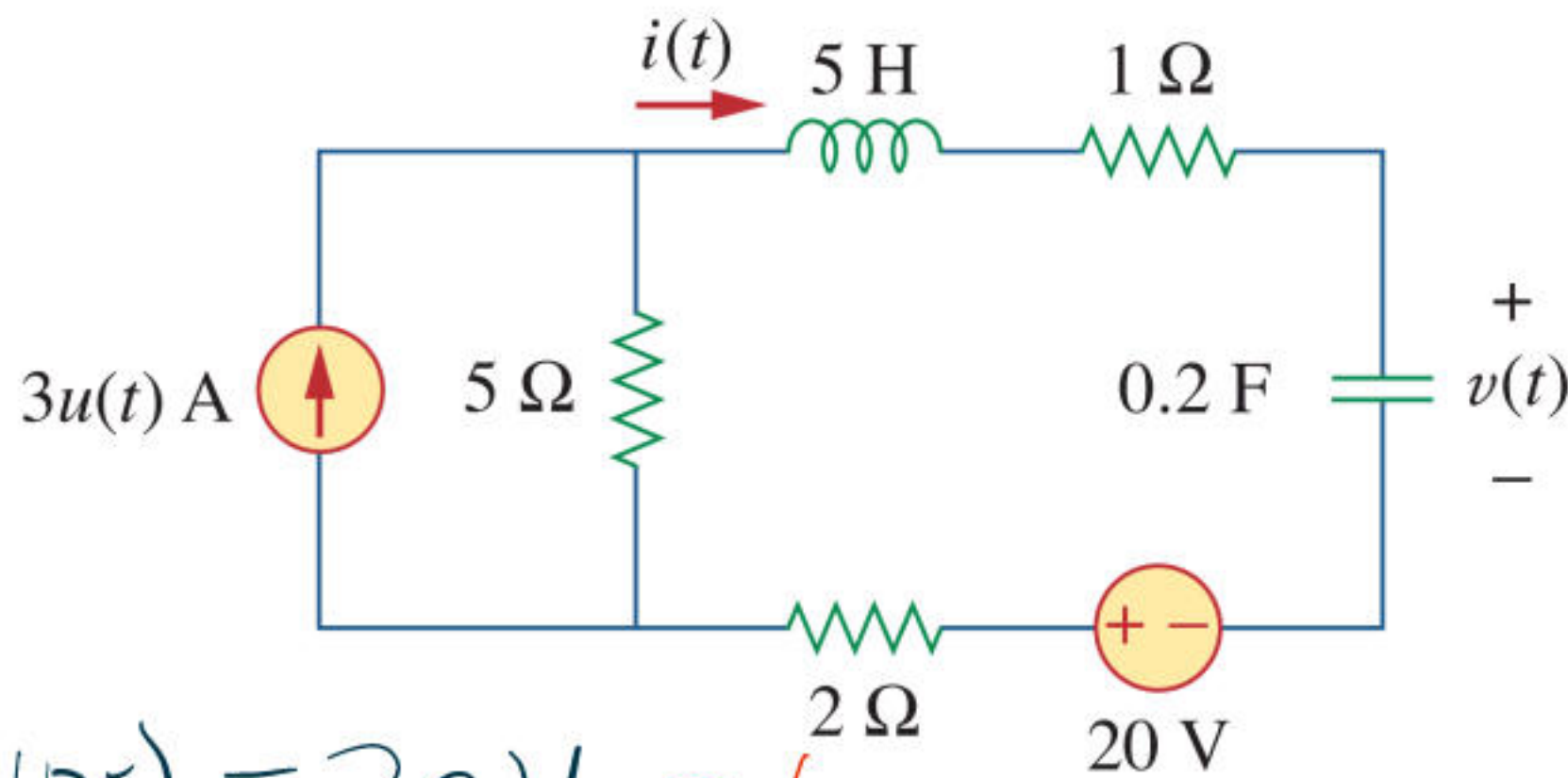
4. Use Laplace domain method to obtain $v(t)$ and $i(t)$ for $t > 0$ in the circuit below.



$$V_C(0^-) = 20 \text{ V}$$

$$i_L(0^-) = 0 \text{ A}$$

Solomonin

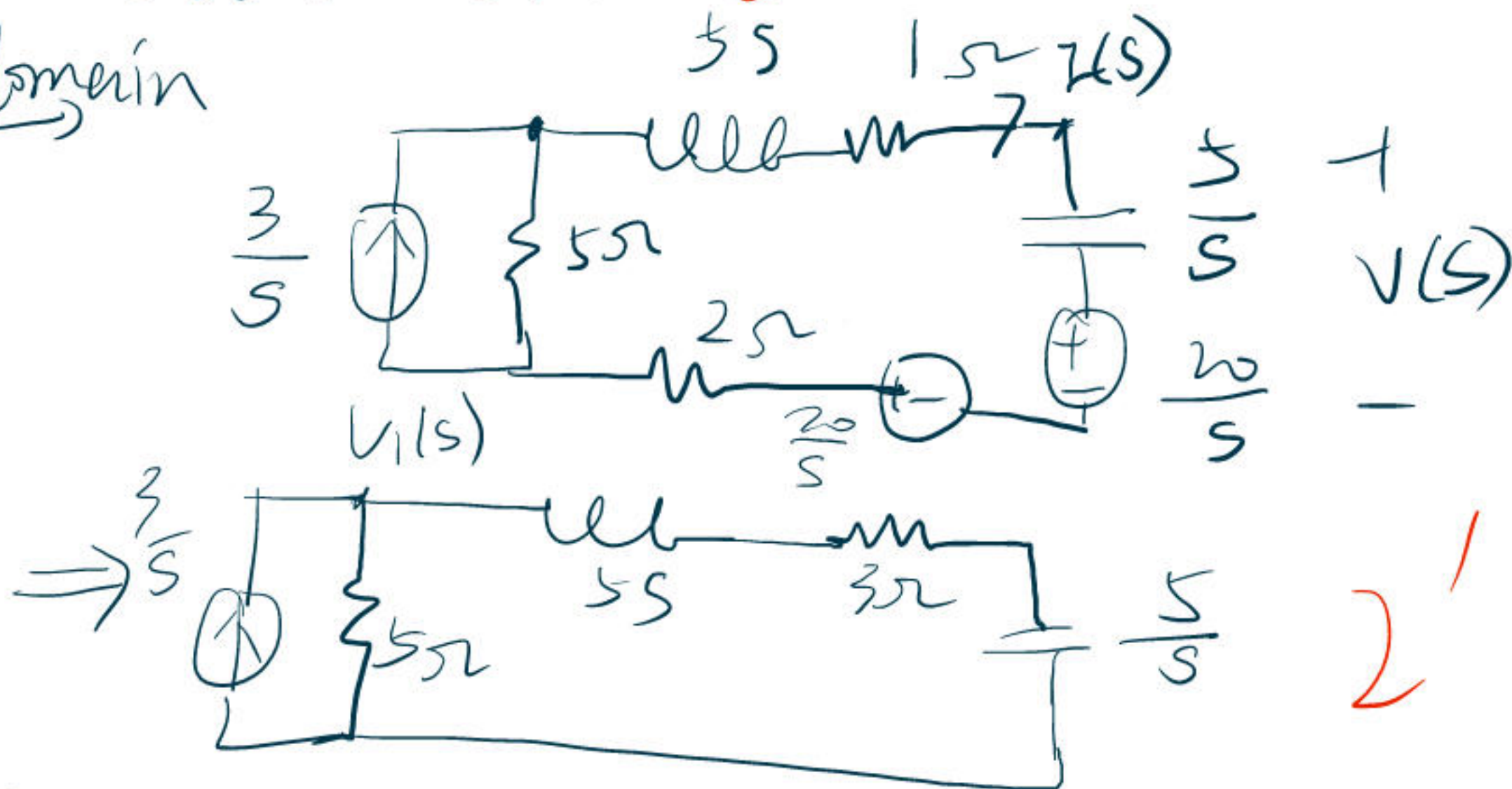

Apply KCL:

$$\frac{v_1(s)}{5} - \frac{3}{s} + \frac{v_1(s)}{5s + 3 + \frac{5}{s}} = 0 \Rightarrow v_1(s) = \frac{15s^2 + 15}{s(s^2 + 1.6s + 1)}$$

$$I(s) = \frac{v_1(s)}{5s + 3 + \frac{5}{s}} = \frac{3}{s^2 + 1.6s + 1} = \frac{K_1}{s - (-0.8 + 0.6j)} + \frac{K_1^*}{s - (-0.8 - 0.6j)}$$

$$K_1 = [s - (-0.8 + 0.6j)] I(s) \Big|_{s = -0.8 + 0.6j} = 2.5 \angle -90^\circ \quad \left. \begin{array}{l} \alpha = -0.8 \\ \omega = 0.6 \end{array} \right\}$$

$$\Rightarrow i(t) = \frac{1}{5} e^{-0.8t} \cos(0.6t - 90^\circ) u(t) \text{ A} \quad t > 0$$

$$V(s) = V(s) \frac{\frac{5}{s}}{5s+3+\frac{5}{s}} + \frac{20}{s} = \frac{100s^2+160s+175}{s(5s^2+25s+5)} = \frac{20s^2+32s+35}{s(s^2+5s+1)} = \frac{k_1}{s} + \frac{k_2}{s(-0.8+0.6j)} + \frac{k_2^*}{s(-0.8-0.6j)}$$

$$k_1 = s V(s) \Big|_{s=0} = 35 \quad 2'$$

$$k_2 = s(-0.8+0.6j) V(s) \Big|_{s=-0.8+0.6j} = 12.5 \angle 126.87^\circ \quad 2'$$

Since $\alpha = -0.8$ $\omega = 0.6$

$$\Rightarrow v(t) = \left[35 + 25 e^{-0.8t} \cos(0.6t + 126.87^\circ) \right] u(t) \quad t \geq 0 \quad 2'$$