

Homework 1

Due date:

Mar.12th, 2018

Turn in your homework in class

Rules:

- Please try to work on your own. Discussion is permissible, but identical submissions are unacceptable!
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

1. (16%=4*4%) Determine the current flowing through an element if the charge flow is given by (a)(b).

Also, find the charge flowing through an element if the current is given by (c)(d).

(a) $q(t) = 1.7t(1 - e^{-1.2t}) \text{ nC}$

(b) $q(t) = 0.2t\sin(120\pi t) + \cos(2e^{-\sin t}) \text{ mC}$

(c) $i(t) = 4e^{-t} - 3e^{-2t} \text{ mA}, q(0) = 0.2 \text{ A}$

(d) $i(t) = 12e^{-3t} \cos(40\pi t) \text{ nA}, q(0) = 2.28 \text{ pA}$

Solutions:

(a) $q(t) = 1.7t(1 - e^{-1.2t}) \text{ nC}$

$$i(t) = \frac{dq(t)}{dt} = \frac{d}{dt} [1.7t(1 - e^{-1.2t})] * 10^{-9} \text{ A}$$

$$= [1.7(1 - e^{-1.2t}) + 1.7t * (-1.2) * (1 - e^{-1.2t})] * 10^{-9} \text{ A}$$

$$= 1.7(1 - e^{-1.2t} + 1.2te^{-1.2t}) \text{ nA}$$

(b) $q(t) = 0.2t\sin(120\pi t) + \cos(2e^{-\sin t}) \text{ mC}$

$$i(t) = \frac{dq(t)}{dt} = \frac{d}{dt} [0.2t\sin(120\pi t)] + \frac{d}{dt} [\cos(2e^{-\sin t})] \text{ mA}$$

$$= 0.2 \sin(120\pi t) + 0.2t * 120\pi \cos(120\pi t) + (-\sin(2e^{-\sin t})) \frac{d}{dt} (2e^{-\sin t}) \text{ mA}$$

$$= 0.2 \sin(120\pi t) + 75.4t\cos(120\pi t) + 2 \cos(t) * e^{-\sin t} * \sin(2e^{-\sin t}) \text{ mA}$$

(c) $i(t) = 4e^{-t} - 3e^{-2t} \text{ mA}, q(0) = 0.2 \text{ C}$

$$q(t) = \int_0^t i(t)dt + q(0) = \int_0^t (4e^{-t} - 3e^{-2t})dt + 0.2 * 10^3 \text{ mC}$$

$$= \left(-4e^{-t} + \frac{3}{2}e^{-2t}\right) \Big|_0^t + 200 \text{ mC} = -4e^{-t} + \frac{3}{2}e^{-2t} + 202.5 \text{ mC}$$

(d) $i(t) = 12e^{-3t} \cos(40\pi t) \text{ nA}, q(0) = 2.28 \text{ pC}$

$$q(t) = \int_0^t i(t)dt + q(0) = \int_0^t 12e^{-3t} \cos(40\pi t) dt + 2.28 * 10^{-3} \text{ nC}$$

$$= 12e^{-3t} * \frac{-3 \cos(40\pi t) + 40\pi \sin(40\pi t)}{9 + (40\pi)^2} \Big|_0^t + 2.28 * 10^{-3} \text{ nC}$$

$$= 12e^{-3t} * \frac{-3 \cos(40\pi t) + 40\pi \sin(40\pi t)}{9 + (40\pi)^2} + 4.56 * 10^{-3} \text{ nC}$$

2. (14%) Find the current i_1 and i_2 shown in Figure 1.

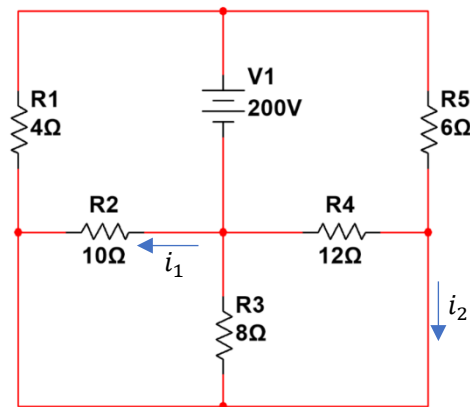


Figure 1

$$\frac{200 - V_B}{4\Omega} + \frac{200 - V_B}{6\Omega} = \frac{V_B}{12\Omega} + \frac{V_B}{8\Omega} + \frac{V_B}{10\Omega}$$

$$\frac{5}{12}(200 - V_B) = \frac{37}{120} V_B$$

$$V_B = \frac{10000}{87} \text{ V}$$

$$i_1 = \frac{-V_B}{10\Omega} = -\frac{1000}{87} \text{ A} = -11.49 \text{ A}$$

$$i_2 = \frac{200 - V_B}{6\Omega} - \frac{V_B}{12\Omega} = \frac{400}{87} \text{ A} = 4.60 \text{ A}$$

3. (14%) Find the power absorbed by each of the elements from p_1 to p_5 with the following circuit shown in Figure 2.

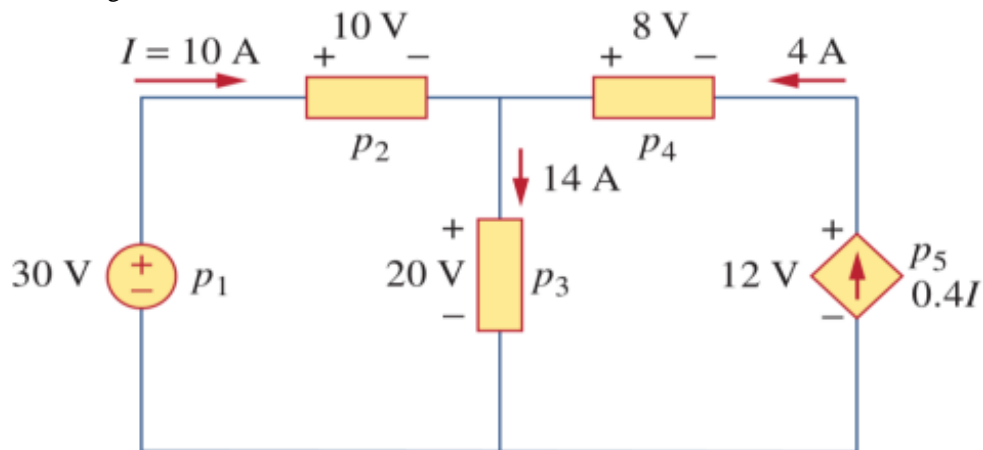


Figure 2

$$p_1 = 30 \text{ V} * (-10 \text{ A}) = -300 \text{ W}$$

$$p_2 = 10 \text{ V} * 10 \text{ A} = 100 \text{ W}$$

$$p_3 = 20 \text{ V} * 14 \text{ A} = 280 \text{ W}$$

$$p_4 = 8 \text{ V} * (-4 \text{ A}) = -32 \text{ W}$$

$$p_5 = 12 \text{ V} * (-0.4 * 10 \text{ A}) = -48 \text{ W}$$

4. (14%) Find i_1, i_6, v and power on the voltage source of 8V with the circuit shown in the Figure 3.

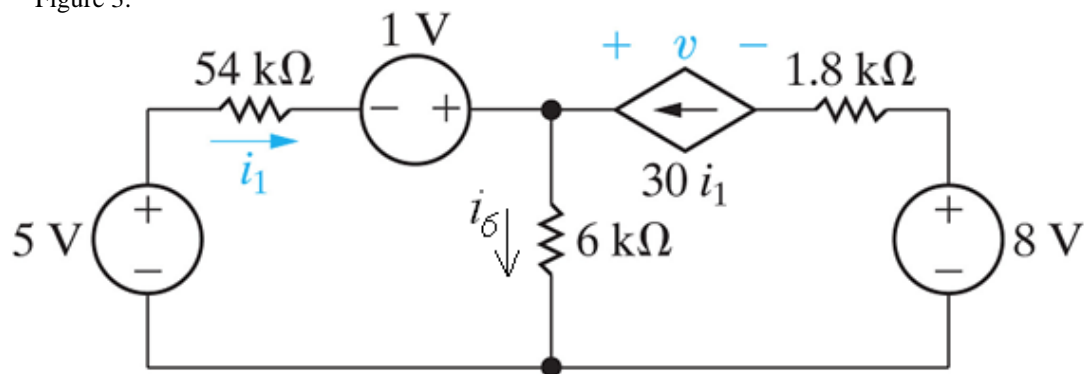


Figure 3

$$\text{KVL left : } -5 + 54,000i_1 - 1 + 6000i_6 = 0$$

$$\text{KCL top : } i_1 + 30i_1 = i_6 = 31i_1$$

$$\Rightarrow -5 + 54,000i_1 - 1 + 6000(31i_1) = 0$$

$$\Rightarrow [54,000 + (6000)(31)]i_1 = 6 \quad \therefore i_1 = 25\mu\text{A}$$

$$\text{KVL right : } -v + (6000)(31i_1) - 8 + 1800(30i_1) = 0$$

$$\Rightarrow v = (6000)(31)(25\mu) - 8 + (1800)(30)(25\mu) = -2 \text{ V}$$

$$i_1 = 25\mu\text{A}, i_6 = 31i_1 = 775\mu\text{A}, v = -2 \text{ V}$$

$$P_{8V} = -8 * 750\mu\text{W} = -6 \text{ mW}$$

5. (14%) Use nodal analysis to find V_o in the circuit of Figure 4.

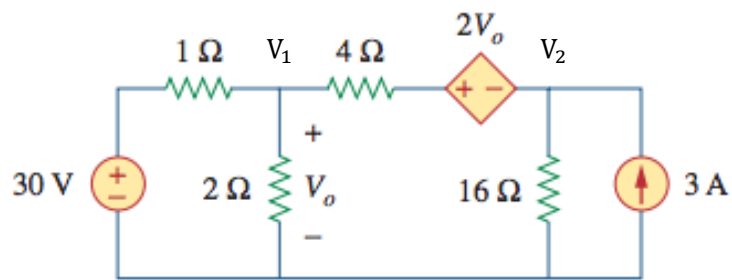


Figure 4

$$\left\{ \begin{array}{l} \text{Node 1: } \frac{30 - V_1}{1} + \frac{V_2 + 2V_o - V_1}{4} + \frac{0 - V_1}{2} = 0 \\ \text{Node 2: } 3 + \frac{0 - V_2}{16} + \frac{V_1 - (V_2 + 2V_o)}{4} = 0 \\ V_1 = V_o \end{array} \right.$$

$$\Rightarrow V_o = 22.34 \text{ V}$$

6. (14%) Apply mesh analysis to find I_x in the circuit of Figure 6.

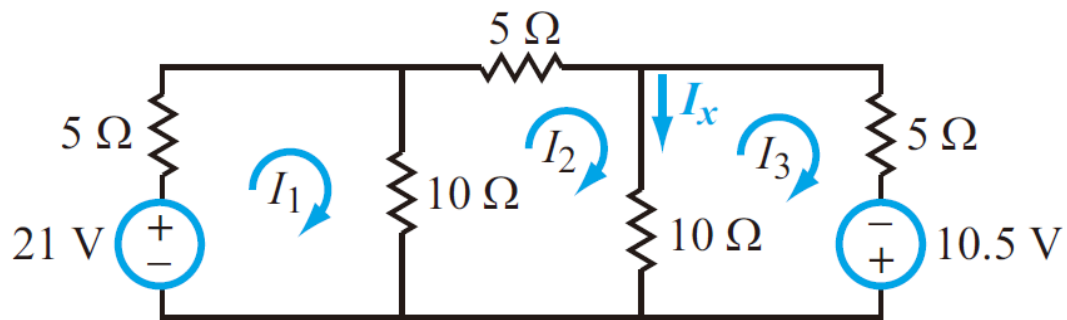


Figure 6

Solution:

$$\text{Mesh 1:} \quad -21 + 5I_1 + 10(I_1 - I_2) = 0$$

$$\text{Mesh 2:} \quad 10(I_2 - I_1) + 5I_2 + 10(I_2 - I_3) = 0$$

$$\text{Mesh 3:} \quad 10(I_3 - I_2) + 5I_3 - 10.5 = 0$$

Solution is:

$$I_1 = \frac{13}{5} \text{ A}, \quad I_2 = \frac{9}{5} \text{ A}, \quad I_3 = \frac{19}{10} \text{ A},$$

and

$$I_x = I_2 - I_3 = \frac{9}{5} - \frac{19}{10} = -\frac{1}{10} = -0.1 \text{ A}.$$

7. (14%) Determine A if $V_{\text{out}}/V_s = 9$ in the circuit of Figure 7.


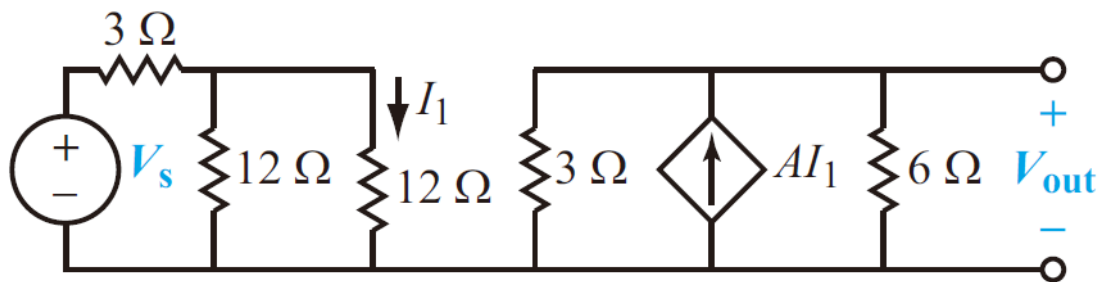


Figure 7

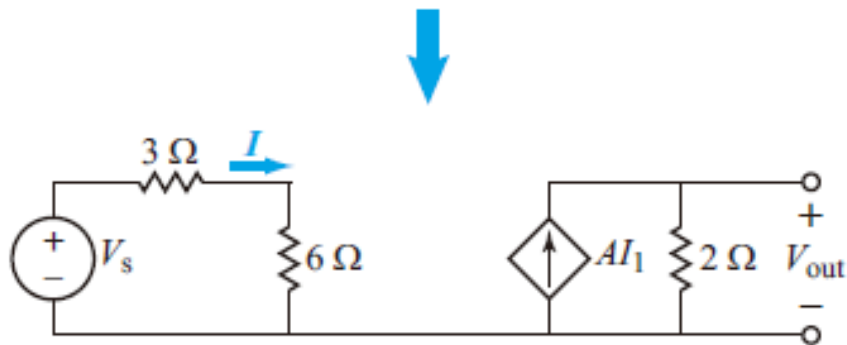

$$I = \frac{V_s}{9}$$

$$I_1 = \frac{I}{2} = \frac{V_s}{18}$$

$$V_{\text{out}} = AI_1 \times 2 = \frac{AV_s}{18} \times 2 = \frac{AV_s}{9}$$

$$\frac{V_{\text{out}}}{V_s} = \frac{A}{9} = 9.$$

Hence

$$A = 81.$$