

上海科技大学

2017-2018 学年第 1 学期本科生第 2 次期中考试卷

姓名: _____

开课单位: 信息学院

学院: _____

授课教师: 周平强

学号: _____

考试科目: 《电路基础》

课程代码: EE111

考试时间: 2016 年 11 月 28 日 10 点 15 分 – 12 点 15 分。

考试成绩录入表:

题目	1	2	3	4	5	总分
计分						
复核						

评卷人签名:

复核人签名:

日期:

日期:

编写说明:

1. 要求评卷人和复核人不能是同一人。
2. 试卷内页和答题纸编排格式由各学院和出题教师根据实际需要自定, 每页须按顺序标注页码(除封面外), 要求排版清晰、美观, 便于在页面左侧装订。为方便印刷归档, 建议使用 A4 双面印刷(学校有印刷一体机提供)。
3. 主考教师编写试卷时尽可能保证试题科学、准确、合理, 如考试过程中发现试题有误, 主考教师需负责现场解释, 此类情况学校将作为教学评估记录的一部分。

Problem 1 (15 pts) — First-Order RL Circuit Analysis

The current and voltage at the terminals of the inductor in Fig. 1 are

$$i(t) = (4 + 4e^{-40t})\text{A}, t \geq 0; \quad v(t) = -80e^{-40t}\text{V}, t \geq 0.$$

- Find the numerical values of V_s , R , L , and I_0 (the initial current of L at $t = 0$);
- How many milliseconds after the switch has been closed does the energy stored in the inductor reach 9 Joule?

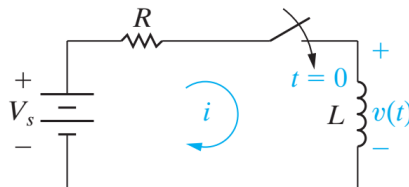


Fig. 1 for Problem 1.

Problem 2 (20 pts) — First-order RL Circuit Analysis

Before it closes at time $t = 0$, the switch in the circuit shown in Fig. 2 has been open for a long time. Find the current through the inductor $i_o(t)$ for $t \geq 0$.

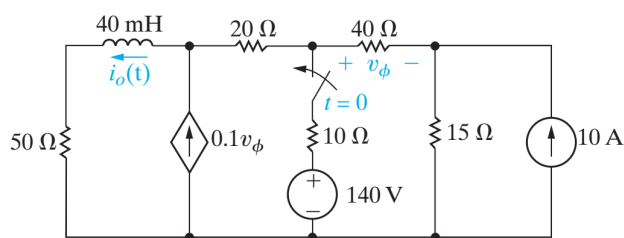


Fig. 2 for Problem 2.

Problem 3 (20 pts) — Second-order RLC circuit

The initial value of the voltage v in the circuit shown in Fig. 4 is zero, and the initial value of the capacitor current, $i_c(0^+)$, is 45mA. The expression for the capacitor current is known to be

$$i_c(t) = A_1 e^{-200t} + A_2 e^{-800t}, t \geq 0^+. \quad R = 250\Omega. \text{ Find}$$

- The values of L , C , A_1 and A_2 .
- The express for $v(t)$, $t \geq 0$.

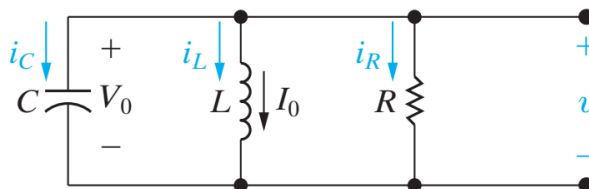


Fig. 5 for Problem 5.

Problem 4 (15 pts) — Second-order RLC circuit

Determine the Thevenin equivalent circuit of the circuit shown in Fig. 5 at terminals (a, b), given that $v_s(t) = 12 \cos 2500t$ V, $i_s(t) = 0.5 \cos(2500t - 30^\circ)$ A.

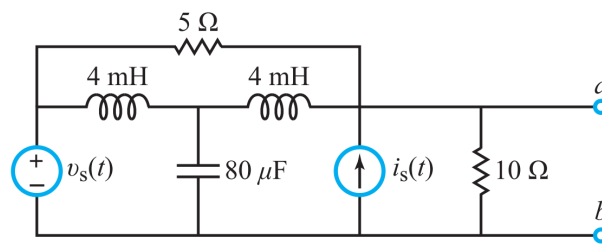


Fig. 5 for Problem 5.

Problem 5 (30 pts) — Second-order RLC circuit

In the circuit shown in Fig. 6, the switch was closed at $t = 0$ and re-opened at $t = 0.5$ s. Determine the response $i_L(t)$ for $t \geq 0$. Before $t = 0$, there is no energy stored in the inductor and capacitor.

Assume that $V_s = 18$ V, $R_s = 1\Omega$, $R_1 = 5\Omega$, $R_2 = 2\Omega$, $L = 2$ H, and $C_1 = \frac{1}{17}$ F.

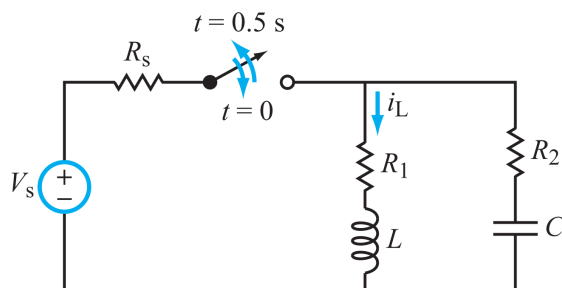


Fig. 6 for Problem 6.