

Discussion 6

Second-Order Circuits



Overview


Second-Order Circuits

- Initial and final values
- Source-Free RLC Circuits
 - Series
 - Parallel
- Step Response of RLC Circuits
 - Series
 - Parallel
- Second-Order Op Amp Circuits


Application

- automobile ignition circuit

Second Order Circuits

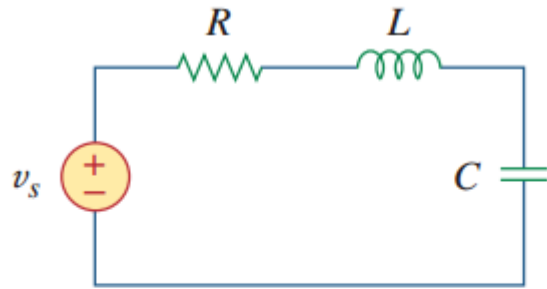


(a)

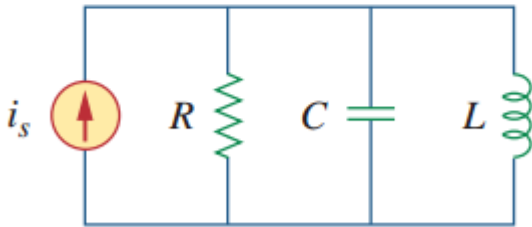


(b)

Different storage element

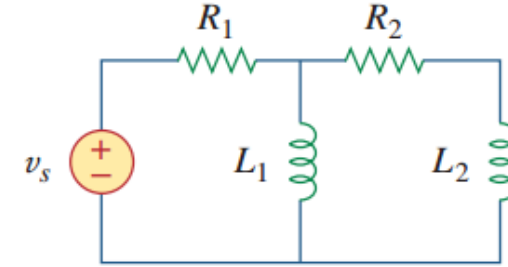

(c)

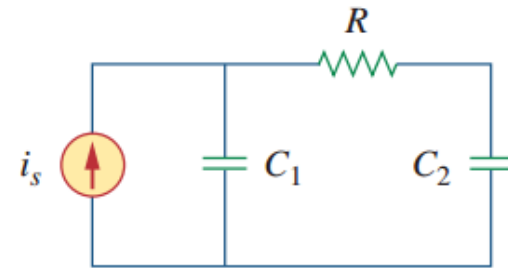

(d)

Same storage element




Second Order Circuits

- This time, though we will only consider **DC independent** sources
- Steps to find a solution $x(t)$:
 - **Step one:** Find initial and final values.
 - **Step two:** Extract the second-order differential equation out of the circuit.
 - **Step three:** Solve the second-order ODE and get the general solution of homogeneous equation -- $x_t(t)$.
 - **Step four:** $x(t) = x_{ss} + x_t(t)$ where x_{ss} is the final state value.
 - **Step five:** Substitute the initial values in and confirm the coefficients.

Initial and final values

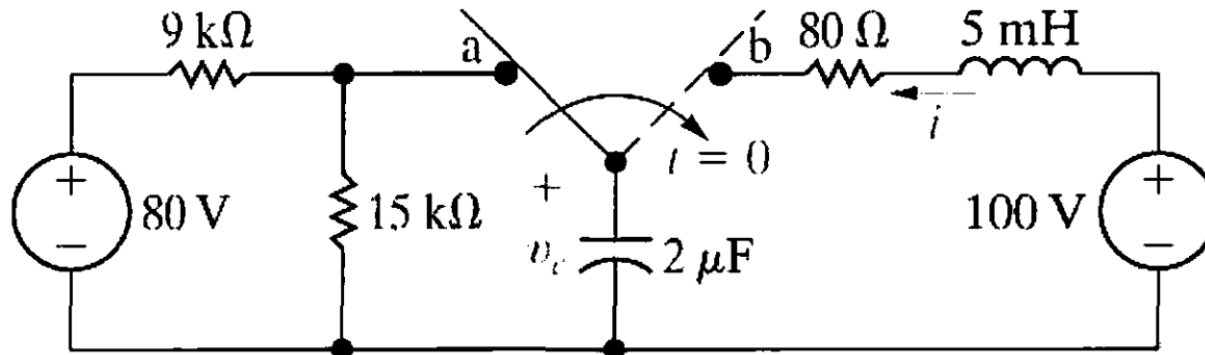
- Use methods of analysis you have learned before to find the **capacitor voltage** and the **inductor current** on **initial** and **final** states
- Regard the capacitor as **open circuit** and inductor as **short circuit**.
- **Example:**



Initial state: $i_l(0^+) = i_l(0^-) = 0$
 $v_c(0^+) = v_c(0^-) = 50\text{V}$

Final state: $i_l(\infty) = 0$
 $v_c(\infty) = 100\text{V}$


Source Free Second Order Circuits

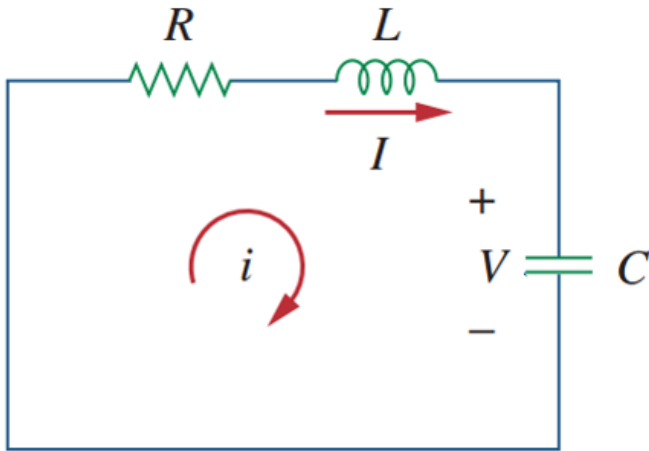

$$\text{KVL: } Ri + L \frac{di}{dt} + v = 0$$

$$\text{But } i = C \frac{dv}{dt}$$
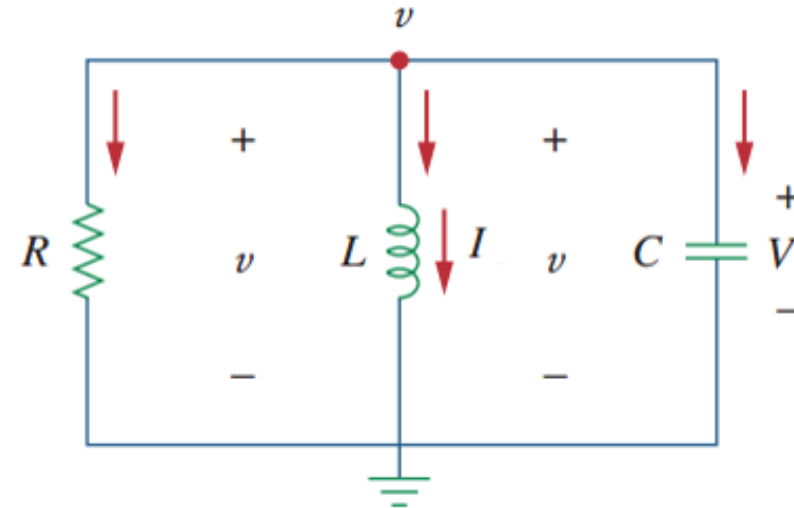
$$\text{So: } \frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$




$$\text{KCL: } \frac{v}{R} + C \frac{dv}{dt} + i = 0$$

$$\text{But } v = L \frac{di}{dt}$$

$$\text{So: } \frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

Step Response of RLC Circuits

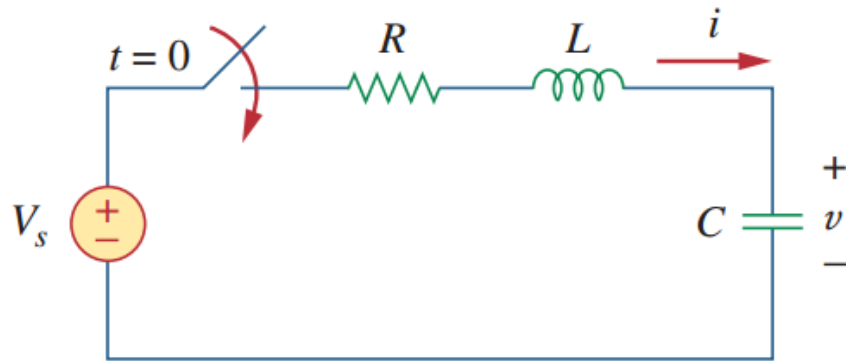
- When there is a DC source, the ODE becomes Inhomogeneous:



$$\text{KVL: } Ri + L \frac{di}{dt} + v = V_s$$

$$\text{But } i = L \frac{dv}{dt}$$
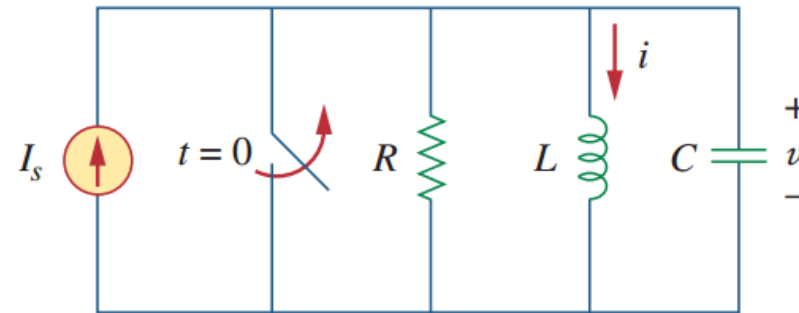
$$\text{So: } \frac{d^2 v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = \frac{V_s}{LC}$$




$$\text{KCL: } \frac{v}{R} + C \frac{dv}{dt} + \frac{1}{L} \int_{-\infty}^t v dt = I_s$$

$$\text{But } v = C \frac{di}{dt}$$

$$\text{So: } \frac{d^2 i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + \frac{1}{LC} i = \frac{I_s}{LC}$$



Example

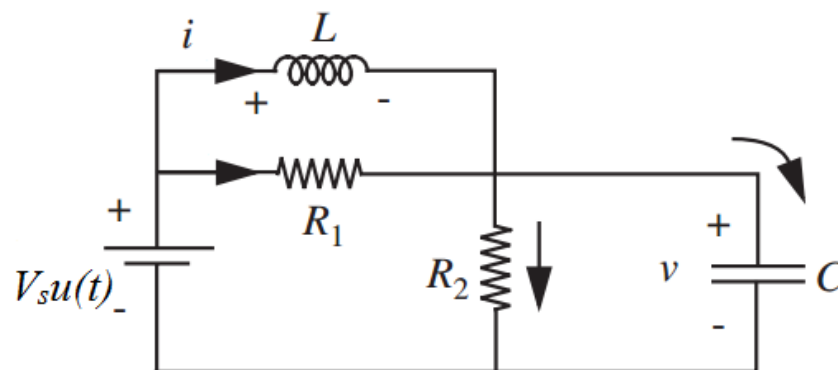


Initial state:

$$i(0^+) = i(0^-) = 0 \quad v(0^+) = v(0^-) = 0$$

Final state:

$$i(\infty) = \frac{V_s}{R_2} \quad v(\infty) = V_s$$

Example

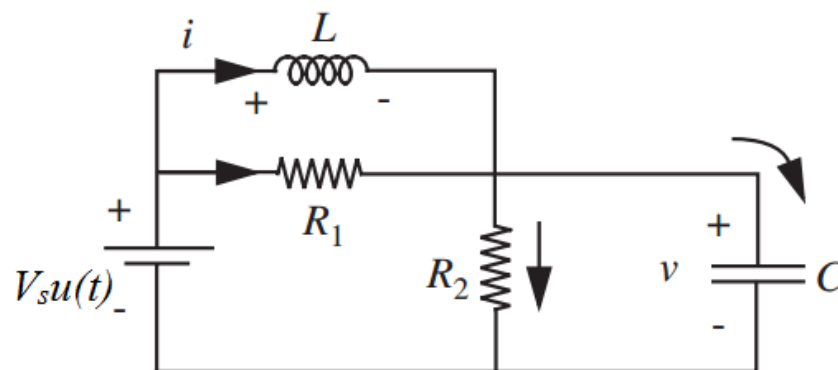

Since we got a circuit with voltage source, so generate the differential equation in terms of **capacitor voltage v** . Apply KVL we obtain:

$$v + L \frac{di}{dt} = V_s \quad (1)$$


Then we rewrite i in terms of v :

$$i = C \frac{dv}{dt} + \frac{v}{R_2} - \frac{(V_s - v)}{R_1} \quad (2)$$

Substitute (2) into (1) then

$$\frac{d^2 v}{dt^2} + \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \frac{1}{LC} \frac{dv}{dt} + \frac{1}{LC} v = \frac{1}{LC} V_s$$

Example

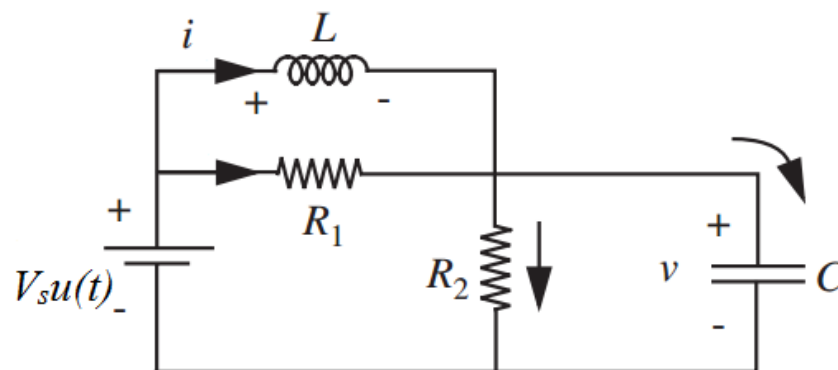


$$\frac{d^2 v}{dt^2} + \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \frac{1}{C} \frac{dv}{dt} + \frac{1}{LC} v = \frac{1}{LC} V_s$$

Firstly we solve the homogeneous equation ③ to find the general solution.

$$\frac{d^2 v}{dt^2} + \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \frac{1}{C} \frac{dv}{dt} + \frac{1}{LC} v = 0 \quad \text{③}$$

Is the circuit **overdamped, critically damped or underdamped?**

Example

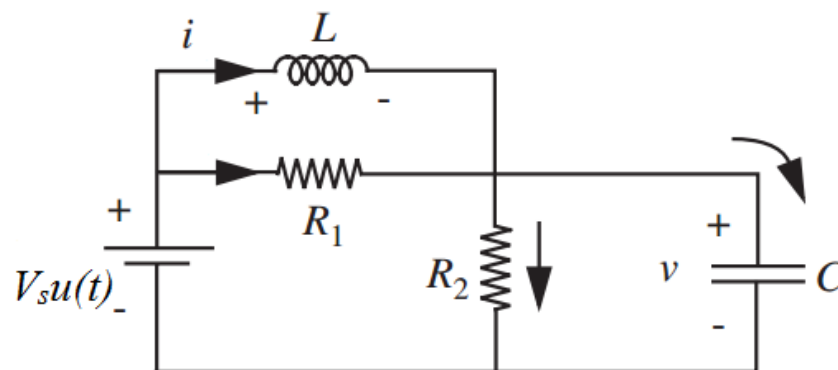

It depends on the coefficients $\alpha = \frac{1}{2} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \frac{1}{C}$ and $\omega_0 = \frac{1}{\sqrt{LC}}$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$\alpha > \omega_0 \Rightarrow$ two distinct real solutions $\Rightarrow v_t(t) = Ae^{s_1 t} + Be^{s_2 t}$ **overdamped**


$\alpha = \omega_0 \Rightarrow$ only one real root $\Rightarrow v_t(t) = Ae^{s_1 t} + Bte^{s_1 t}$ **critically damped**

$\alpha < \omega_0 \Rightarrow$ two complex conjugate roots $\Rightarrow v_t(t) = Ae^{s_1 t} + Be^{s_2 t}$ **underdamped**


$$\Rightarrow v_t(t) = Ae^{-\alpha t} \cos(\omega_d t) + Be^{-\alpha t} \sin(\omega_d t) \quad \text{where } \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$



Example

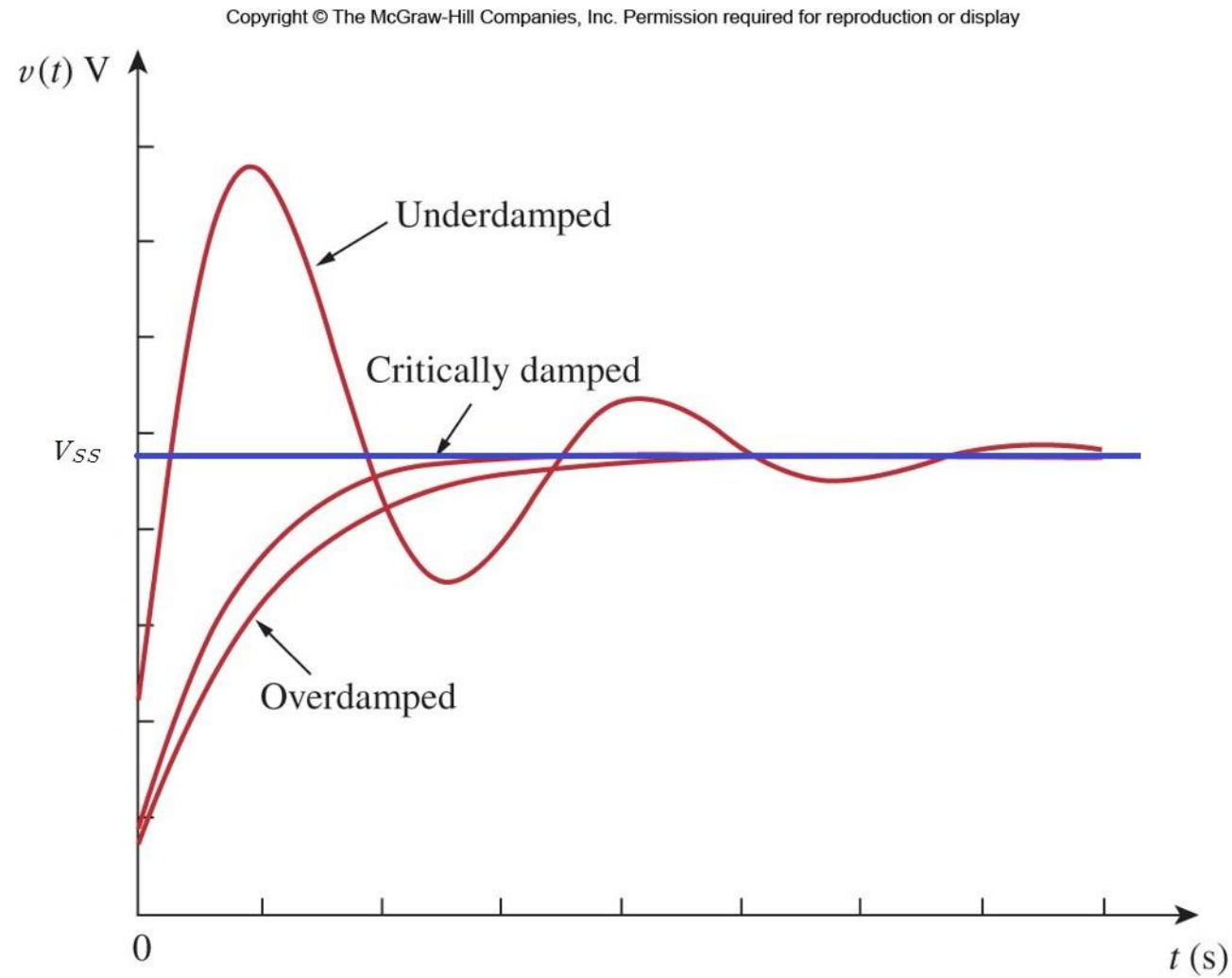

Example

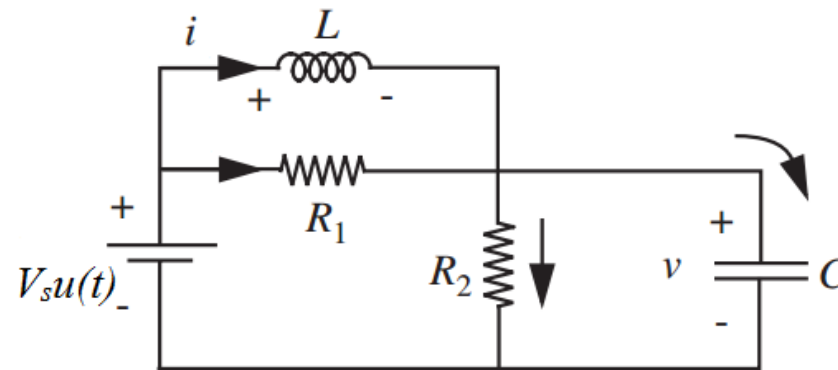

We know that $v(\infty) = V_s$

So

$$v(t) = v_s + v_t(t)$$

Then substitute the initial values in and confirm the coefficients A and B.

$$i(0^+) = i(0^-) = 0 \quad v(0^+) = v(0^-) = 0$$



Second Order Circuits

- Please think: what if the voltage source is an AC source?
 - Is there still a steady state?
 - How to solve the ODE?



Overview

Second-Order Circuits

- Initial and final values
- Source-Free RLC Circuits
 - Series
 - Parallel
- Step Response of RLC Circuits
 - Series
 - Parallel
- Second-Order Op Amp Circuits

Application

- automobile ignition circuit

Second-Order Op Amp Circuits

Determine the differential equation in terms of v_o .

For the first op amp:

$$\frac{v_o - 0}{R} = C \frac{dv_1}{dt}$$

For the second op amp:


$$\frac{-v_1 - 0}{R} = C \frac{dv_2}{dt}$$

But

$$v_o = -v_2$$

So
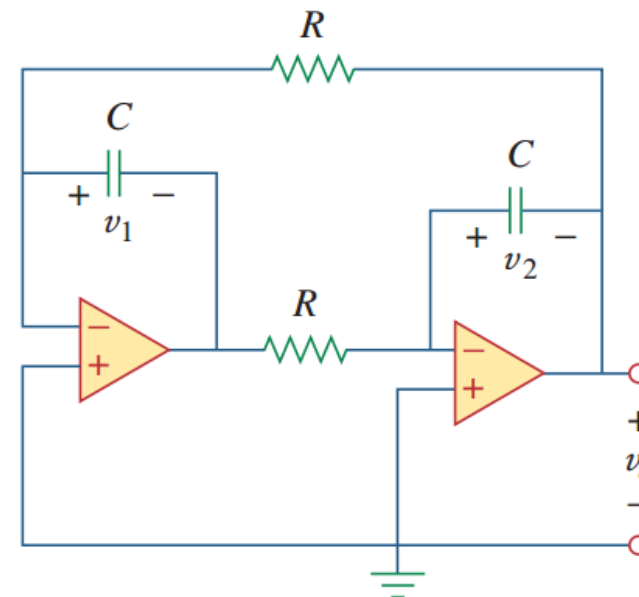
$$\frac{d^2 v_o}{dt^2} - \frac{1}{R^2 C^2} v_o = 0$$





Overview

Second-Order Circuits


- Initial and final values
- Source-Free RLC Circuits
 - Series
 - Parallel
- Step Response of RLC Circuits
 - Series
 - Parallel
- Second-Order Op Amp Circuits

Application


- automobile ignition circuit

Application: Automobile Ignition System

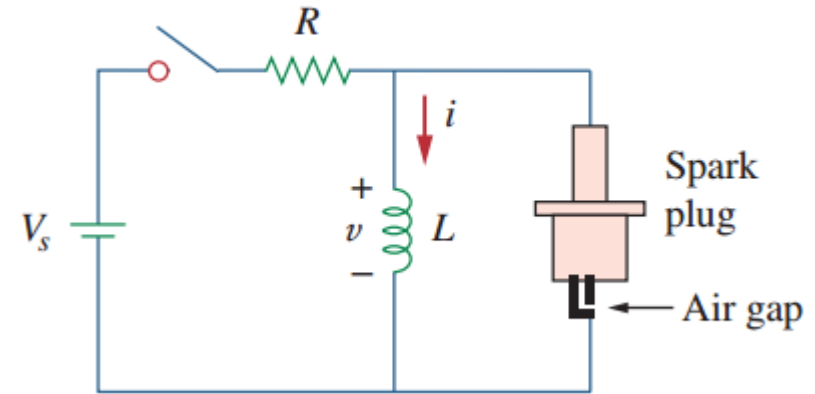- Mechanism: generate a voltage much higher than the voltage source through the transient response of the inductor.
- Please think:
 - What's different between (1) and (2) ?
 - Which one is better?
 - Is the circuit (2) overdamped, critically damped or underdamped when we could get a much higher voltage?
 - How to choose the value of R , C and L ?



(1)

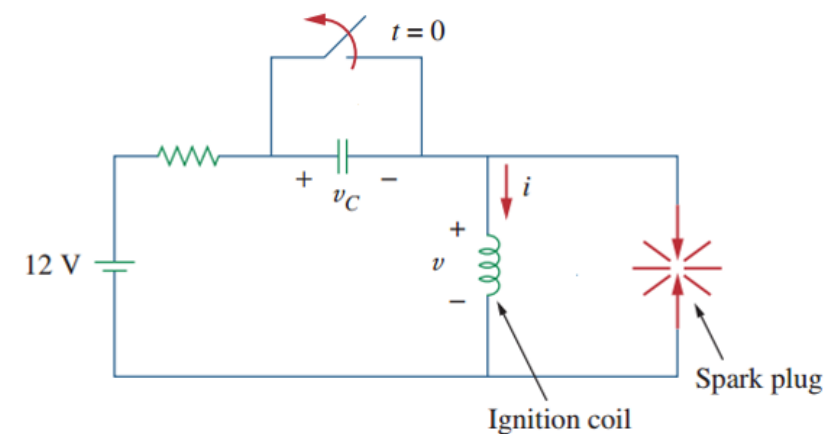

(2)

Application: Automobile Ignition System

- Regard the spark plug as open circuit. It becomes a series RLC circuit, in which:

- $\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$

- $\alpha = \frac{R}{2L}$


- $\omega_0 = \frac{1}{\sqrt{LC}}$

- $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$

- $i_{ss} = 0$

- $i(t) = Ae^{-\alpha t} \cos(\omega_d t) + Be^{-\alpha t} \sin(\omega_d t)$

- $v(t) = L \frac{di(t)}{dt}$

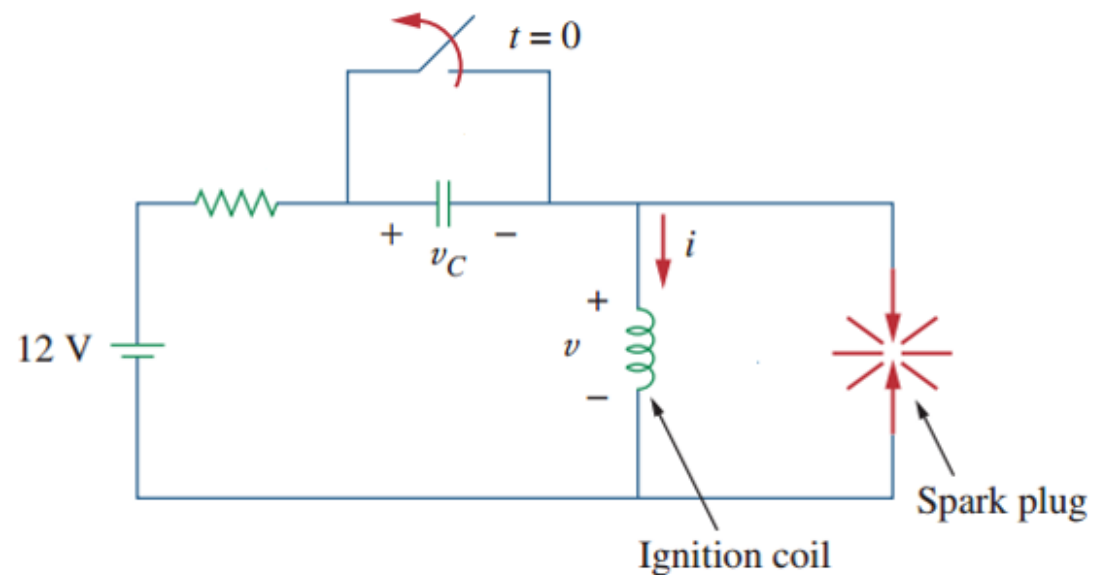

(2)



End